



Wrocław
University
of Science
and Technology


Actuators: relays & motors





References


- S. L Herman, Industrial motor control, Clifton Park, 2014
- T. R. Kuphaldt, Lessons In Electric Circuits, Volume II – AC, 6th Edition, 2007 (<http://www.faqs.org/docs/electric/AC/index.html>)
- J. Przepiorkowski, Silniki elektryczne w praktyce elektronika, BTC





Outline


- relays
 - electromechanical
 - electronic relay (SSR – Solis State Relay)
- Electric motors

Relays

SPST 

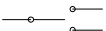SPDT 

DPST 


DPDT 

Single(Double)Pole

Single(Double;Triple)Throw

CO – centre off/change over
example
SPTT=SPCO

Relay

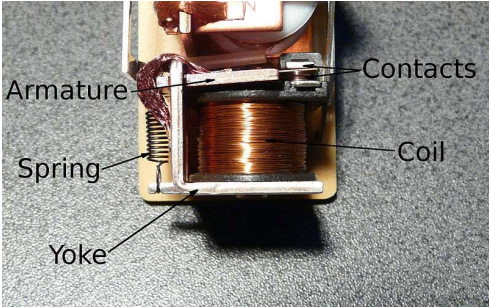

Armature


Spring

Yoke

Contacts

Coil

Relays



AC relay

reed relay

Relays - types

- Regular
- Latching (bistable)
- Polarized relay
- Reed relay
 - (mercury wetted)
- Contactor

- Solid state relay
 - transistor
 - triac
 - Thyristor

- Other (safety switches, over current,.....)

Relay - diagram symbol

Ohm's law for inductance

$$U_L = L \frac{dI}{dt}$$

$$U_L = X_L I_L = \frac{1}{i\omega C} I_L$$

TIPS:

- higher voltage applied – faster changes of current
- fast changes in current – higher voltage induced
- when current change „slope direction” – voltage change polarity:
 - positive voltage applied – current increased
 - current decreased – negative voltage induced

Switching on and off an inductor

13

Relay – spark discharge

High voltage can destroy transistor and relay and can be very dangerous !!!!

14

Switching on and off an inductor

protection diode;
flyback diode;
clamp diode;

I_L

U_{CE}

U_L

$V_{CC} + U_D$

V_{CC}

$-U_D$

15

Switching on and off an inductor

I_L

U_{CE}

U_L

$V_{CC} + U_b + U_z$

$V_{CC} + U_D$

V_{CC}

$-U_D - U_z$

$-U_D$

16

Switching on and off an inductor

- series resistor influence

The diagram shows a transistor switching an inductor L with a series resistor R . The collector is connected to V_{CC} . The waveforms show the current I_L rising to a peak and then decaying, the collector-emitter voltage U_{CEI} , and the inductor voltage U_L . The peak voltage across the inductor is $V_{CC} + U_D + U_Z$ during turn-off, and $V_{CC} + U_D$ during turn-on. The inductor voltage U_L is V_{CC} during turn-on and $-U_D - U_Z$ during turn-off.

17

Decreasing rise time (off to on time)

1. Increase V_{CC}
 2. add R_s to preserve I_{max}
 3. result => higher power dissipation

18

Decreasing rise time with current limit

$V_{CC} > U_{MNom}$

Driving relays and motors

$I <= 1A$

19

Driving relays and motors

74HC04

20

Darlington array ULN2004

LOGIC DIAGRAM

ULN2004A: $R_{10} = 2.7 k\Omega$
 ULN2004B: $R_{10} = 2.7 k\Omega$
 ULN2004A: $R_{10} = 10.5 k\Omega$

<http://focus.ti.com/lit/ds/symlink/uln2004a.pdf>

21

Driving relay/motor with MOSFET and IGBT


MOSFET
T
BUZ...
IRF....
1-30A...


IGBT
..10-300A...


Solid State Relays (SSR)
Solid State Contactor (SSC)


SSR of different types
can be used for AC driven mechanical relays

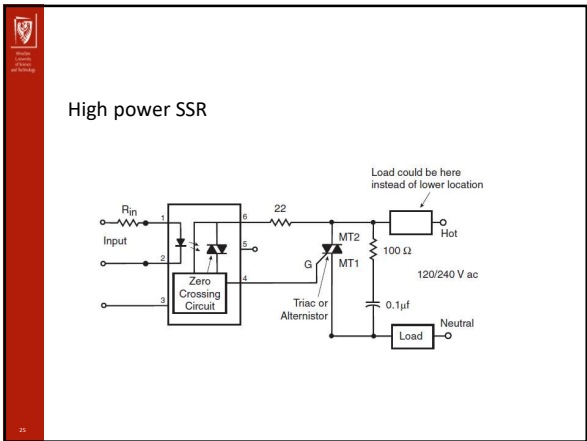
- Usually small power but can drive any type of load (including induction)
• AC and DC applications
- Be careful with inductive load – the load can be not switched off !!!
• AC applications only




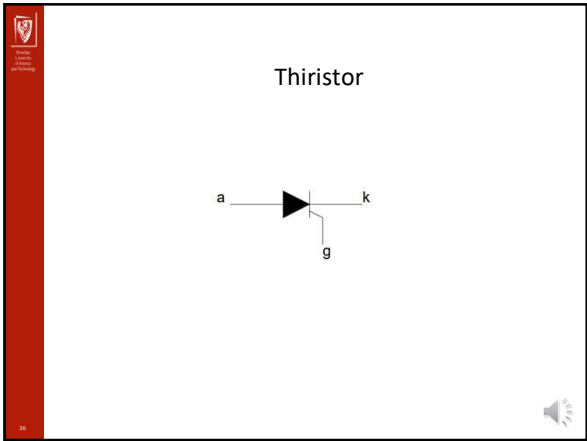

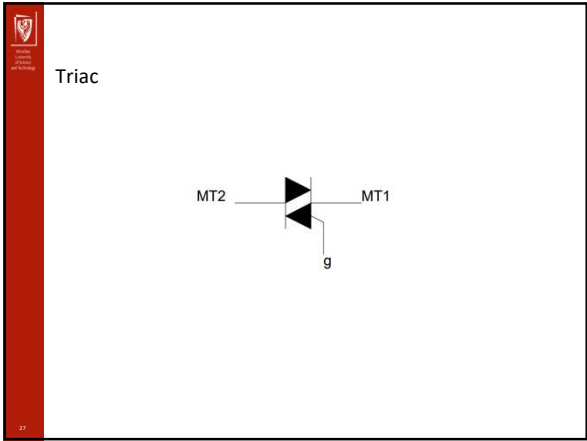

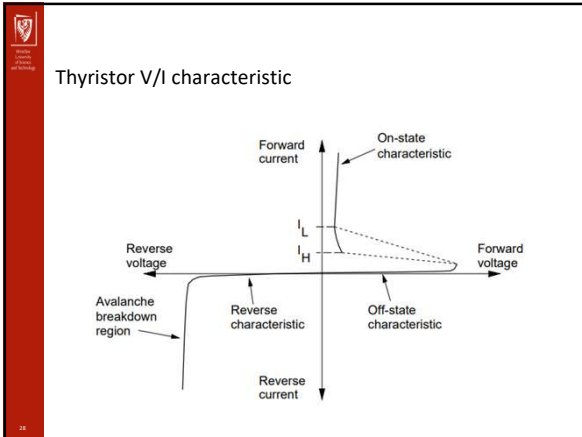

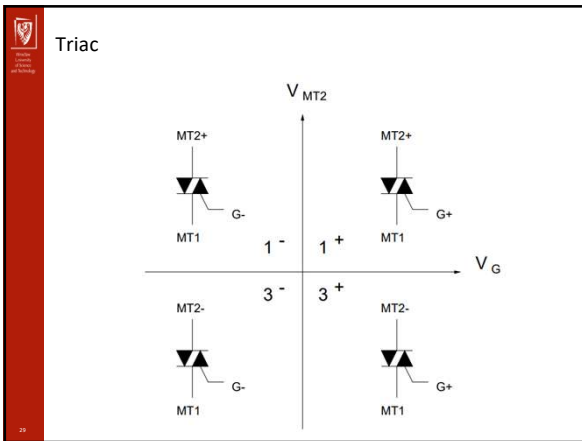

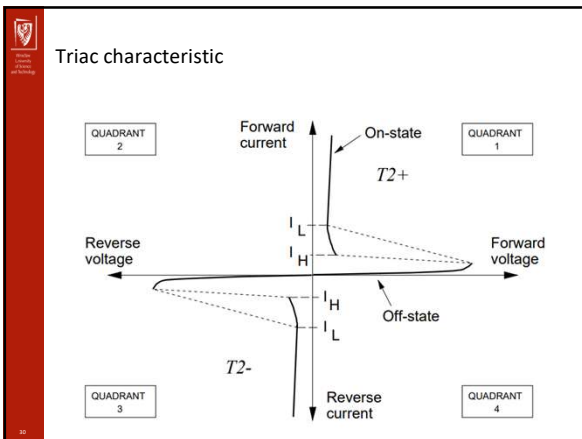

Important parameters:


gate current I_{GT}
 latch current I_L
 holding current I_H

•Uncontrolled triac switching:


- Noise in the gate circuit (filter and shunt the gate)
- Exceeding dV_{COM}/dt (during switching off of the inductive load – **snubber**)
- Exceeding dI_{COM}/dt (unexpected current shutdown – **uH inductance without saturation**)
- Momentary exceeding of dV_D/dt (without permanent exceeding of V_{DRM} – **network filtering; MOV**)

RC snubber


Shaded pole induction motor

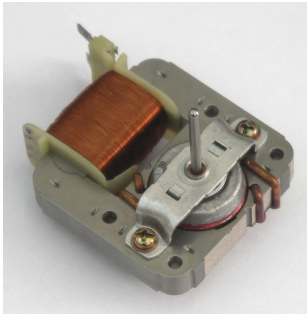

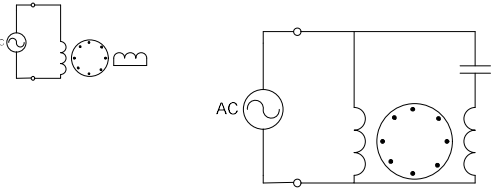Capacitor Run
Permanent Split Capacitor(PSD Motor)



Split Phase Induction Motor

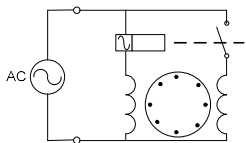



Squirrel cage – drivig inverter

Fig. 1 A Three Phase Inverter Circuit

Fig. 2. Programmed Harmonic Elimination of Fifth and Seventh Harmonics

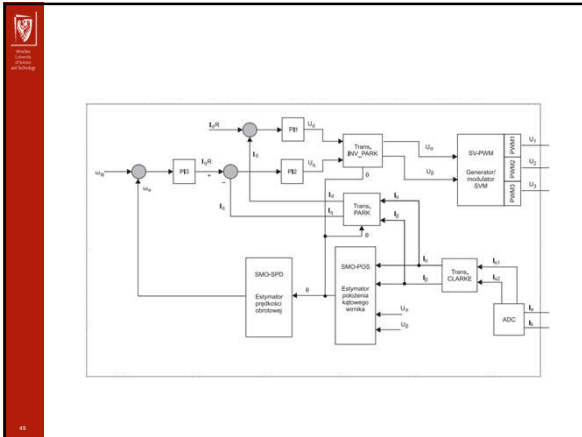Inverter
IRAMS10UP60A
by International Rectifier



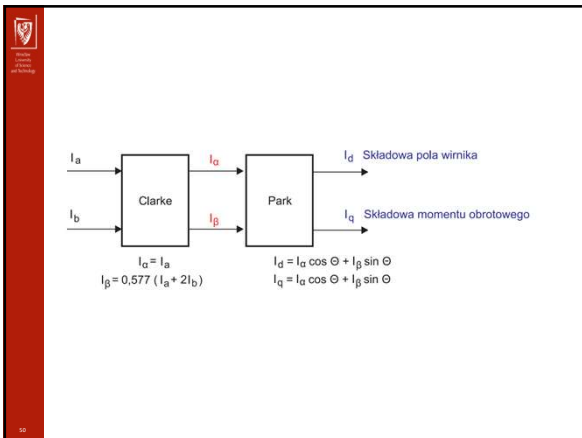

Braking resistor

$$J = J_{Motor} + J_{Load} \quad \text{inertial momentum}$$

$$P_B = \frac{J\omega_B(\omega_B - \omega_0)}{t} \quad \text{Braking power}$$

$$R = \frac{V_{DC}^2}{P_B} \quad \text{Resistor}$$

$$P_{Res} = 1.30 * (P_B - P_{Inv}) \quad \text{Resistor power}$$

The diagram illustrates the recommended spacing for cables of different classes. Class 1 and Class 2 cables are spaced 5cm apart. Class 2 and Class 3 cables are spaced 15cm apart. Class 3 and Class 4 cables are spaced 15cm apart. Cables of the same class are spaced 50cm apart. A 1m spacing is also indicated for the overall run. The cables are shown above a PEC (Perfect Electric Conductor) ground plane.

The cables from adjustable **speed inverter** drives to their motors may be specified by the drive manufacturers to have **600mm** or more spacing from any other parallel run of cable (**drives are perhaps the noisiest devices on the planet!**).

Figure from: Tim Williams, „EMC for Product Designers“, Fifth edition, Elsevier, 2017.





Direction control - H bridge

TIPS:
BJT, MOSFET, IGBT transistors can be used,
diodes conduct self inductance currents

current limit or control

H bridge operation 1


drive


slow decay

H bridge operation 2


drive


slow decay

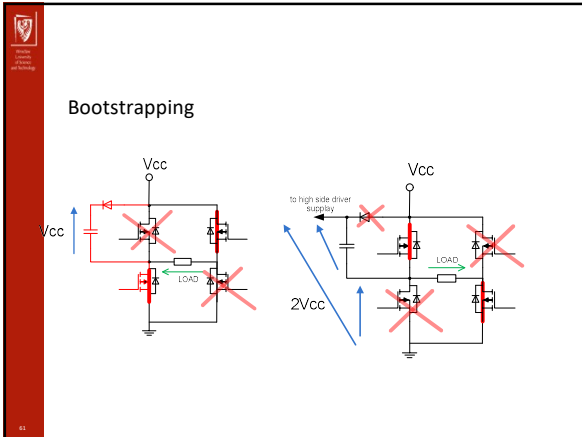


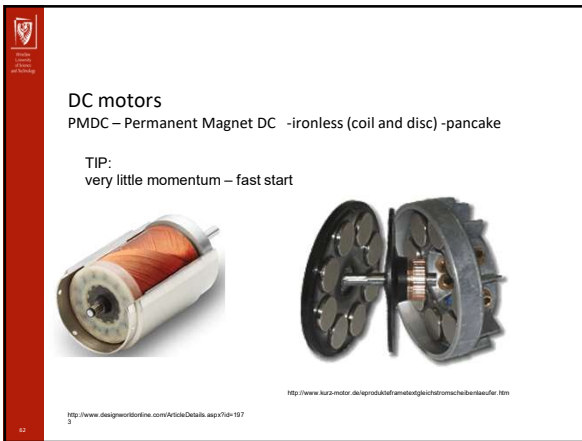


Type	Advantages	Disadvantages	Typical Application	Typical Drive
AC Induction (Shaded Pole) (31)	Least expensive Long life low power	Rotation slips from frequency Low starting torque	Fans	difficult to control
AC Induction (split phase capacitor) (34)	Medium power high starting torque	Rotation slips from frequency	Appliances Stationary Power Tools	Uni/Poly-phase AC
AC Squirrel cage 3ph (40)	High power	Rotation slips from frequency	Industry/ hp machines	Inverter frequency Vector control (if/contant)
Brushed DC (41)	Low initial cost Simple speed control	Maintenance (brushes) Medium lifespan	Treadmill exercisers automotive motors (seats, blowers, windows)	Direct DC or PWM
BLDC (49)	Long lifespan low maintenance High efficiency	High initial cost Requires a controller	Hard drives CD/DVD players electric vehicles	DC switching, PWM
Universal motor (51)	High starting torque, compact, high speed	Maintenance (brushes) Medium lifespan	Portable tools Grid powered	Uni-phase AC or Direct DC
Brushed DC 1ph/2ph (66)	Precision positioning High holding torque	High initial cost Requires a controller	Positioning in printers and floppy drives	DC switching
AC Synchronous (82)	Rotation in-sync with freq - hence no slip long-life	More expensive	Industrial motors Clocks Audio turntables tape drives	Uni/Poly-phase AC

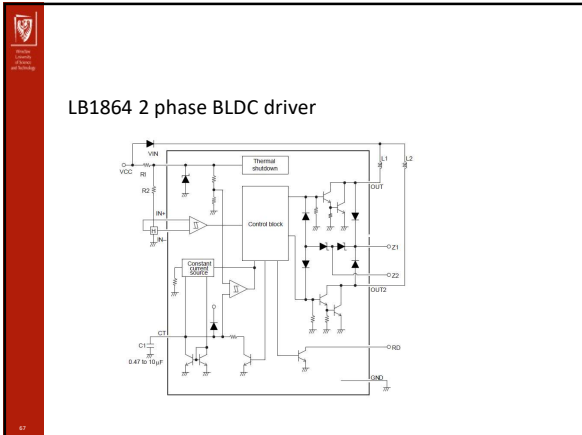


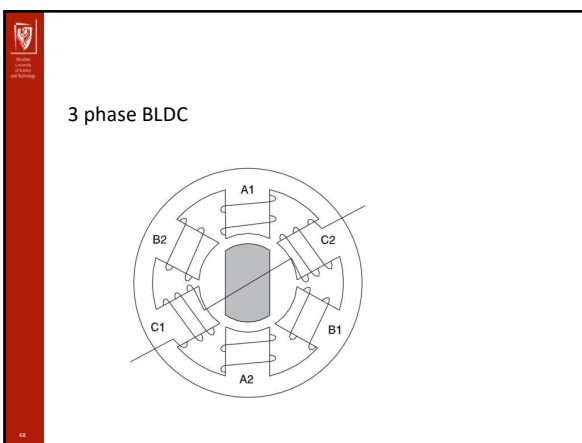


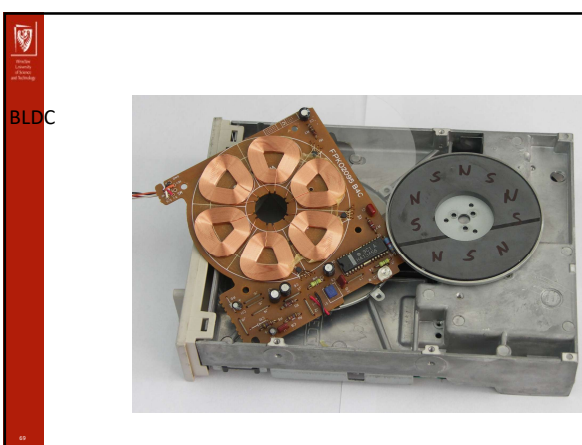




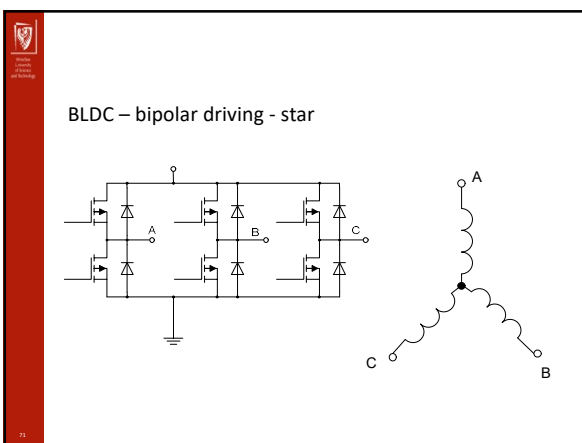

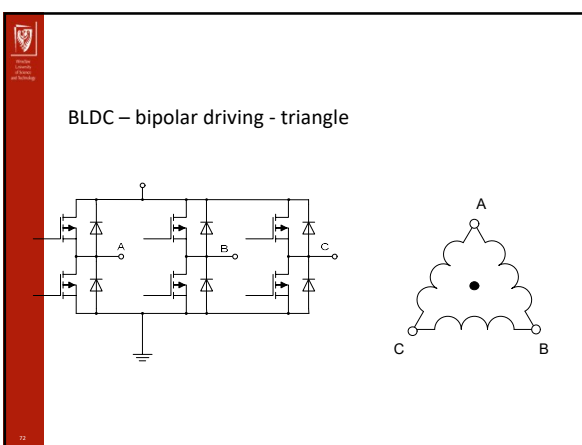

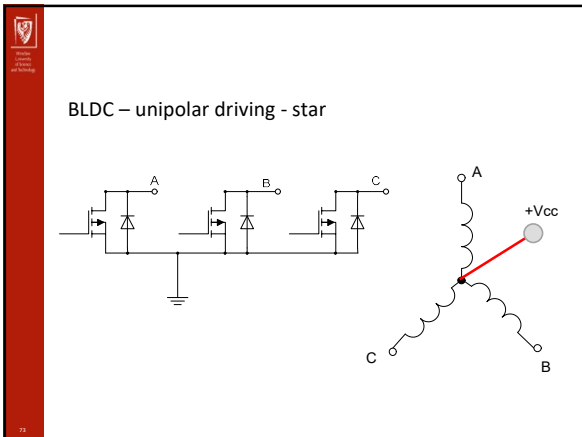


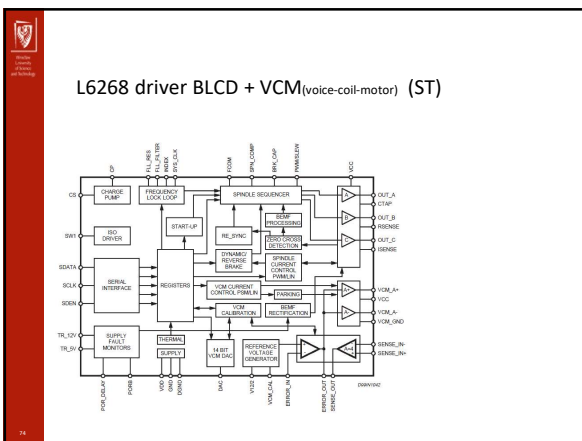

Type	Advantages	Disadvantages	Typical Application	Typical Drive
AC Induction (Shaded Pole) (31)	Least expensive Long life low-power	Rotation slips from frequency Low starting torque	Fans	difficult to control
AC Induction (split phase capacitor) (34)	Medium power high starting torque	Rotation slips from frequency	Appliances Stationary Power Tools	Uni/Poly-phase AC
AC Squirrel cage (40)	High power	Rotation slips from frequency	Industry hp machines	Inverter frequency Vector control (f-current)
Brushed DC (41)	Low initial cost Simple speed control	Maintenance (brushes) Medium lifespan	Treadmill exercisers automotive motors (seats, blowers, windows)	Direct DC or PWM
BL DC (49)	Long lifespan low maintenance High efficiency	High initial cost Requires a controller	Hard drives CD/DVD players electric vehicles	DC switching, Pwm
Universal motor (51)	High starting torque, compact, high speed	Maintenance (brushes) Medium lifespan	Portable tools Grid powered	Uni-phase AC or Direct DC
Stepper DC 1ph/2ph (56)	Precision positioning High holding torque	High initial cost Requires a controller	Positioning in printers and floppy drives	DC switching
AC Synchronous (82)	Rotation in-sync with freq - hence no slip long-life	More expensive	Industrial motors Clocks Audio turntables tape drives	Uni/Poly-phase AC

Permanent magnet replaced by electromagnet – universal motor

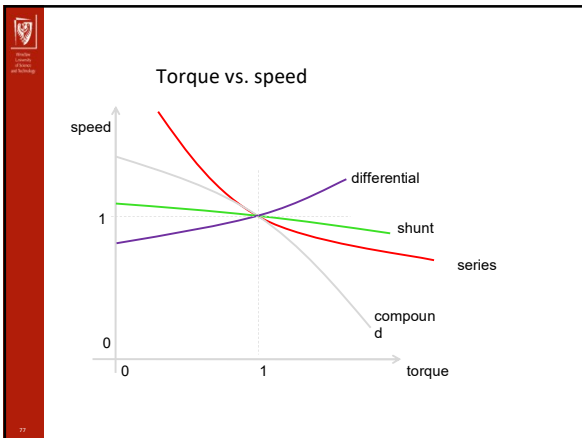series motor shunt motor compound motor differential compound m.



Universal motor – driver / controller

Tips:

1. voltage controlled
2. direction can be changed by switching stator or rotor winding
3. the example shown is the most simple

stepper motors- bi/uni-polar

bipolar winding
H bridge needed

unipolar winding
single swich

(2 phase) steppper motor internal conections

4 wires (bipolar only)

6 wires (bipolar handicapped/ /unipolar)

8 wires (bipolar/unipolar)

5 wires (unipolar only)

Unipolar/Bipolar stepper motor driving

Stepper motor – reluctance motor

Lessons In Electric Circuits, Volume II – AC By Tony R. Kuphaldt, Sixth Edition, last update July 25, 2007

Permanent magnet motor wave driving

Lessons In Electric Circuits, Volume II – AC By Tony R. Kuphaldt, Sixth Edition, last update July 25, 2007

Permanent magnet motor full step driving

Lessons In Electric Circuits, Volume II – AC By Tony R. Kuphaldt, Sixth Edition, last update July 25, 2007

Permanent magnet motor
half step driving

1,3,5,7 - phase
A
2,4,6,8 - phase
B

Step = $\frac{360 \text{ deg}}{N_{\text{teeth}} \cdot N_{\text{phases}}}$

18°

Full/microstep driving

Unipolar motor

Coils
A
B
C
D


Full Step
Half Step
Microstepping


Hybrid motor


1,3,5,7 - phase
A
2,4,6,8 - phase
B


Step = $\frac{360 \text{ deg}}{N_{\text{teeth}} \cdot N_{\text{phases}}}$


18°

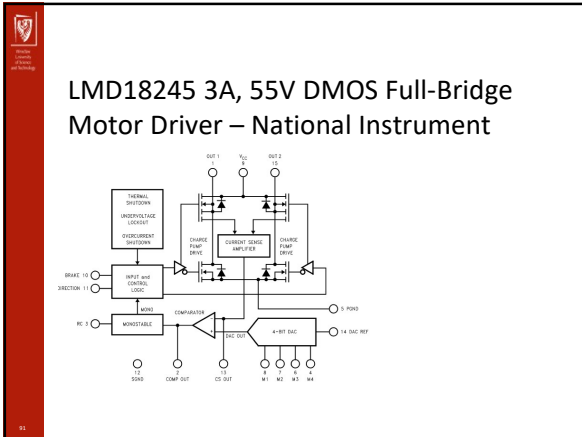

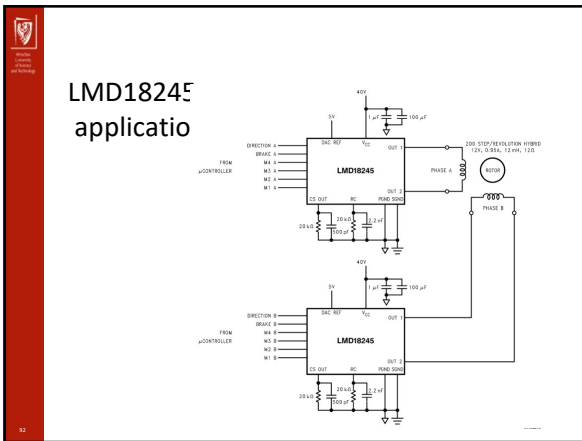

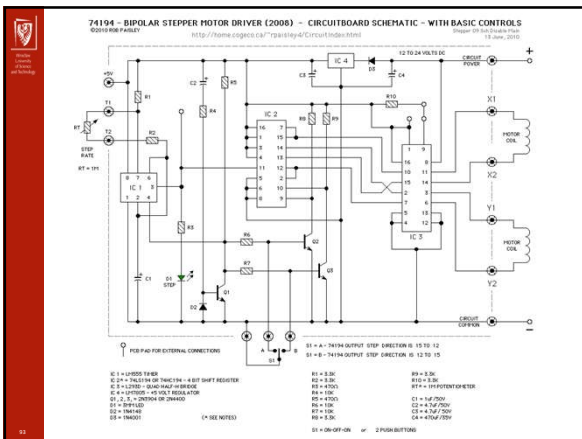

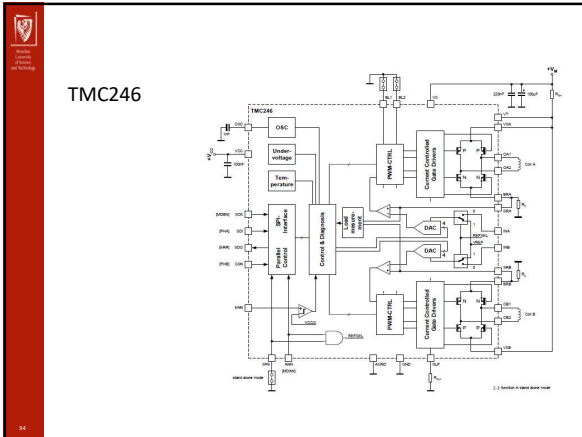

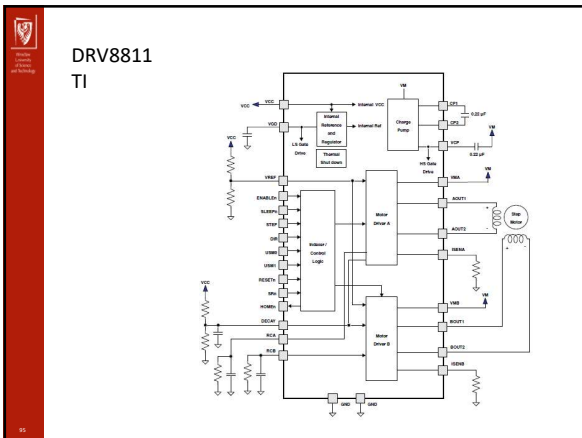

Type	Advantages	Disadvantages	Typical Application	Typical Drive
AC Induction (Shaded Pole) (31)	Least expensive Long life lowpower	Rotation slips from frequency Low starting torque	Fans	difficult to control
AC Induction (Squirrel-cage capacitor) (34)	Medium power high starting torque	Rotation slips from frequency	Appliances Stationary Power Tools	Uni/Poly-phase AC
AC Squirrel-cage (40)	High power	Rotation slips from frequency	Industry/ hp machines	Inverter frequency Vector control (if recurrent)
Brushed DC (41)	Low initial cost Simple speed control	Maintenance (brushes) Medium lifespan	Treadmill exercisers Automotive motors (seats, blowers, windows)	Direct DC or PWM
BL DC (49)	Long lifespan low maintenance High efficiency	High initial cost Requires a controller	Hard drives CD/DVD players electric vehicles	DC switching, Pwm
Universal motor (63)	High starting torque, compact, high speed	Maintenance (brushes) Medium lifespan	Portable tools Grid powered	Uni-phase AC or Direct DC
Stepper DC 1ph/2ph (66)	Precision positioning High holding torque	High initial cost Requires a controller	Positioning in printers and floppy drives	DC switching
AC Synchronous (82)	Rotation in-sync with frequency no slip long-life	More expensive	Industrial motors Clocks Audio turntables tape drives	Uni/Poly-phase AC

17

Department of Electrical and Electronic Engineering

Synchronous motor

Lessons in Electric Circuits, Volume II – AC By Tony R. Kuphaldt, Sixth Edition, last update July 26, 2007

18


Department of Electrical and Electronic Engineering

Multipole synchronous motor

The induction or self starting and the bar magnet as synchronous motor


19

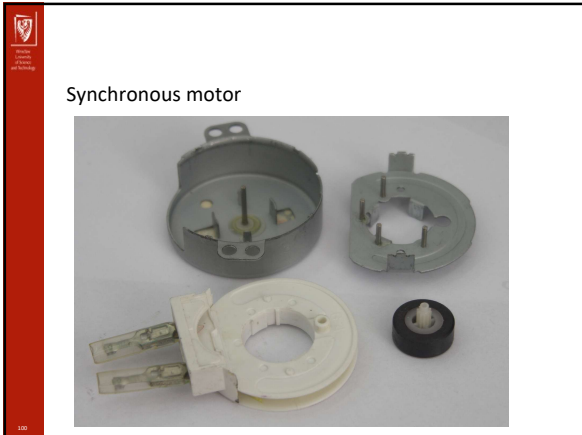
Department of Electrical and Electronic Engineering








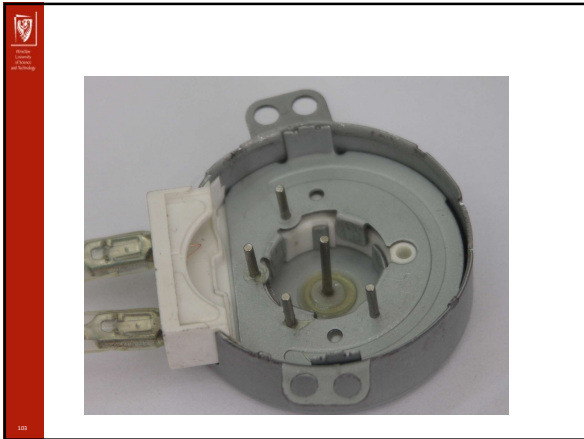

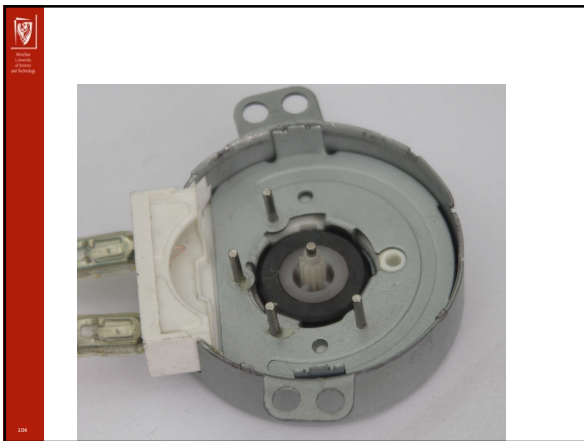

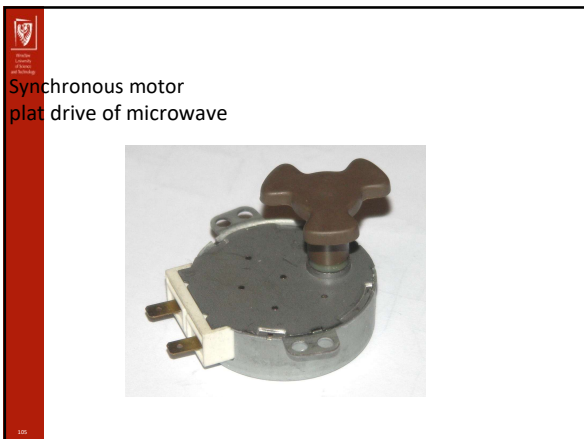







 VCM
 Voice Coil Motor



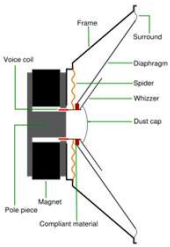 VCM motors (actuators)
 (hard disk head, laser positioner in CD)





 Linear motor

