



Power suppliers:

- rectifiers,
- Power Factor
- voltage multipliers





Transformer parameters

- Power (single phase up to 3kW)
- Nominal voltage 230V +10% -10%
- Frequency 50Hz
- Transformer parameters:
 - Turn ratio (secondary voltage and current)
 - Idle current
 - Isolation breakdown voltage
 - Dimensions, weight
 - temperature





Types of transformers
-most popular

- Cores: EI type (shell), wound core (strip construction) , toroidal (wound ring-shape core, strip construction)
- Core Materials
 - Silicon steel,
 - permalloy







transformersr
[voltage / turn]


$$\frac{U}{z} = \sqrt{2} \pi f B_{\max} S$$


Transformers - power vs. type


S[cm²]@P[W]	core	B _{max} [T]
$S \approx 1,25 \cdot \sqrt{P_1}$	Hot rolled steel sheet, EI core	1T
$S \approx 1,1 \cdot \sqrt{P_1}$	Cold rolled steel sheet EI core	1.1T
$S \approx \sqrt{P_1}$	Cold rolled steel sheet wound core	1.5T
$S \approx 0.8 \cdot \sqrt{P_1}$	Cold rolled steel sheet Toroid	1.6T

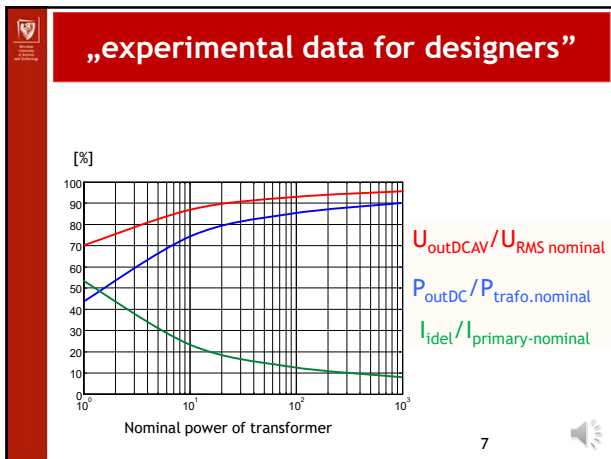


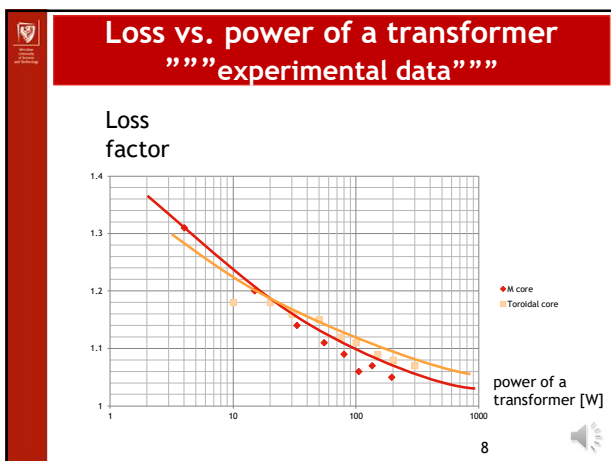


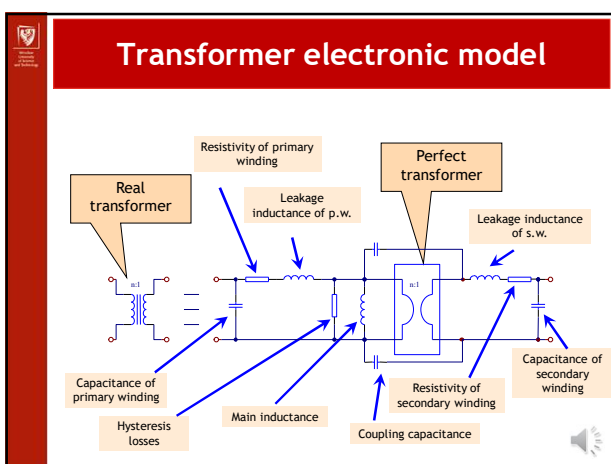


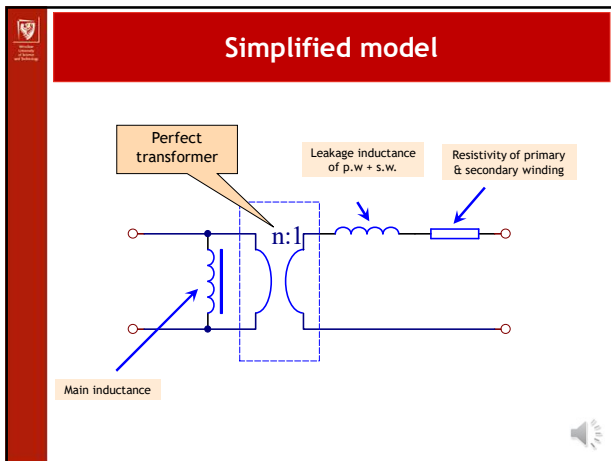


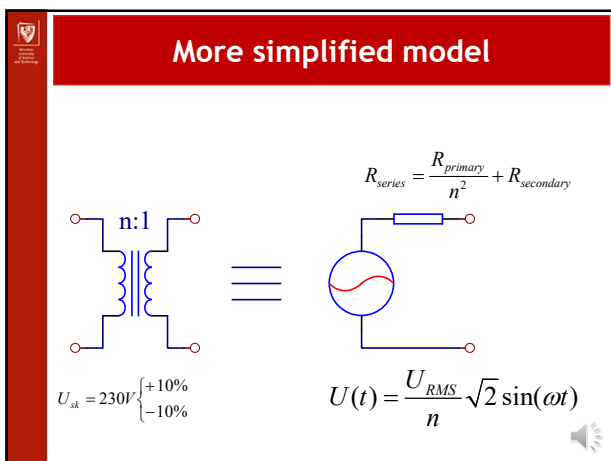


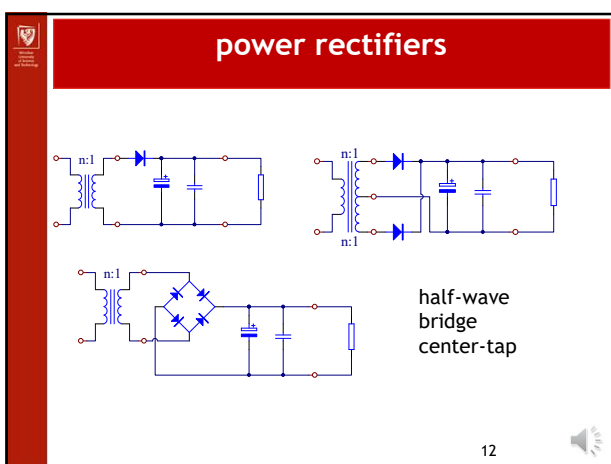


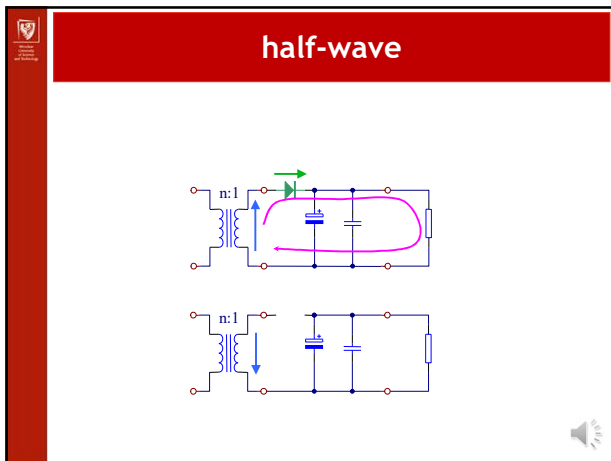


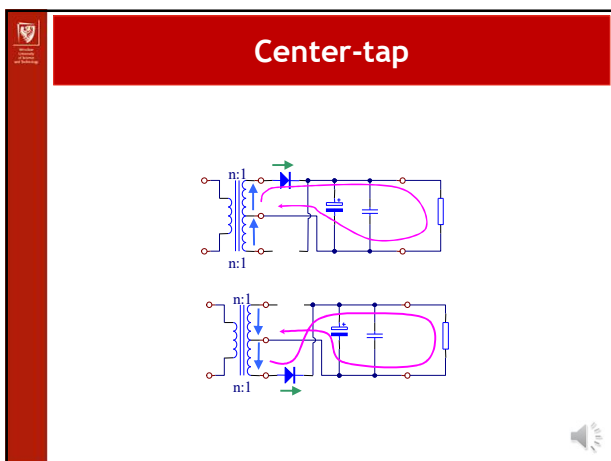

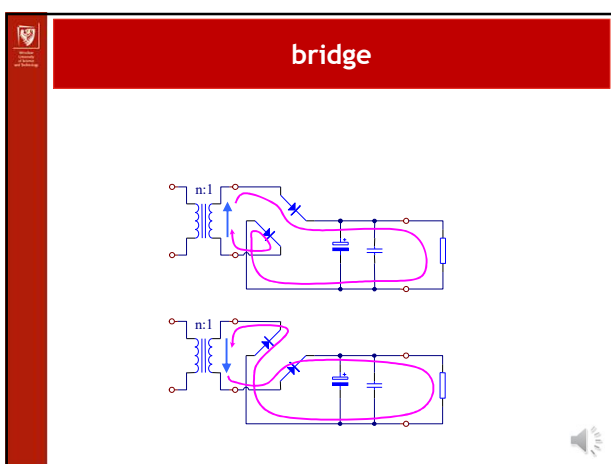

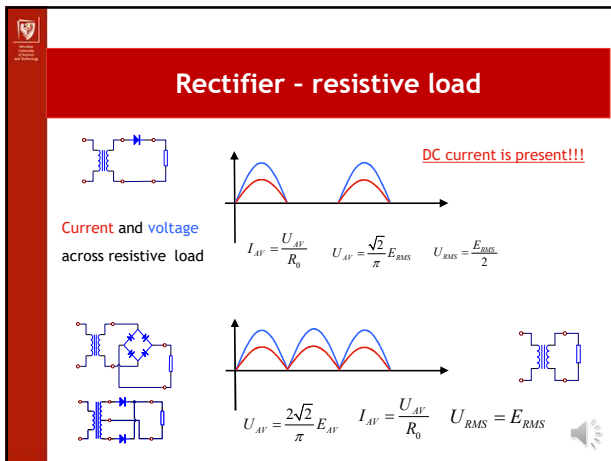

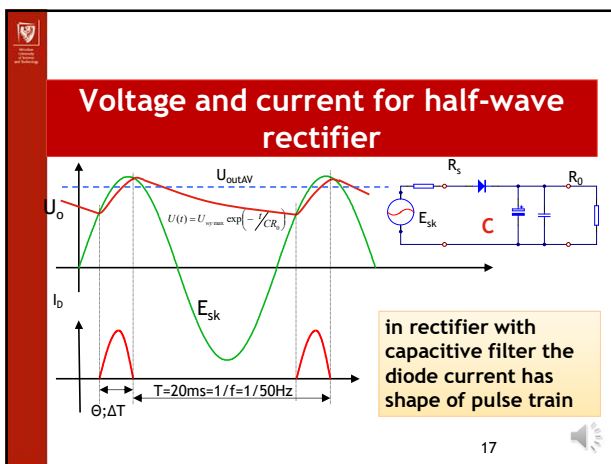

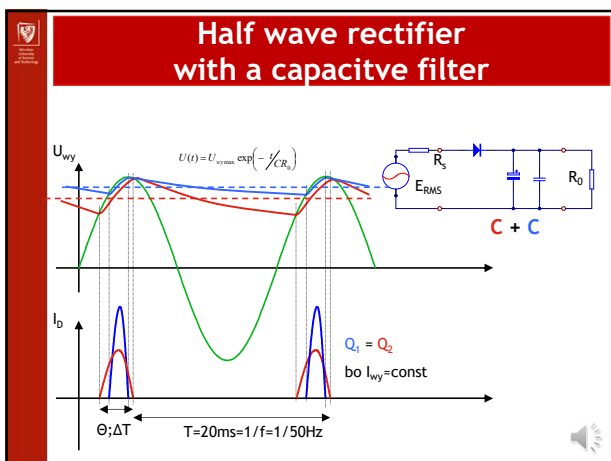

Basic relations


Maximum idle voltage:

$$U_{\max} \approx \sqrt{2}E_{\text{RMS}} - U_F \approx \sqrt{2}E_{\text{RMS}}$$

ripples:

$$U_{\text{rip.pp}} \approx \frac{Q}{C} = \left(\frac{U_{\max}}{R_0} \right) \frac{T}{C} = \frac{U_{\max}}{fR_0C} \approx \frac{I_{AV}}{fC}$$

How to figure out this relationship!

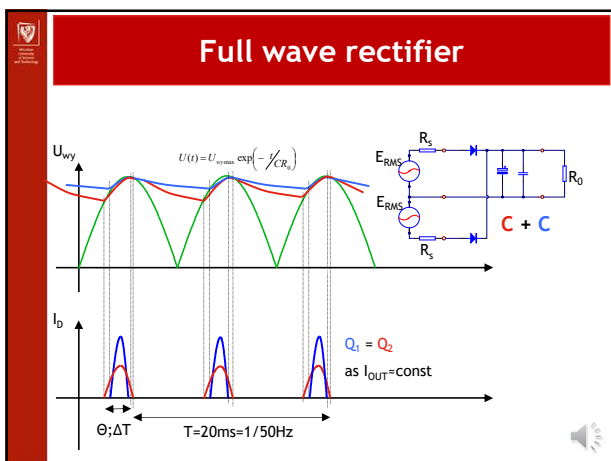

Basic relations

Maximum idle voltage:

$$U_{\max} \approx \sqrt{2}E_{\text{RMS}} - U_F$$


bridge:

$$U_{\max} \approx \sqrt{2}E_{\text{RMS}} - 2U_F$$

ripples:

$$U_{\text{rip.pp}} \approx \frac{Q}{C} = \frac{I_{AV} T/2}{C} = \frac{I_{AV}}{2fC}$$

How to figure out this relationship!

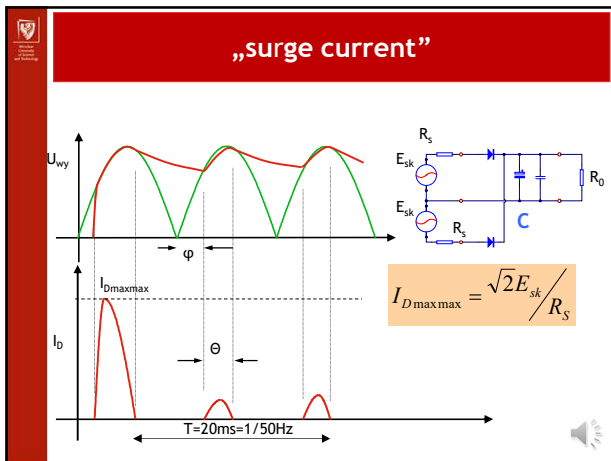

half-wave rectifier
for $U_{rpp}/U_{outAV} < 10\%$

No-load voltage	$U_{outMax} = \sqrt{2}E_{RMS} - U_F$
On-load voltage ($C=\infty$)	$U_{outAV} = U_{outMax} \left(1 - \sqrt{\frac{R_s}{R_L}}\right)$
Peak revers voltage	$U_{Dmax} = 2\sqrt{2}E_{sk}$
Mean diode current	$I_{Dmean} = I_{outAV}$
Repetitive diode current	$I_{Dmax} = U_{outAV} / \sqrt{R_s R_L}$
Ripple voltage (peak to peak)	$U_{rpp} = \frac{I_{outAV}}{fC} \left(1 - \sqrt{\frac{R_s}{R_L}}\right)$
Minimum output voltage	$U_{outMin} = U_{outAV} - \frac{2}{3}U_{rpp}$

23

bridge rectifier
for $U_{rpp}/U_{outAV} < 10\%$

No-load voltage	$U_{outMax} = \sqrt{2}E_{RMS} - 2U_F$
On-load voltage ($C=\infty$)	$U_{outAV} = U_{outMax} \left(1 - \sqrt{\frac{R_s}{2R_L}}\right)$
Peak revers voltage	$U_{Dmax} = \sqrt{2}E_{sk}$
Mean diode current	$I_{Dmean} = \frac{1}{2} I_{outAV}$
Repetitive diode current	$I_{Dmax} = U_{outAV} / \sqrt{2R_s R_L}$
Ripple voltage (peak to peak)	$U_{rpp} = \frac{I_{outAV}}{2fC} \left(1 - \sqrt{\frac{R_s}{2R_L}}\right)$
Minimum output voltage	$U_{outMin} = U_{outAV} - \frac{2}{3}U_{rpp}$

24

center-tap rectifier


for $U_{rip}/U_{outAV} < 10\%$

No-load voltage	$U_{outMax} = \sqrt{2}E_{RMS} - U_F$
On-load voltage ($C=\infty$)	$U_{outAV} = U_{outMax} \left(1 - \sqrt{\frac{R_s}{2R_L}}\right)$
Peak revers voltage	$U_{Dmax} = 2\sqrt{2}E_{ak}$
Mean diode current	$I_{Dmean} = \frac{1}{2} I_{outAV}$
Repetitive diode current	$I_{Dmax} = U_{outAV} / \sqrt{2R_s R_L}$
Pipple voltage (peak to peak)	$U_{rip} = \frac{I_{outAV}}{2fC} \left(1 - \sqrt{\frac{R_s}{2R_L}}\right)$
Minimum output voltage	$U_{outMin} = U_{outAV} - \frac{2}{3} U_{rip}$

25

Main parameters

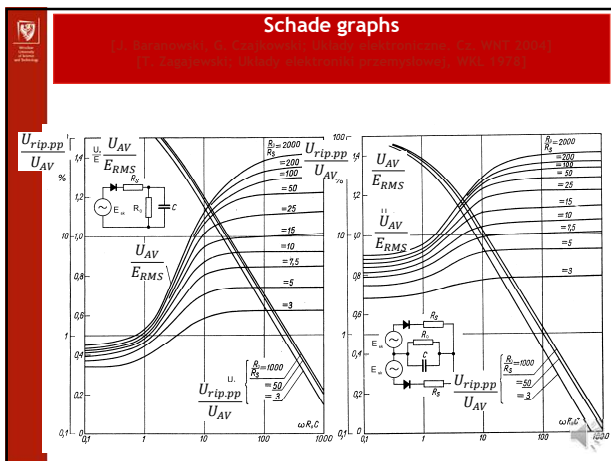- Assumed:
 - $E_{RMS} = U_{RMS} / n$ (turn ratio)
 - R_s - series resistivity
 - U_F - forward diode voltage
- calculated
 - U_{OUTRMS} ; U_{OUTAV} ; U_{OUTMAX} ; U_{OUTMIN} ; U_{rip}
 - I_{DAV} ; I_{DRMS} ; I_{DMAX} ; I_{OUTAV}
 - Θ ; ΔT - flow angle; conducting time
 - $k_t = U_{rip,pp} / U_{OUTAV}$ - ripples coefficient
 - $\eta_u = U_{OUTAV} / E_{RMS}$ - voltage efficiency



Crest & Wave Form factors

$$CF = I_{MAX} / I_{RMS}$$


Crest Factor -
For sin = $1,41 = \sqrt{2}$

$$FF = I_{RMS} / |I|_{AV}$$

Wave Form Factor -
For sin = $1,11 = \pi/2\sqrt{2}$




Form Factor

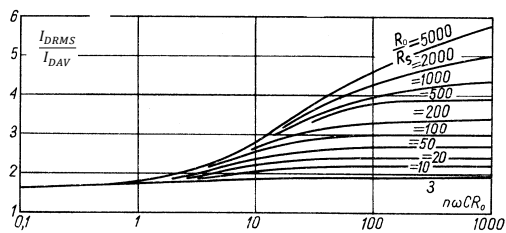

n - numbers of phases (1, 2, 3, 6)




$$I_{DMAX} / I_{DAV} = CF * FF$$

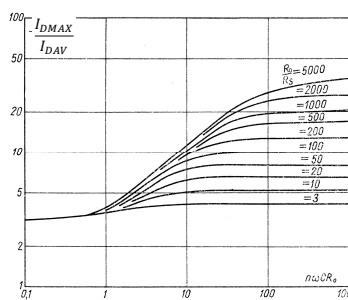

n - liczba faz
(1, 2, 3, 6)



Flow angle θ & start flow angle φ

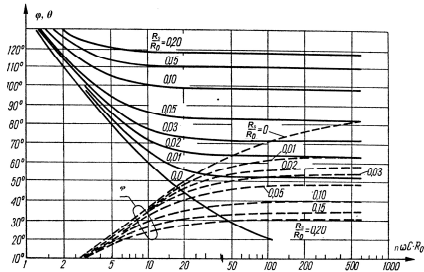


For
 $\omega R_0 C \gg 1$ i $R_0 \gg R_s$

When C increases


- Ripples fall down $\sim 1/nfCR_0$!!!!
- Flow angle decrease (diode conducting time)
- peak current increase
- RMS diode & transformer currents increase (heating up)

RMS of pulse

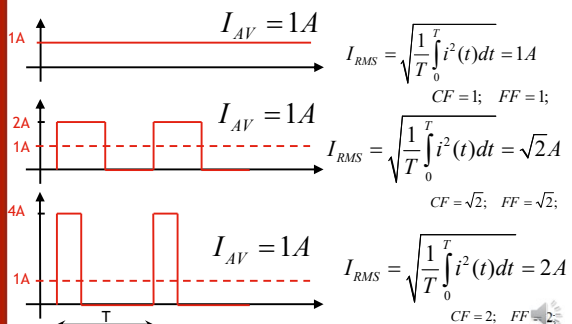

Power dissipated in diode
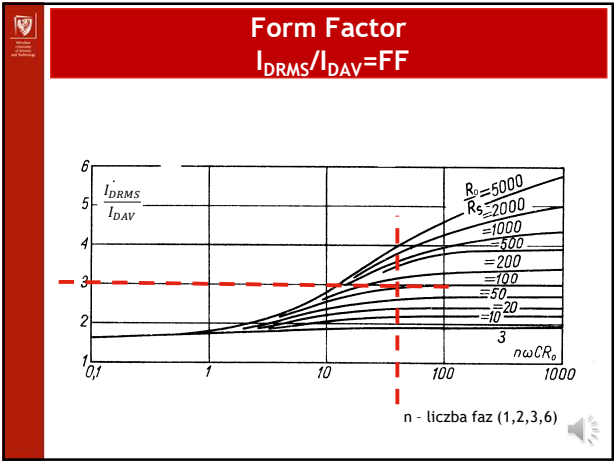
$$P_{Dreal} = \frac{1}{T} \int_0^T u_D(t) i_D(t) dt + \frac{1}{T} \int_0^T i_D^2(t) R_{D,series} dt =$$
$$= U_D I_{DAV} + I_{DRMS}^2 R_{D,series}$$
$$P_{Dreal} = 0.7V \cdot 1A + (3A)^2 \cdot 0.1\Omega =$$
$$= 0.7W + 0.9W$$



Rectifier comparison

	Half-wave	Center-tap	Bridge
C To reach proper U_{ip}	$C \approx \frac{U_{OUT,max}}{U_{rip,pp}} \cdot \frac{1}{fR_0}$	$\frac{1}{2}(..)$	$\frac{1}{2}(..)$
Maximum and RMS diode current)	high	meadium	meadium
Diode revers voltage	$2E_{max}$	$1(..)$	$\frac{1}{2}(..)$
Current Harmonics	All Including DC ???	odd	odd


Crest Factor & Waveform Factor


$$CF = \frac{I_{MAX}}{I_{RMS}}$$

Crest Factor - współczynnik szczytu
For sin wave = $1,41 = \sqrt{2}$

$$FF = \frac{I_{RMS}}{|I|_{AV}}$$

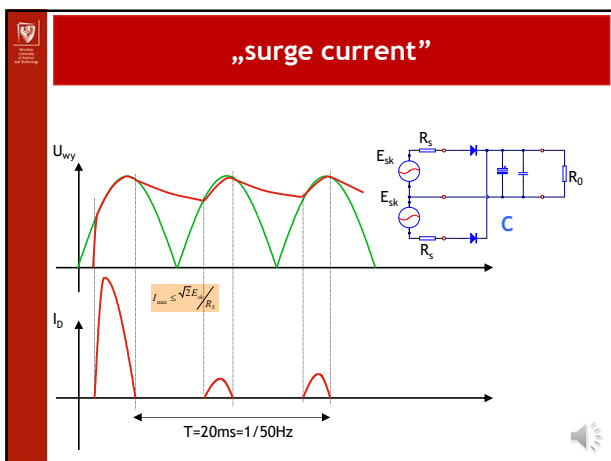Waveform Factor - współczynnik kształtu
For sine wave = $1,11 = \pi/\sqrt{2}$



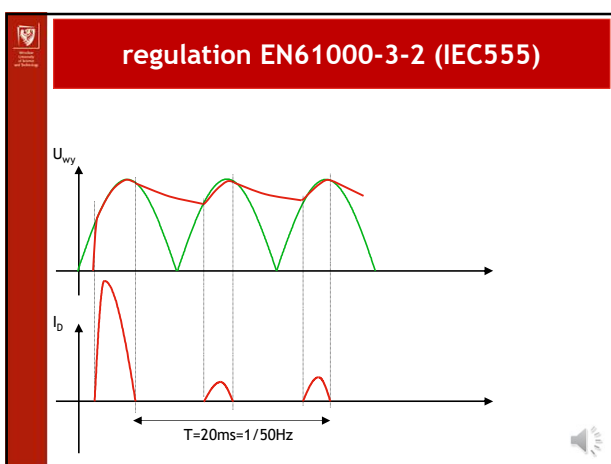




Example of parameters for a rectifier diode

MAXIMUM RATINGS (T _A = 25 °C unless otherwise noted)									
PARAMETER	SYMBOL	1N4001	1N4002	1N4003	1N4004	1N4005	1N4007	UNIT	
Maximum repetitive peak reverse voltage	V _{RRM}	50	100	200	400	600	800	1000	V
Maximum RMS voltage	V _{RMS}	35	70	140	280	420	560	700	V
Maximum DC blocking voltage	V _{OC}	50	100	200	400	600	800	1000	V
Maximum average forward rectified current 0.375" (9.5 mm) lead length at T _A = 75 °C	I _{F(AV)}	1.0						A	
Peak forward surge current 8.3 ms single half sine-wave superimposed on rated load	I _{FSM}	30						A	
Non-repetitive peak forward surge current square waveform T _A = 25 °C (Fig. 3)	t _p = 1 ms	45						A	
	t _p = 2 ms	35							
	t _p = 5 ms	30							
Maximum full load reverse current, full cycle average 0.375" (9.5 mm) lead length T _A = 75 °C	I _{RV}	30						µA	
Rating for fusing (t < 8.3 ms)	Pt (t)	3.7						A ² s	
Operating junction and storage temperature range	T _J , T _{STG}	-50 to +150						°C	

Note
(1) For device using on bridge rectifier application



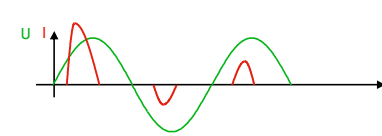Supply current distortion - IEC555 EN 61000-3-2




- harmonics (up to 40 harmonic)
- current fluctuations of load
- surge current ???





Input Characteristics of a Typical Switched-Mode Power Supply without PFC


Top: Input Voltage Bottom: Input Current

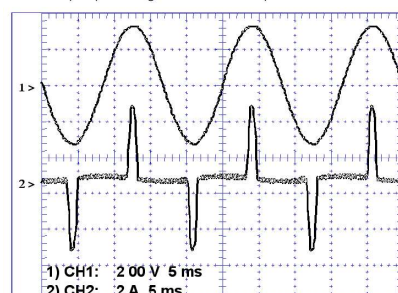



1) CH1: 200 V 5 ms
2) CH2: 2 A 5 ms

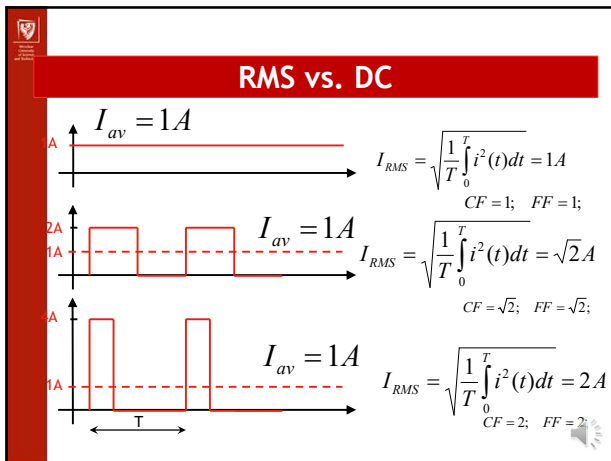


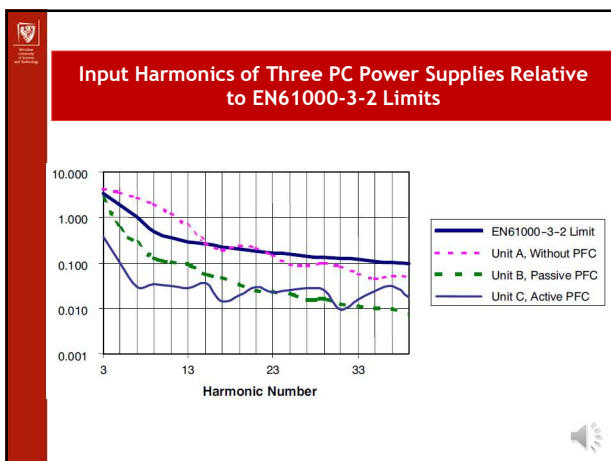

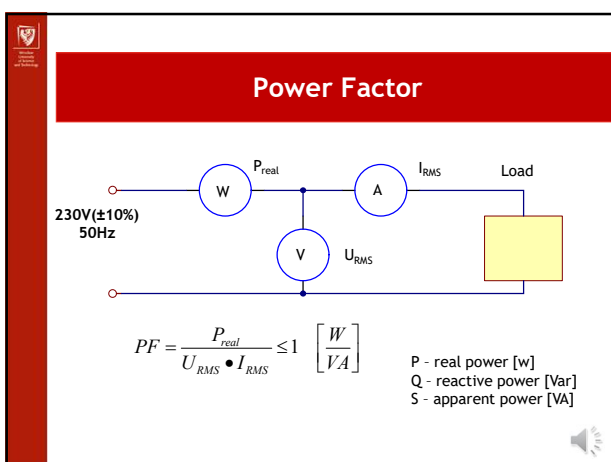

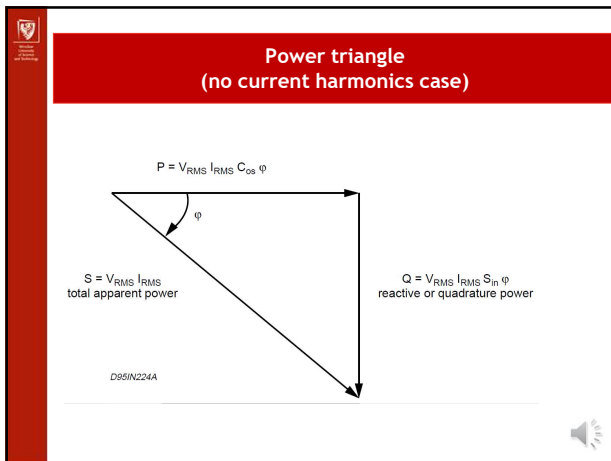

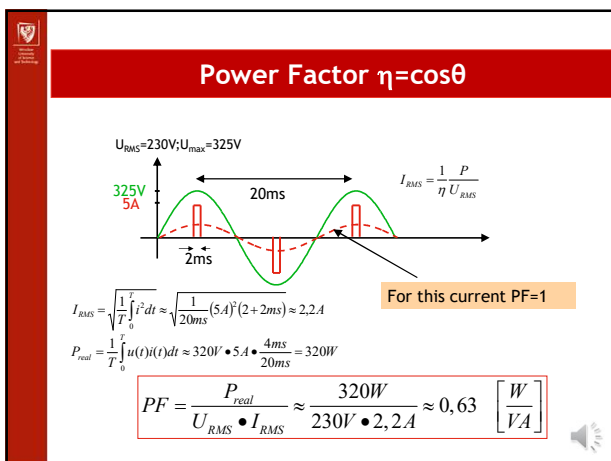

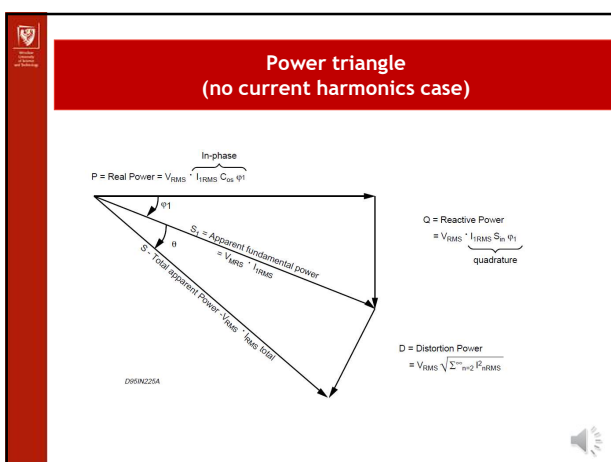

Total P.F. = $\eta = \cos \varphi_1 \cos \theta$

φ_1 is the "conventional" displacement angle (phase lag) between the in-phase fundamental I and V
 θ is the distortion angle linked to the harmonic content of the current.

Both of reactive (Q) and distortion (D) powers produce extra RMS currents, giving extra losses so that then the mains supply network efficiency is decreased.

Improving P.F. means to improve both of factors i.e.:

$\varphi_1 \rightarrow 0 \quad \cos \varphi_1 \rightarrow 1 = \text{reduce phase lag between I and U}$
 $\theta \rightarrow 0 \quad \cos \theta \rightarrow 1 = \text{reduce harmonic content of I}$

THD vs. PF ($\cos \varphi_1 = 1$)


$$THD(\%) = 100 * \sqrt{\frac{1}{Kd^2} - 1}$$


$$Kd = \frac{1}{\sqrt{1 + \left(\frac{THD(\%)}{100}\right)^2}}$$


$$PF = \frac{1}{\sqrt{1 + \left(\frac{THD(\%)}{100}\right)^2}}$$

THD vs. P.F.

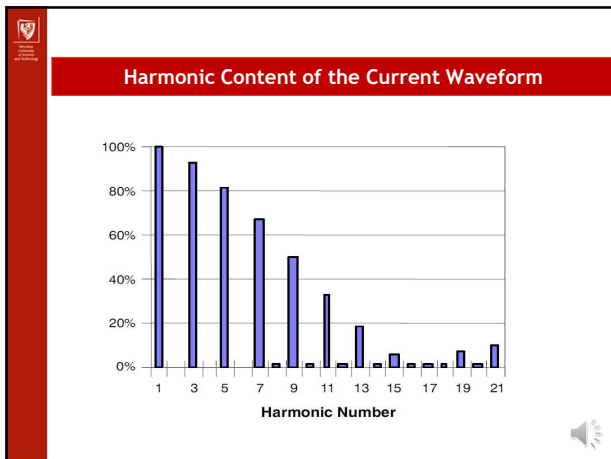
$$PF = \frac{\cos(\varphi_1)}{\sqrt{1 + \left(\frac{THD(\%)}{100}\right)^2}} = \cos(\theta) \cdot \cos(\varphi_1)$$



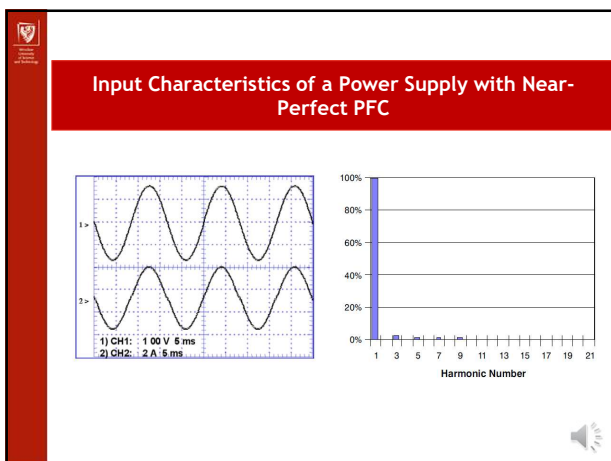

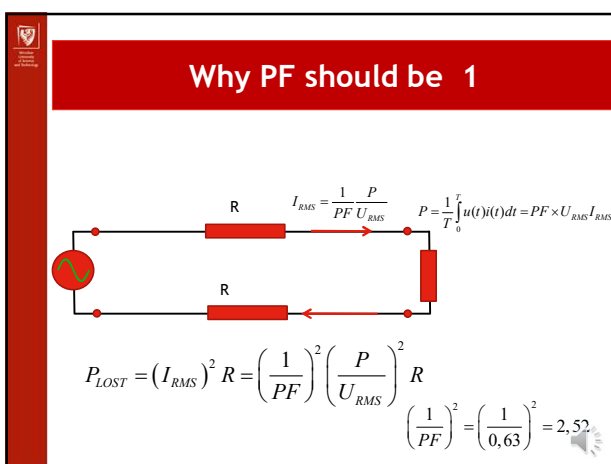

LC filter

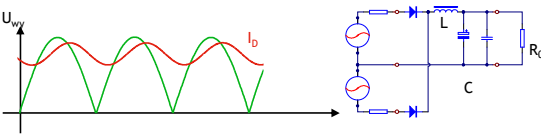

Results:

- Smaller ripples
- Smaller THD
- Higher cost
- Choke must be „big“


$$L > L_{\text{system}} = \frac{R_0}{3\omega}$$

For $L > L_{\text{cr}}$ I_L not drop to 0 (continues mode)


Input Characteristics of PC Power Supplies with Different PFC Types (None, Passive, and Active)


Waveforms:

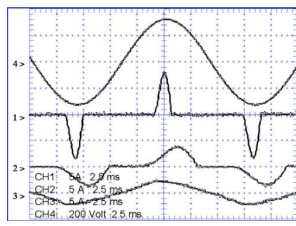
1. Input current with no PFC
2. Input current with passive PFC
3. Input current with active PFC
4. Input voltage





Passive PFC in a 250W PC Power Supply

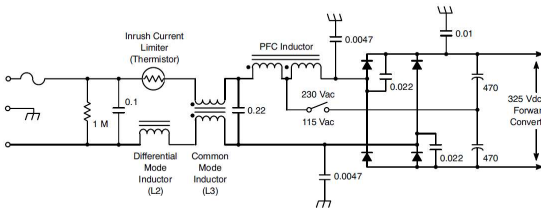


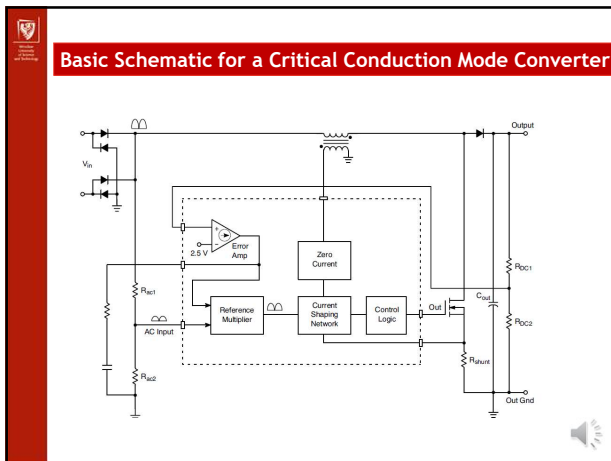


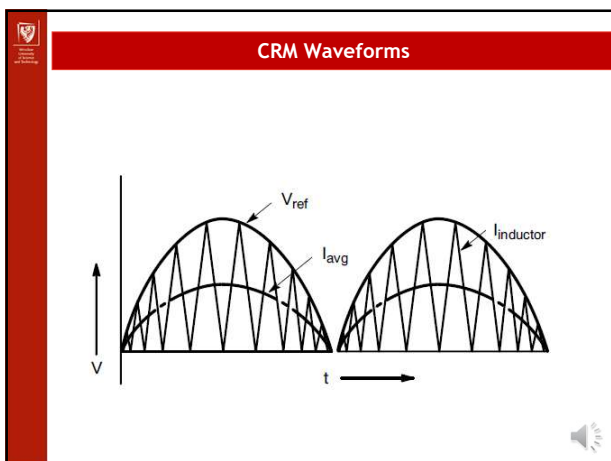


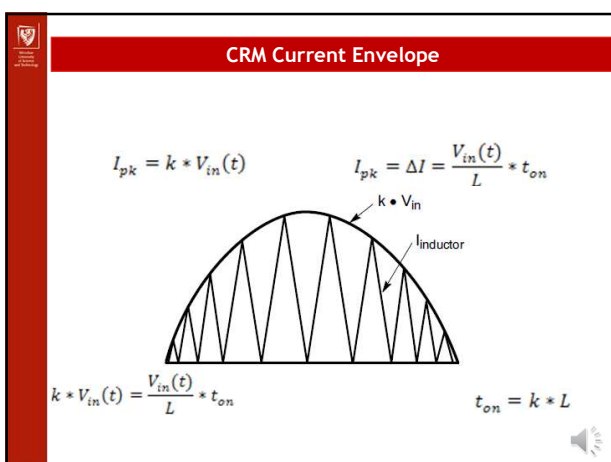


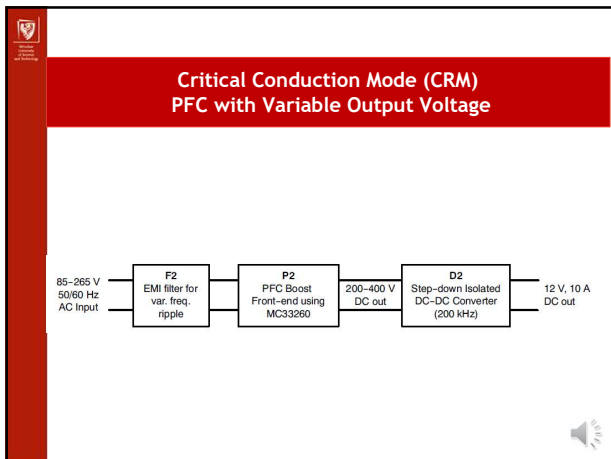


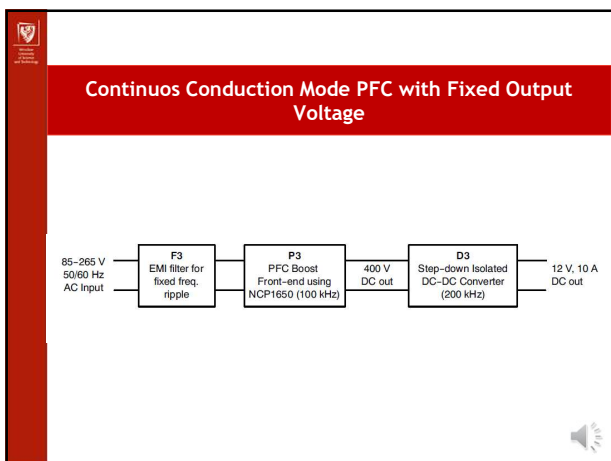


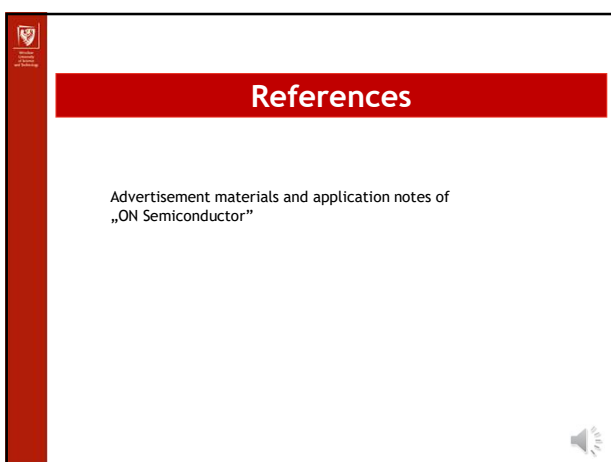


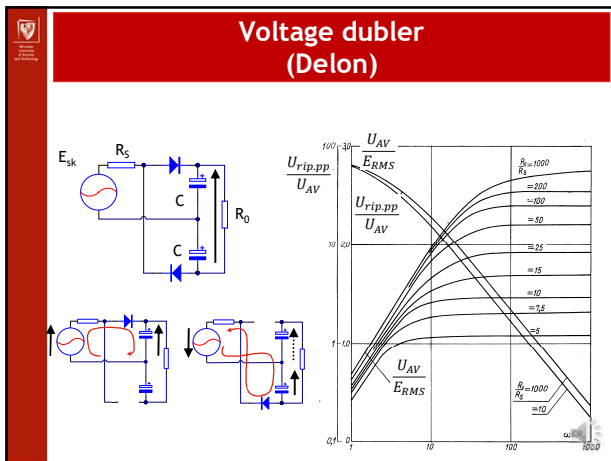

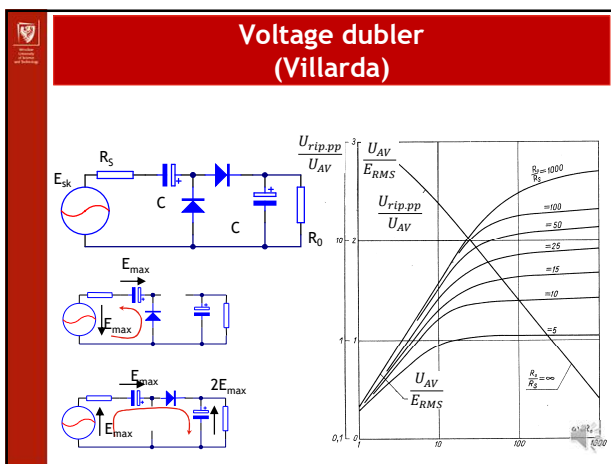

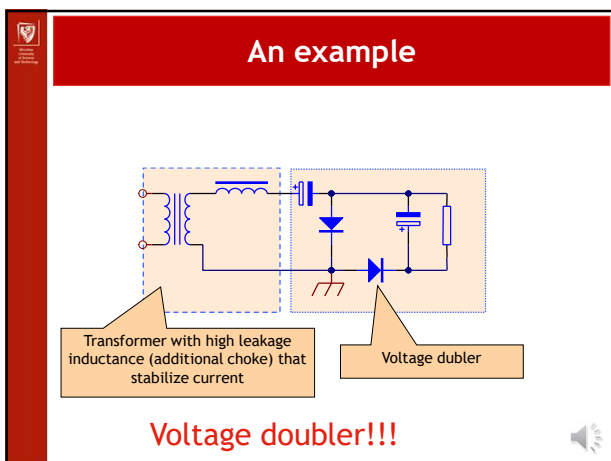

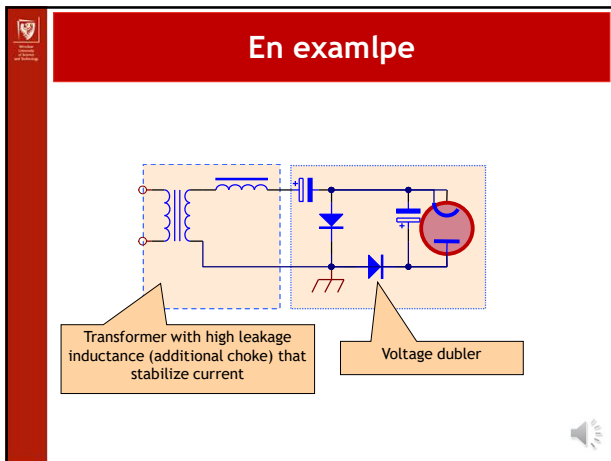


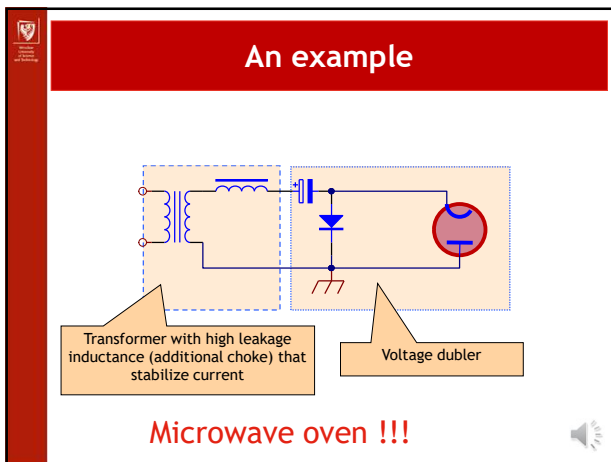







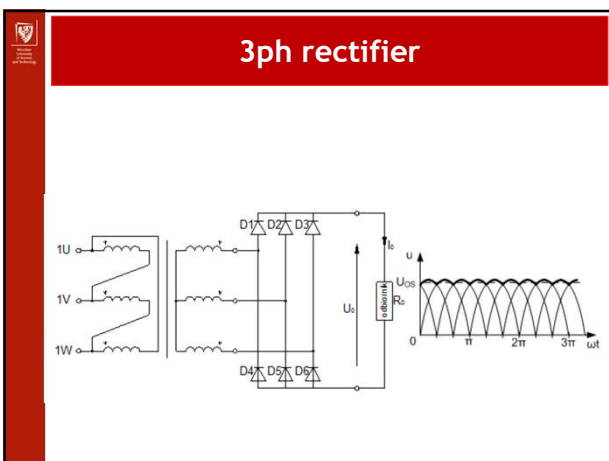




Technik und Design

3ph rectifier - hv


- Dides must be „matched” !

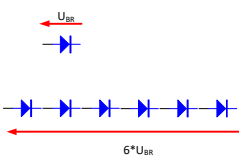



Technik und Design

3ph rectifier hv practice

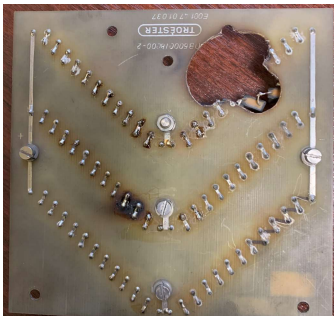



Technik und Design



Voltage multipliers

$$C \geq \frac{2n(n+2)}{fR_0}$$

$$U_{wy, \Delta r} = n\sqrt{2}E_{sk} - U_i$$

$$U_i = \frac{I_{max}}{fC} \left(\frac{2}{3}n^3 + \frac{1}{2}n^2 + \frac{1}{6}n \right)$$

$$U_i = \frac{I_{max}}{fC} \left(\frac{1}{6}n^3 + \frac{1}{4}n^2 + \frac{1}{12}n \right)$$

summary

- Transformer (parameters, types, equivalent schematic diagram)
- Types of rectifiers
- Resistive load rectifier (voltage, current waveforms)
- Rectifier with capacitive filter (voltage, current waveforms)
- Power Factor (definition, way of correction)

Test questions

- Draw a simplified diagram of a transformer and describe its individual components.
- Draw a schematic diagram of a rectifier (half-wave, full-wave, bridge).
- Draw the voltage and current waveforms in a rectifier (3 types).
- What is the definition of power factor?
- Estimate PF using a simple example.
