


Wrocław  
University  
of Science  
and Technology



hr



IEP

# Relays

---

---

---


---

---

---

---

---



Wrocław  
University  
of Science  
and Technology

## References

- S. L Herman, Industrial motor control, Clifton Park, 2014
- T. R. Kuphaldt, Lessons In Electric Circuits, Volume II – AC, 6th Edition, 2007 (<http://www.faqsg.org/docs/electric/AC/index.html>)
- J. Przepiorkowski, Silniki elektryczne w praktyce elektronika, BTC

---

---

---


---

---

---

---

---



Wrocław  
University  
of Science  
and Technology

## Outline

- relays
  - mechanical
  - electronic relay (SSR)
- Electric motors

---

---

---


---

---

---

---

---

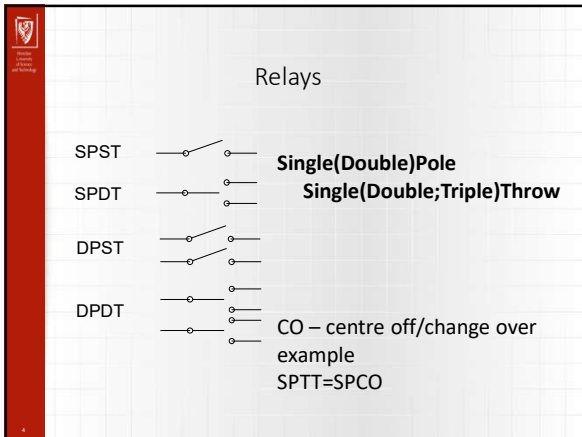


---

---

---


---

---

---

---

---

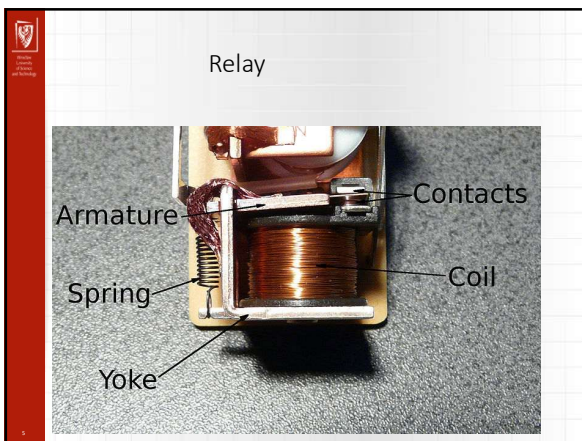


---

---

---

---

---

---

---

---




---

---

---


---

---

---

---

---

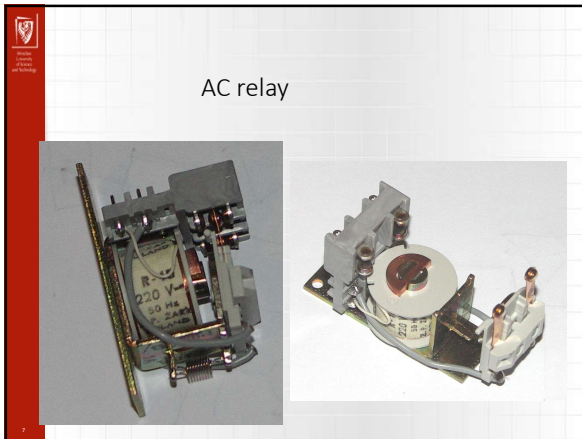

---

---


---

---

---

---

---

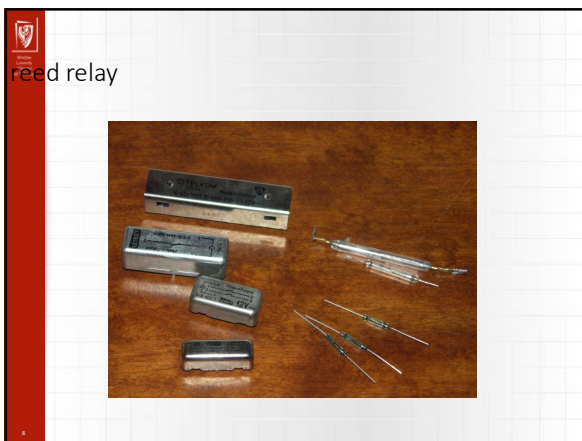

---

---


---

---

---

---

---

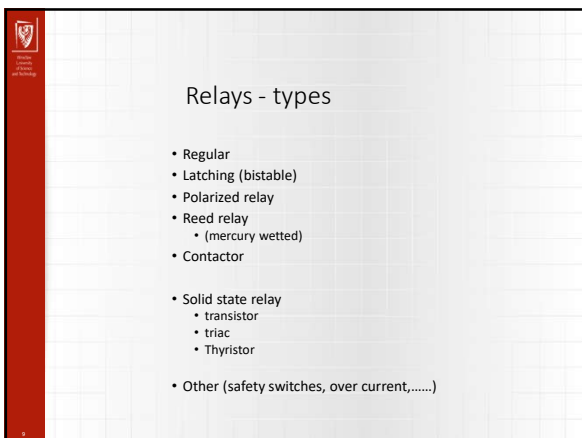

---

---


---

---



---

---

---



### Relay - diagram symbol

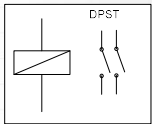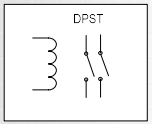---

---

---


---

---

---

---

---



### Ohm's low for inductance

$$U_L = L \frac{dI}{dt}$$

$$U_L = X_L I_L = \frac{1}{i\omega C} I_L$$

TIPS:

- higher voltage applied – faster changes of current
- fast changes in current – higher voltage induced
- when current change „slope direction“ – voltage change polarity:
- positive voltage applied – current increased
- current decreased – negative voltage induced

---

---

---


---

---



---

---

---



### Switching on and off an inductor

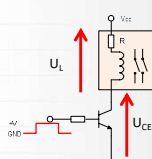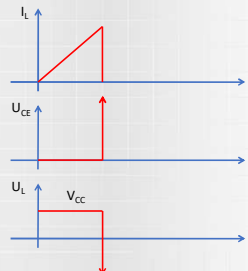---

---

---

---

---

---

---

---

Relay – spark discharge

High voltage can destroy transistor and relay and can be very dangerous !!!!

---

---

---

---

---

---

---

---

Switching on and off an inductor

protection diode;  
flyback diode;  
clamp diode;

---

---

---

---

---

---

---

---

Switching on and off an inductor

---

---

---


---

---

---

---

---

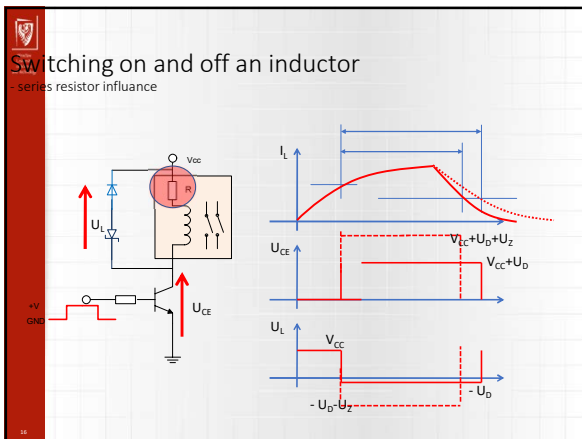


---

---

---


---

---

---

---

---

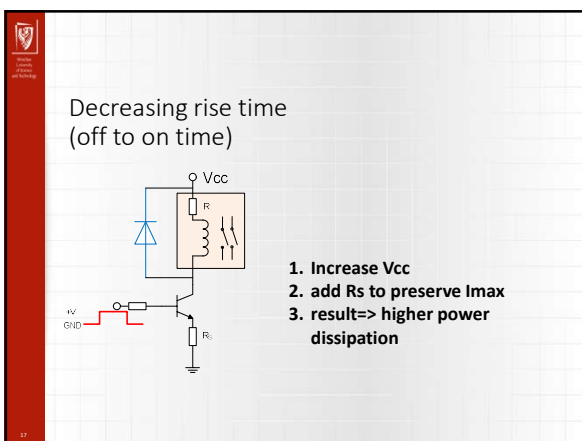


---

---

---


---

---

---

---

---

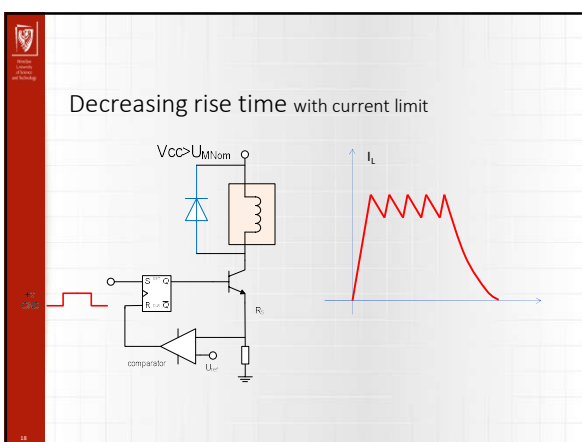


---

---

---

---

---

---

---

---

---

---

---

---

---

---

---

---

---

---

---

---

---

---

---

---

---

---

---


---

---

---

---

---

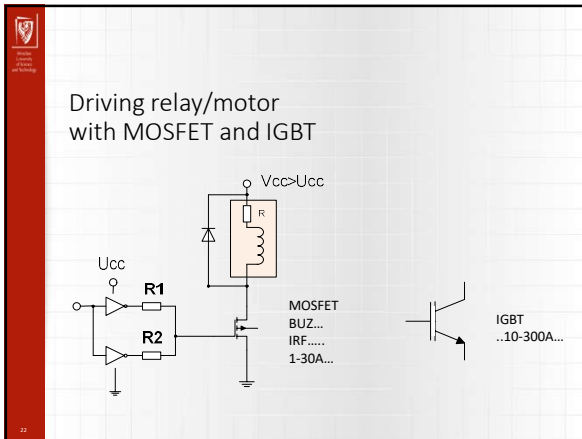


---

---

---


---

---

---

---

---

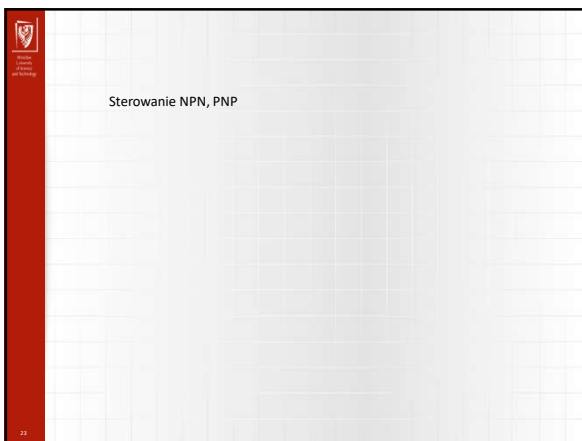


---

---

---


---

---

---

---

---

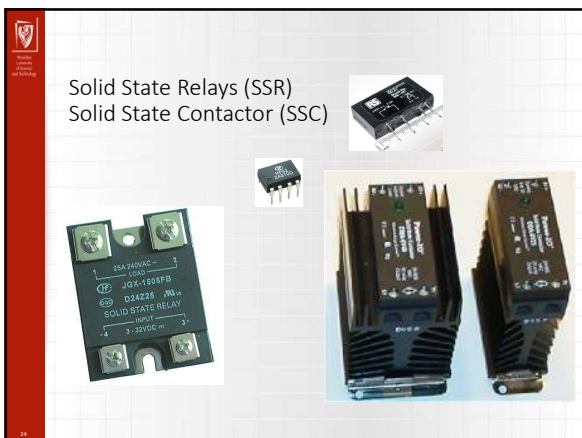


---

---

---

---

---

---

---

---



### SSR of different types

can be used for AC driven mechanical relays

- Usually small power but can drive any type of load (including induction)
- AC and DC applications

- Be careful with inductive load – the load can be not switched off !!!
- AC applications only

---

---

---

---

---

---

---

---

### High power SSR

---

---

---

---

---

---

---

---

### BT136 data

Absolute maximum ratings

Parameter	Symbol	Value	Unit	Test condition
peak repetitive off-state voltage	$V_{DRM}, V_{RRM}$	600	V	
on-state RMS current	$I_T(RMS)$	4	A	$T_L \leq 66^\circ C$
NON repetitive surge peak on-state current	$I_{TSM}$	25	A	$T_p = 20ms, T_J = 25^\circ C$
critical rate of rise on-state current	$di/dt (Q_{13})$	50	A/ $\mu s$	$I_{HM} = 20A, T_G = 0.2A$
peak gate current	$I_{GM}$	2	A	
average gate power dissipation	$P_G(AV)$	0.5	W	
storage temperature range	$T_{stg}$	-40 to +150	$^\circ C$	
operating junction temperature range	$T_J$	125	$^\circ C$	

Electrical characteristics (  $T_J = 25^\circ C$  ) unless otherwise specified

Parameter	Symbol	Value	Unit	Test condition
gate trigger current	$I_{GT}$	$\leq 10$	mA	$T_2 + G + V_D = 12V, I_H = 0.1A$
		$\leq 10$	mA	$T_2 + G - V_D = 12V, I_H = 0.1A$
		$\leq 10$	mA	$T_2 - G - V_D = 12V, I_H = 0.1A$
		$\leq 25$	mA	$T_2 - G + V_D = 12V, I_H = 0.1A$
gate trigger voltage	$V_{GT}$	$\leq 1.5$	V	$V_D = 12V, I_H = 0.1A$
hold current	$I_H$	$\leq 30$	mA	$V_D = 12V, I_H = 0.1A$
critical rate of rise off-state voltage	$dv/dt$	$\geq 50$	V/ $\mu s$	$V_D = 67\% V_{DRM}$
on-state voltage	$V_{TM}$	$\leq 1.7$	V	$I_H = 5A$
off-state leakage current	$I_{ORM}$	$\leq 0.5$	mA	$V_D = V_{DRM}, T_J = 125^\circ C$
thermal resistance	$R_{th(j-a)}$	60	$^\circ C/W$	
	$R_{th(j-c)}$	$\leq 3.7$	$^\circ C/W$	

---

---

---


---

---

---

---

---

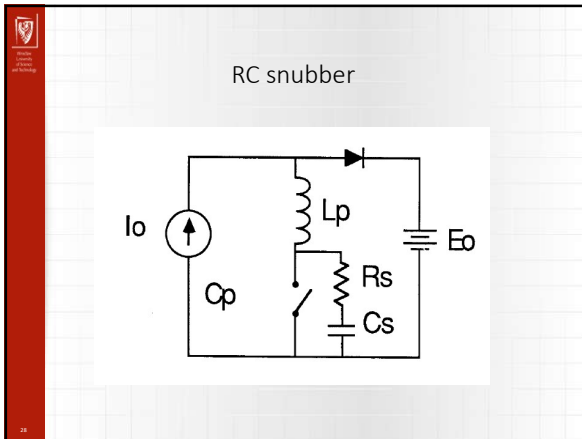


---

---

---


---

---

---

---

---

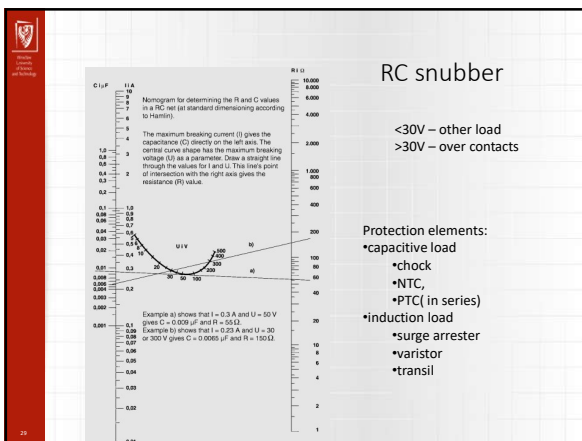


---

---

---

---

---

---

---

---

**Motors**

---

---

---


---

---

---

---

---

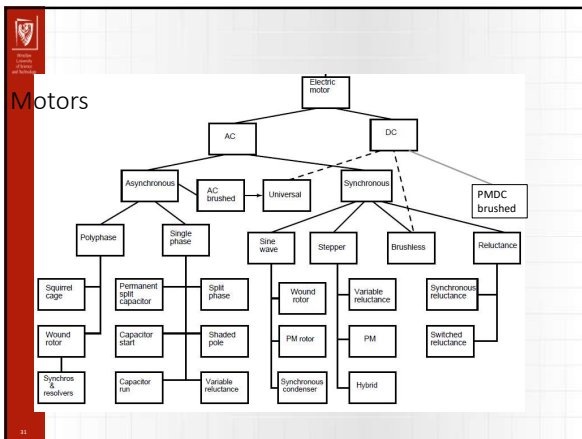


---

---

---

---

---

---

---

---

- Electric motors**
- AC motors
    - squirrel cage (3 phase, 1 phase -shade pole, capacitor, split phase)
    - synchronous
  - DC motors
    - Permanent magnet DC
    - Universal motors
      - series
      - shunt
      - compound wound
  - BrushLess DC (BLDC)
    - 2 phase
    - 3 phase
  - Stepper motors
    - reluctance
    - permanent magnet
    - hybrid
  - Linear (Voice Coil Motor – VCM)

---

---

---

---

---

---

---

---

Type	Advantages	Disadvantages	Typical Application	Typical Drive
AC Induction (Shaded Pole)	Least expensive Long life Low power	Rotation slips from frequency Low starting torque	Fans	difficult to control
AC Induction (split-phase capacitor)	Medium power high starting torque	Rotation slips from frequency	Appliances Stationary Power Tools	UniPoly-phase AC
AC Squirrel cage 3ph	High power	Rotation slips from frequency	Industry/ hp machines	Inverter frequency Vector control (trickier)
Brushed DC	Low initial cost Simple speed control	Maintenance (brushes) Medium lifespan	Treadmill exercisers automotive motors (seats, blowers, windows)	Direct DC or PWM
BLDC	Long lifespan low maintenance High efficiency	High initial cost Requires a controller	Hard drives CD/DVD players electric vehicles	DC switching, Perm
Universal motor	High starting torque, compact, high speed	Maintenance (brushes) Medium lifespan	Portable tools Grid powered	Uni-phase AC or Direct DC
Stepper DC: 1ph/2ph	Precision positioning High holding torque	High initial cost Requires a controller	Positioning in printers and floppy drives	DC switching
AC Synchronous	Rotation in-sync with freq - hence no slip long-life	More expensive	Industrial motors Clocks Audio turntables tape drives	UniPoly-phase AC

---

---

---

---

---

---

---

---

Type	Advantages	Disadvantages	Typical Application	Typical Drive
AC Induction (Shaded Pole)	Least expensive Long life low power	Rotation slips from frequency Low starting torque	Fans	difficult to control
AC Induction (Split-phase capacitor)	Medium power high starting torque	Rotation slips from frequency	Appliances Stationary Power Tools	Uni/Poly-phase AC
AC Squirrel cage 3ph	High power	Rotation slips from frequency	Industry hp machines	Inverter frequency Vector control (frequent)
Brushed DC	Low initial cost Simple speed control	Maintenance (brushes) Medium lifespan	Treadmill exercisers automotive motors (seats, blowers, windows)	Direct DC or PWM
BLDC	Long lifespan low maintenance High efficiency	High initial cost Requires a controller	Hard drives CD/DVD players electric vehicles	DC switching, PWM
Universal motor	High starting torque, compact, high speed	Maintenance (brushes) Medium lifespan	Portable tools Grid powered	Uni-phase AC or Direct DC
Stepper DC 1ph/2ph	Precision positioning High holding torque	High initial cost Requires a controller	Positioning in printers and floppy drives	DC switching
AC Synchronous	Rotation in-synch with freq - hence no slip long-life	More expensive	Industrial motors Clocks Audio turntables tape drives	Uni/Poly-phase AC

---

---

---

---

---


---

---

---

---

---

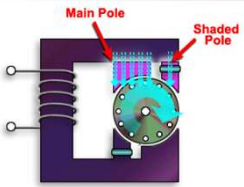

**Shaded pole induction motor**

**advantages**

- Very cheap and reliable
- Extremely rugged in nature
- Easy to construct

**disadvantages**

- Low starting torque
- Low efficiency

---

---

---

---

---


---

---

---

---

---

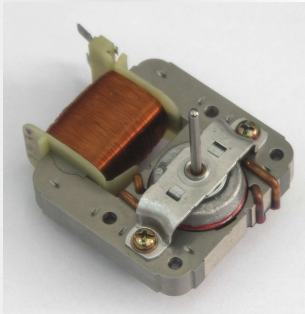

**Shaded pole induction motor**

---

---

---

---

---


---

---

---


---

---



University of Sheffield  
 Faculty of Engineering  
 Department of Electrical and Electronic Engineering
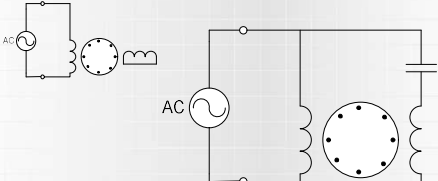
### Capacitor Run Permanent Split Capacitor(PSD Motor)



27

---

---

---


---

---

---


---

---



University of Sheffield  
 Faculty of Engineering  
 Department of Electrical and Electronic Engineering

### Split Phase Induction Motor

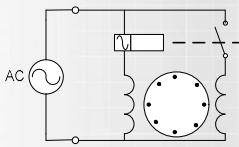

28

---

---

---


---

---

---


---

---



University of Sheffield  
 Faculty of Engineering  
 Department of Electrical and Electronic Engineering
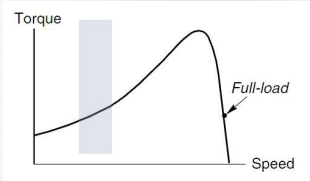
### Induction Motor control by means of slip control



29

---

---

---


---

---

---

---

---

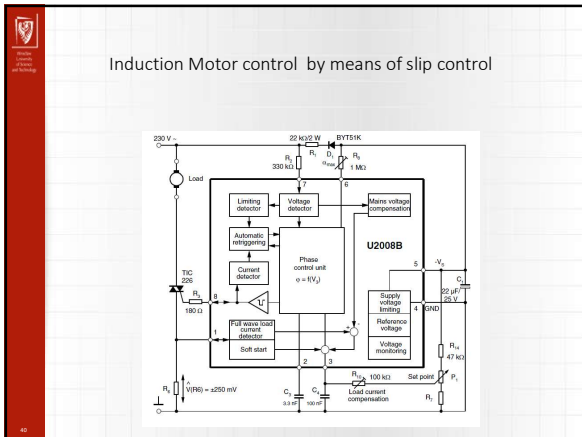


---

---

---


---

---

---

---

---

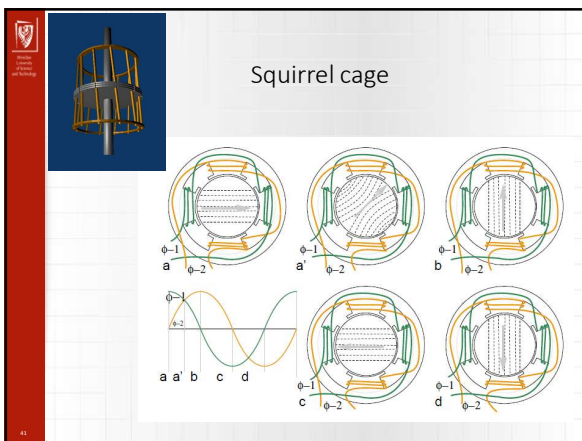


---

---

---


---

---

---

---

---

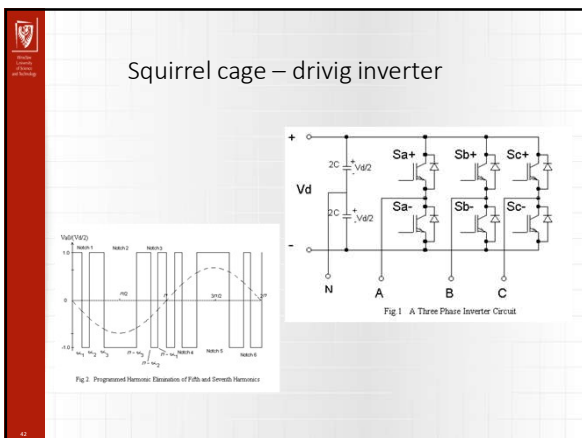


---

---

---




---

---

---

---

---

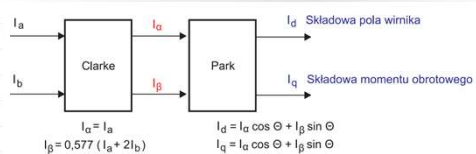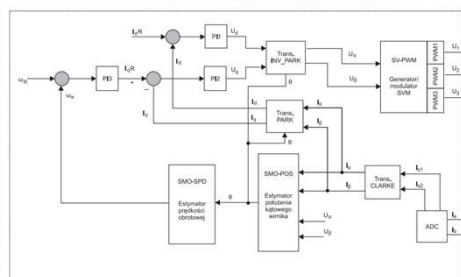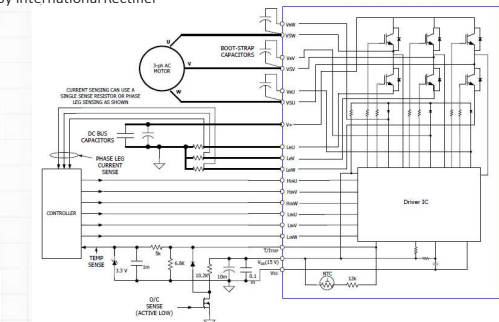


$$I_\alpha = I_a$$

$$I_\beta = 0,577 (I_a + 2I_b)$$

$$I_d = I_\alpha \cos \Theta + I_\beta \sin \Theta$$

$$I_q = I_\alpha \cos \Theta + I_\beta \sin \Theta$$



UNIVERSITY OF  
TWENTE  
Engineering

## Braking resistor

$$J = J_{Motor} + J_{Load} \quad \text{inertial momentum}$$

$$P_B = \frac{J\omega_B(\omega_B - \omega_0)}{t} \quad \text{Braking power}$$

$$R = \frac{V_{DC}^2}{P_B} \quad \text{Resistor}$$

$$P_{Res} = 1.30 * (P_B - P_{Inv}) \quad \text{Resistor power}$$

42



---

---

---

---

---

---



**Class 4 Noisy:** AC power and return, chassis ground, high-power RF and wideband signals; power inputs, outputs and DC links of adjustable speed motor drives, welding equipment, and similar electrically noisy equipment

**Class 3 Slightly Noisy:** DC power, suppressed switched loads, filtered AC; externally supplied low-voltage AC or DC power which does not also supply other noisy equipment, contactor and solenoid coil circuits

**Class 2 Slightly Sensitive:** low-power low frequency signals, low bit rate digital data; analogue instrumentation (e.g. 4–20 mA, 0–10V) and slow digital bus communications (e.g. RS232, RS422, RS485, Centronics); switched I/O such as limit switches, encoders, and the outputs of internal DC power supplies

**Class 1 Sensitive:** low-level analogue signals such as thermocouples, thermistors, RTDs, strain gauges, load cells, microphones; also wideband digital and analogue communications such as Ethernet, video, RF receiver inputs; and all other signals with full-scale range less than 1V or 1mA, or with a source impedance > 1kΩ, or signal frequency > 1MHz

Figure from: Tim Williams, „EMC for Product Designers“, 5th edition, Elsevier, 2017

---

---

---

---

---

---

---

---

Parasitic common mode paths from a VSD

Figure from: Tim Williams, „EMC for Product Designers“, Fifth edition, Elsevier, 2017

---

---

---

---

---

---

---

---

Filtering a VSD output

Figure from: Tim Williams, „EMC for Product Designers“, Fifth edition, Elsevier, 2017

---

---

---

---

---

---

---

---

Grounding of CM filters

Figure from: Tim Williams, „EMC for Product Designers“, Fifth edition, Elsevier, 2017

---

---

---

---

---

---

---

---

Converter-to-load cabling

Figure from: Tim Williams, „EMC for Product Designers“, Fifth edition, Elsevier, 2017

---

---

---

---

---

---

---

---

---

---

---

---

---

---

---

---




---

---

---

---

---

---

---

---

Type	Advantages	Disadvantages	Typical Application	Typical Drive
AC Induction (Shaded Pole)	Least expensive Long life low power	Rotation slips from frequency Low starting torque	Fans	difficult to control
AC Induction (split-phase capacitor)	Medium power high starting torque	Rotation slips from frequency	Appliances Stationary Power Tools	UniPoly-phase AC
AC Squirrel cage 3ph	High power	Rotation slips from frequency	Industry/ hp machines	Inverter frequency Vector control (if current)
Brushed DC	Low initial cost Simple speed control	Maintenance (brushes) Medium lifespan	Treadmill exercisers automotive motors (seats, blowers, windows)	Direct DC or PWM
BL DC	Long lifespan low maintenance High efficiency	High initial cost Requires a controller	Hard drives CD/DVD players electric vehicles	DC switching, Pwm
Universal motor	High starting torque, compact, high speed	Maintenance (brushes) Medium lifespan	Portable tools Grid powered	Uni-phase AC or Direct DC
Stepper DC 1ph/2ph	Precision positioning High holding torque	High initial cost Requires a controller	Positioning in printers and floppy drives	DC switching
AC Synchronous	Rotation in-sync with freq - no slip long-life	More expensive	Industrial motors Clocks Audio turntables tape drives	UniPoly-phase AC

---

---

---

---

---

---

---

---

### DC motors

#### PMDC – Permanent Magnet DC

High starting torque,  
compact,  
high speed,  
easy to control,  
cheap

Maintenance (brushes)  
Medium lifetime,  
Noisy  
EMI emission

---

---

---


---

---

---

---

---

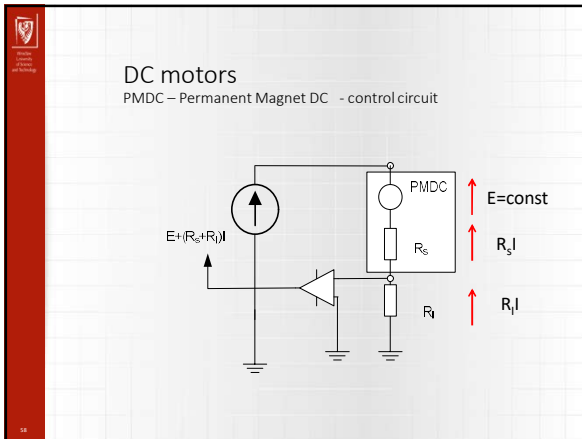


---

---

---


---

---

---

---

---

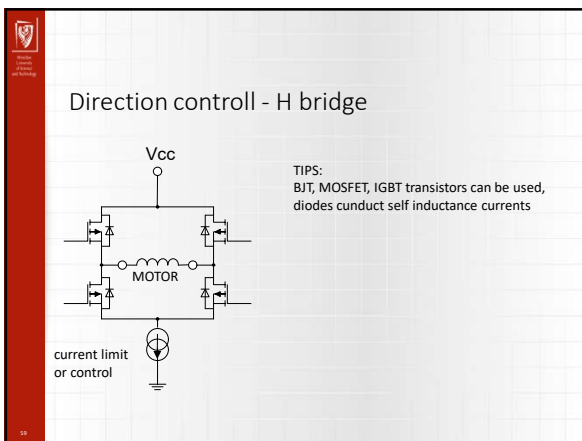


---

---

---


---

---

---

---

---

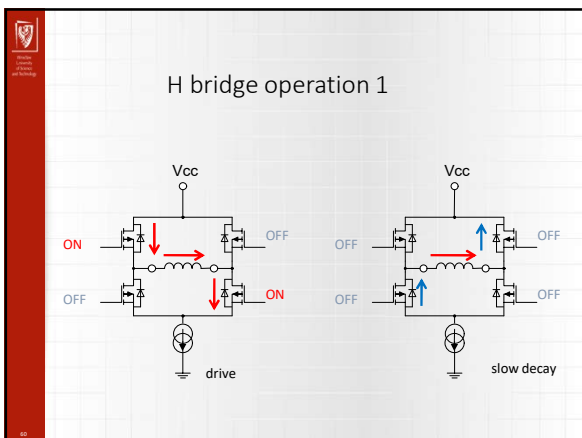


---

---

---


---

---

---

---

---

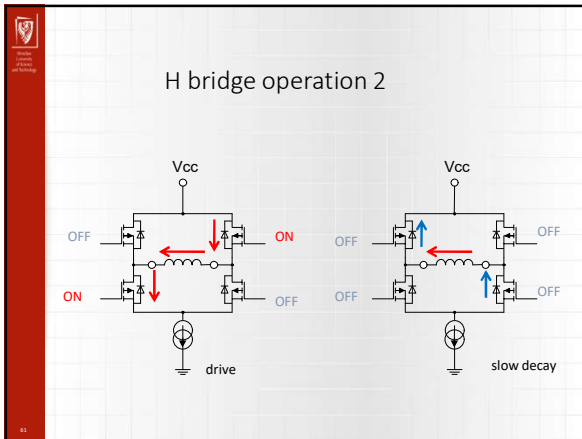


---

---

---


---

---

---

---

---

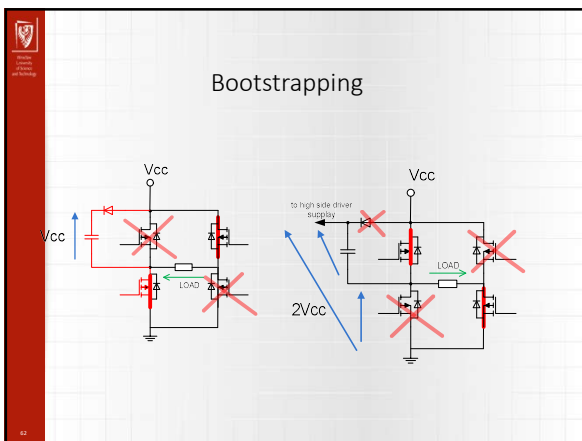


---

---

---


---

---

---

---

---

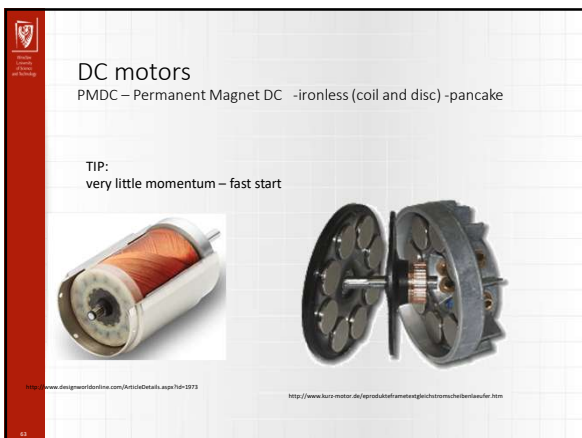


---

---

---

---

---

---

---

---

Type	Advantages	Disadvantages	Typical Application	Typical Drive
AC Induction (Shaded Pole) (31)	Least expensive Long life low power	Rotation slips from frequency Low starting torque	Fans	difficult to control
AC Induction (split phase capacitor) (34)	Medium power high starting torque	Rotation slips from frequency	Appliances Stationary Power Tools	Uni/Poly-phase AC
AC Squirrel cage 3ph (40)	High power	Rotation slips from frequency	Industry/ hp machines	Inverter frequency Vector control (frequent)
Brushed DC (41)	Low initial cost Simple speed control	Maintenance (brushes) Medium lifespan	Treadmill exercisers automotive motors (seats, blowers, windows)	Direct DC or <a href="#">PWM</a>
BL DC (49)	Long lifespan low maintenance High efficiency	High initial cost Requires a controller	Hard drives CD/DVD players electric vehicles	DC switching, Pwm
Universal motor (61)	High starting torque, compact, high speed	Maintenance (brushes) Medium lifespan	Portable tools Grid powered	Uni-phase AC or Direct DC
Stepper DC 1ph/2ph (66)	Precision positioning High holding torque	High initial cost Requires a controller	Positioning in printers and floppy drives	DC switching
AC Synchronous (82)	Rotation in-sync with freq - hence no slip long life	More expensive	Industrial motors Clocks Audio turntables tape drives	Uni/Poly-phase AC

---

---

---

---

---


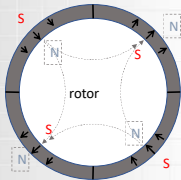
---

---

---

---

---

### BLDC (BrushLess DC) motors

---

---

---

---

---

---

---

---

---

---




### BLDC 1 phase

---

---

---

---

---


---

---

---

---

---

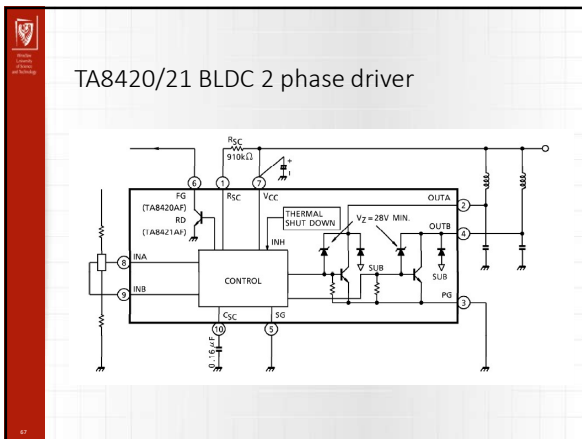


---

---

---


---

---

---

---

---

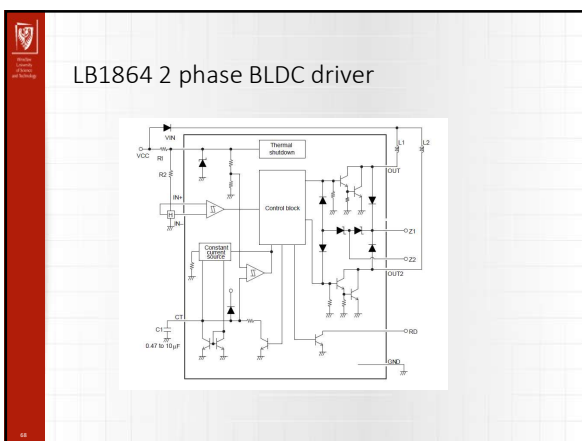


---

---

---


---

---

---

---

---

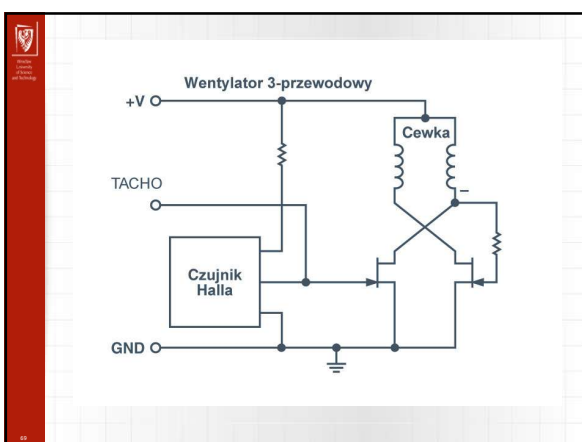


---

---

---


---

---

---

---

---

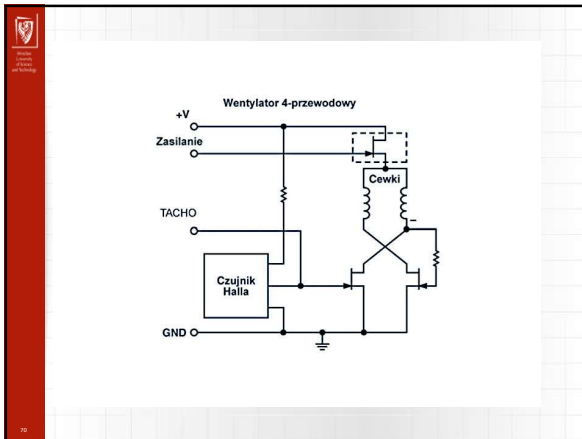


---

---

---


---

---

---

---

---

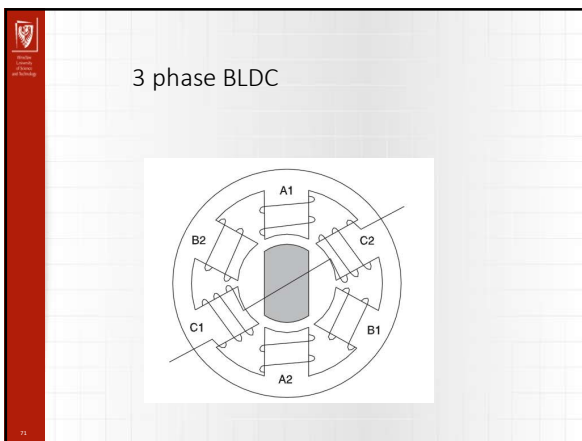


---

---

---


---

---

---

---

---

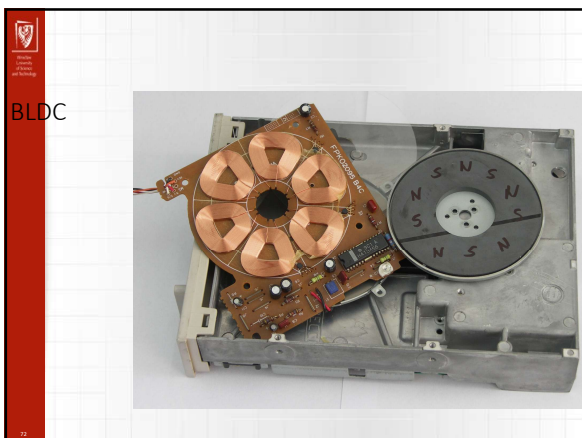


---

---

---

---


---

---

---

---



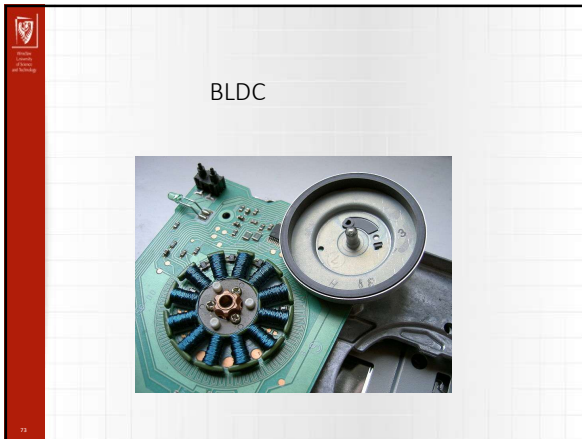


---

---

---


---

---

---

---

---

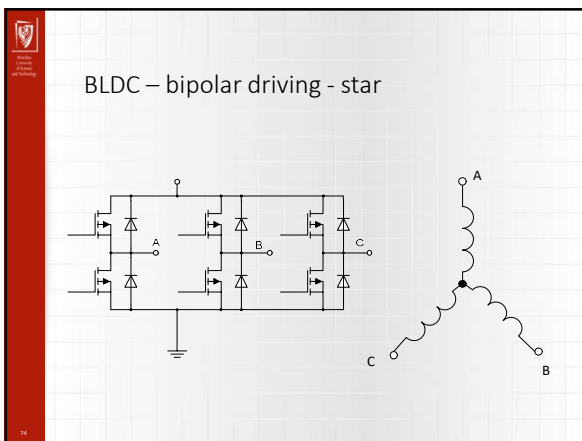


---

---

---


---

---

---

---

---

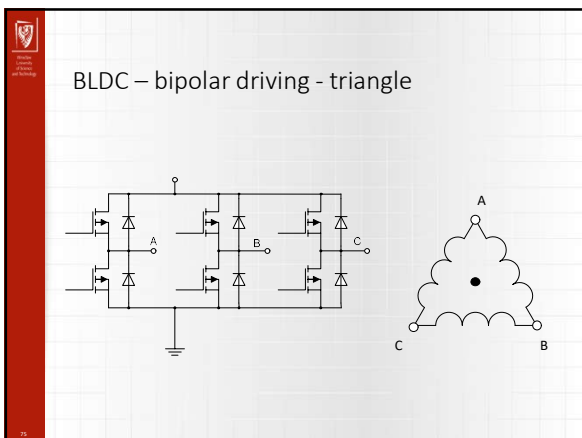


---

---

---

---


---

---

---

---



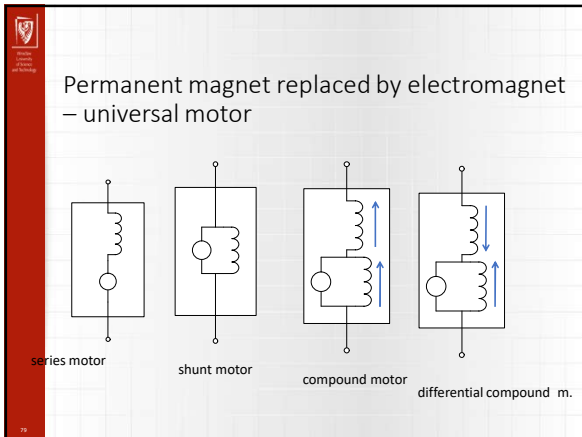


---

---

---


---

---

---

---

---

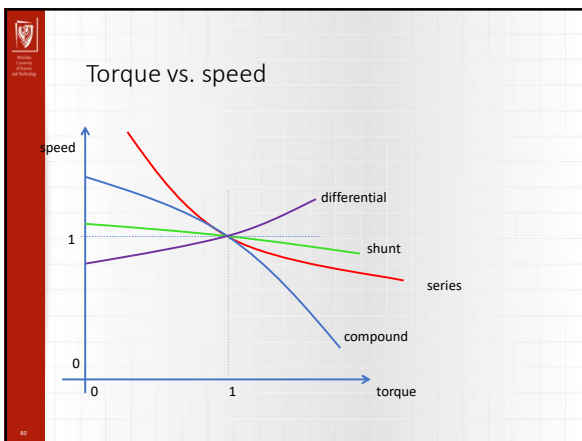


---

---

---


---

---

---

---

---

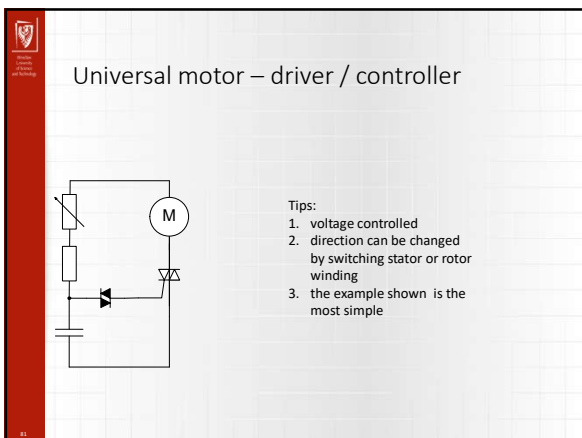


---

---

---


---

---

---

---

---

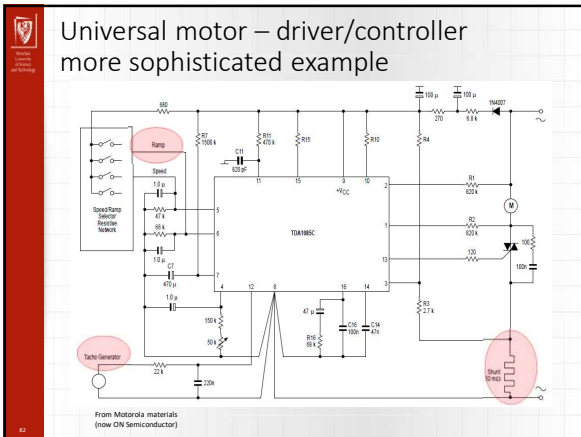


---

---

---

---

---

---

---

---

Type	Advantages	Disadvantages	Typical Application	Typical Drive
AC Induction (Shaded Pole)	Least expensive Long life Low power	Rotation slips from frequency Low starting torque	Fans	difficult to control
AC Induction (split-phase capacitor)	Medium power high starting torque	Rotation slips from frequency	Appliances Stationary Power Tools	Uni/Poly-phase AC
AC Squirrel cage 3ph	High power	Rotation slips from frequency	Industry/ hp. machines	Inverter frequency Vector control (if current)
Brushed DC	Low initial cost Simple speed control	Maintenance (brushes) Medium lifespan	Treadmill exercisers automotive motors (seats, blowers, windows)	Direct DC or PWM
BL DC	Long lifespan low maintenance High efficiency	High initial cost Requires a controller	Hard drives CD/DVD players electric vehicles	DC switching, Pwm
Universal motor	High starting torque, compact, high speed	Maintenance (brushes) Medium lifespan	Portable tools Grid powered	Uni-phase AC or Direct DC
Stepper DC 1ph/2ph	Precision positioning High holding torque	High initial cost Requires a controller	Positioning in printers and floppy drives	DC switching
AC Synchronous	Rotation in-synch with freq - hence no slip long life	More expensive	Industrial motors Clocks Audio turntables tape drives	Uni/Poly-phase AC

---

---

---


---

---

---

---

---

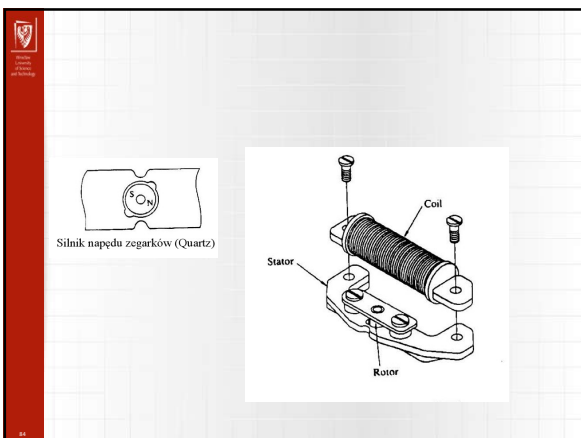


---

---

---

---

---

---

---

---

bipolar winding  
H bridge needed

unipolar winding  
single switch

---


---

---


---

---


---



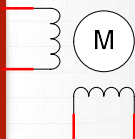
# (2 phase) stepppper motor internal conections




4 wires  
(bipolar only)

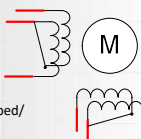

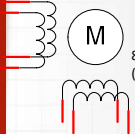6 wires  
(bipolar handicapped/  
unipolar)



8 wires  
(bipolar/unipolar)

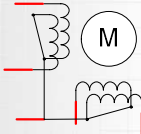

5 wires  
(unipolar only)

84

---

---

---

---

---

---

University of Technology

# Unipolar/Bipolar stepper motor driving

The image displays two circuit diagrams for stepper motor driving. The left diagram illustrates a unipolar motor driver, featuring a central coil connected to a common ground and four transistors (two PNP and two NPN) that can be switched independently. The right diagram shows a bipolar motor driver, where the coil is connected between two transistors (one PNP and one NPN) and a common ground, allowing for current flow in both directions through the coil.

---

---


---

---

---


---

## Stepper motor – reluctance motor

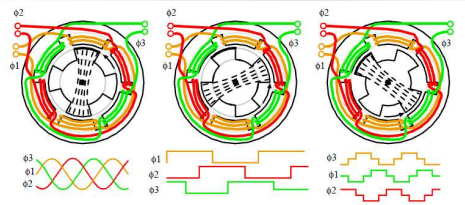

Lessons in Electric Circuits, Volume II – AC By Tony R. Kuphaldt, Sixth Edition, last update July 25, 2007

# Permanent magnet motor wave driving

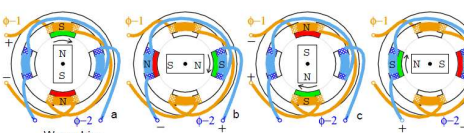


Wave drive

4  
3  
2  
1  
0  
-1  
-2  
-3  
-4

a b c d

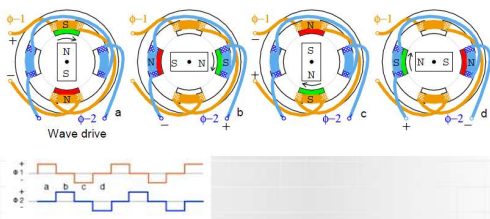Lessons in Electric Circuits, Volume II – AC by Tony R. Kuphaldt, Sixth Edition, last update July 25, 2007



Lessons In Electric Circuits, Volume II – AC By Tony R. Kuphaldt, Sixth Edition, last update July 25, 2007

# Permanent magnet motor full step driving

The diagram illustrates the four steps of a 2-pole, 4-phase permanent magnet motor in full step driving. Each step shows the rotor position and the current in the four phases (a, b, c, d). The rotor has four poles labeled N, S, N, S. The stator has four poles labeled a, b, c, d. The current in each phase is indicated by a number and a sign (+ or -). The steps are labeled a, b, c, and d.


Step a: Phase a is +1, phase b is -2, phase c is 0, and phase d is 0. The rotor is in position a.

Step b: Phase a is 0, phase b is +1, phase c is -2, and phase d is 0. The rotor is in position b.


Step c: Phase a is 0, phase b is 0, phase c is +1, and phase d is -2. The rotor is in position c.

Step d: Phase a is -2, phase b is 0, phase c is 0, and phase d is +1. The rotor is in position d.


The diagram also shows the current waveforms for each phase. The current in phase a is a square wave that is +1 for step a and 0 for steps b, c, and d. The current in phase b is a square wave that is -2 for step a, +1 for step b, and 0 for steps c and d. The current in phase c is a square wave that is 0 for steps a and b, +1 for step c, and -2 for step d. The current in phase d is a square wave that is 0 for steps a, b, and c, and +1 for step d.

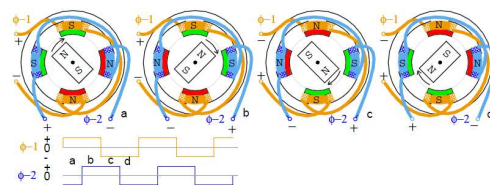

Lessons in Electric Circuits, Volume II – AC by Tony R. Kuphaldt, Sixth Edition, last update July 25, 2007



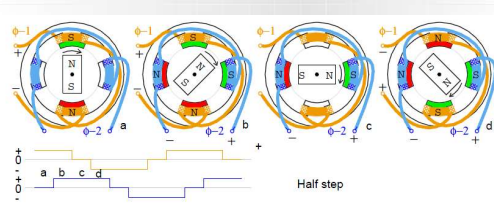Permanent magnet motor  
half step driving



Half step

Leachman Electric Circuits, Volume 8 - AC By Tony R. Rughvelli, Sixth Edition, last update July 25, 2007

51

---

---

---


---

---


---

---

---



Full/microstep  
driving

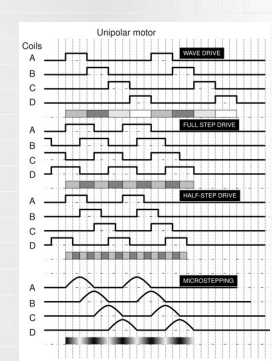

Unipolar motor

Coils  
A  
B  
C  
D

Full Step  
Half Step  
Microstepping  
Microstepping

52

---

---

---


---

---

---


---

---



Hybrid motor

1,3,5,7 - phase A  
2,4,6,8 - phase B

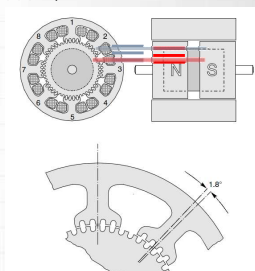

$$Step = \frac{360deg}{N_{teeth} \cdot N_{phases}}$$

53

---

---

---


---

---

---

---

---

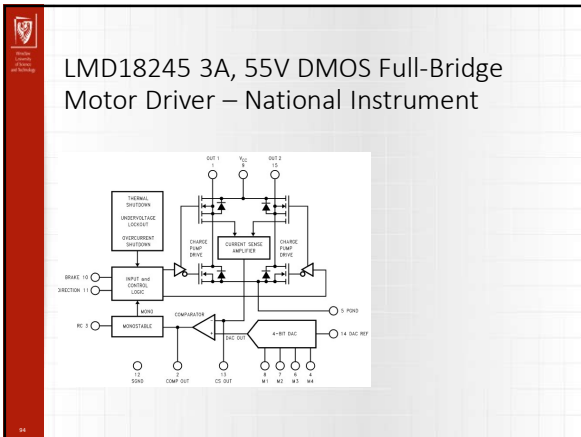


---

---

---


---

---

---

---

---

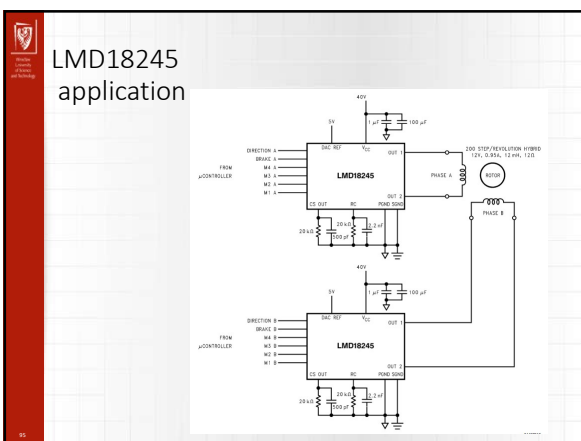


---

---

---


---

---

---

---

---

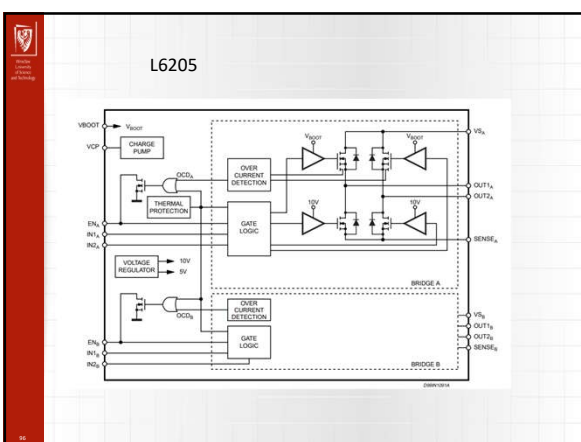


---

---

---

---


---

---

---

---



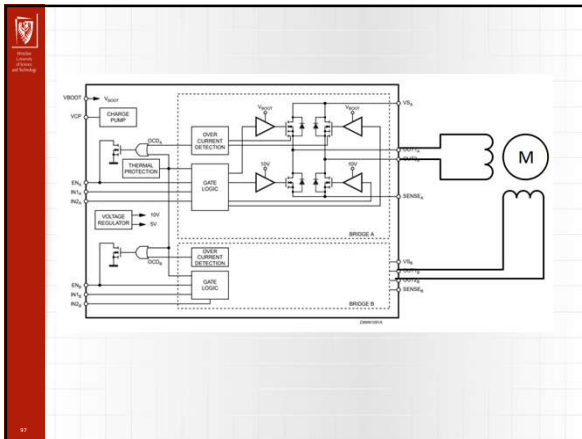


---

---

---


---

---

---

---

---

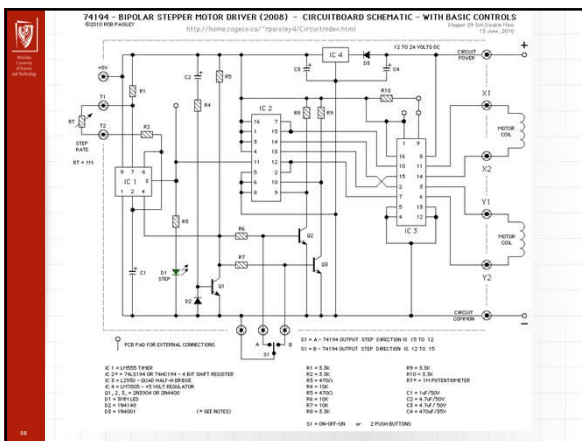


---

---

---


---

---

---

---

---

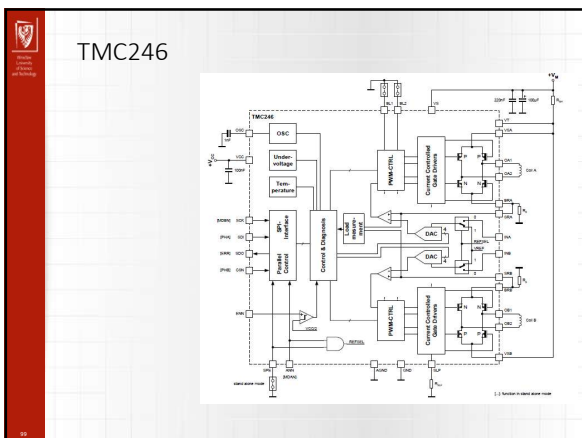


---

---

---

---

---

---

---

---

[illegible][illegible]

Type	Advantages	Disadvantages	Typical Application	Typical Drive
<b>AC Induction</b> <b>(Shaded Pole)</b> (31)	Least expensive Long life lowpower	Rotation slips from frequency Low starting torque	Fans	difficult to control
<b>AC Induction</b> <b>(split-phase capacitor)</b> (34)	Medium power High starting torque	Rotation slips from frequency	Appliances Stationary Power Tools	Uni/Pol-phase AC
AC Squirrel cage 3ph (40)	High power	Rotation slips from frequency	Industry/ hp machines	Inverter frequency Vector control (trickumt)
<b>Brushed DC</b> (41)	Low initial cost Simple speed control	Maintenance (brushes) Medium lifespan	Treadmill exercisers automotive motors (seats, bowsters, windows)	Direct DC or <b>PWM</b>
<b>BL DC</b> (49)	Long lifespan low maintenance High efficiency	High initial cost Requires a controller	Hard drives C/DVD players electric vehicles	DC switching, Pwm
<b>Brushless motor</b> (51)	High starting torque, compact, high speed	Maintenance (brushes) Medium lifespan	Portable tools Grid powered	Uni-phase AC or Direct DC
<b>Brushed DC</b> 1ph/2ph (66)	Precision positioning High holding torque	High initial cost Requires a controller	Positioning in printers and foppy drives	DC switching
<b>VC Synchronous</b> (82)	Rotation in-synch with freq - hence no slip long-life	More expensive	Industrial motors Clocks Audio turntables tape drives	Uni/Pol-phase AC

---

---


---

---

---

---

# Synchronous motor

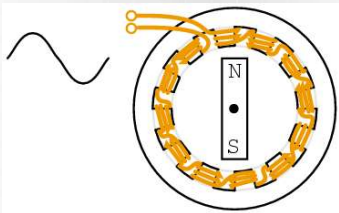

The diagram illustrates a synchronous motor. It features a circular stator with 12 poles, represented by yellow rectangular segments. A central rotor has two poles, labeled 'N' (North) and 'S' (South), with a black dot indicating the rotor's center. Two orange lines connect the stator terminals to a sine wave, representing the AC supply. The entire motor is enclosed in a black circular frame.

Lectures in Electric Circuits, Volume 9 – AC By Tony R. Raghunath, Sixth Edition, last update July 25, 2007

310

---


---

---

---


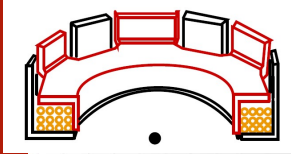
---

---





University of Sheffield

### Multipole synchronous motor

The induction or self starting and the bar magnet as synchronous motor





100

---

---

---


---

---


---


---

---



University of Sheffield





101

---

---

---

---

---

---

---

---



University of Sheffield

### Synchronous motor





102

---

---

---

---

---

---

---

---



---

---

---

---

---

---

---



---

---


---

---

---

---

---

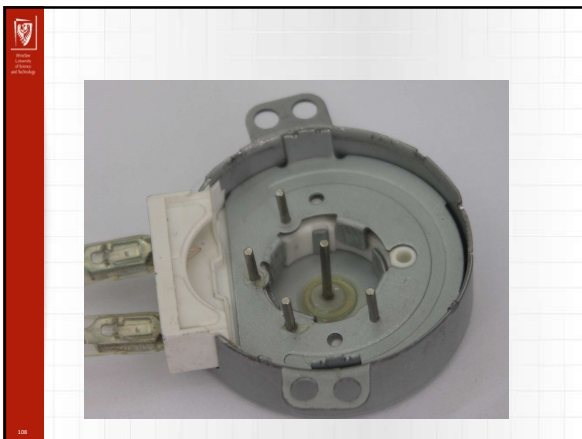

---

---

---

---

---

---

---



---

---


---

---

---

---

---

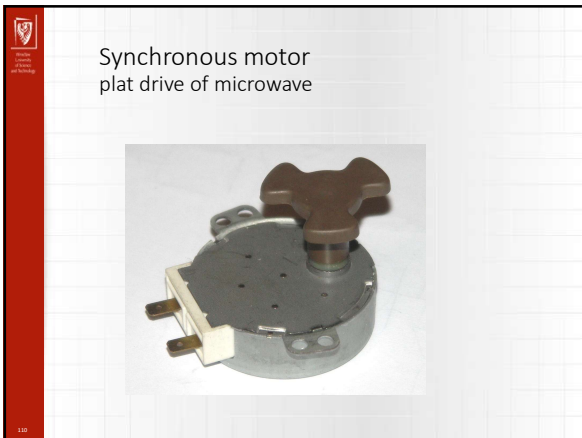

---

---


---

---

---

---

---

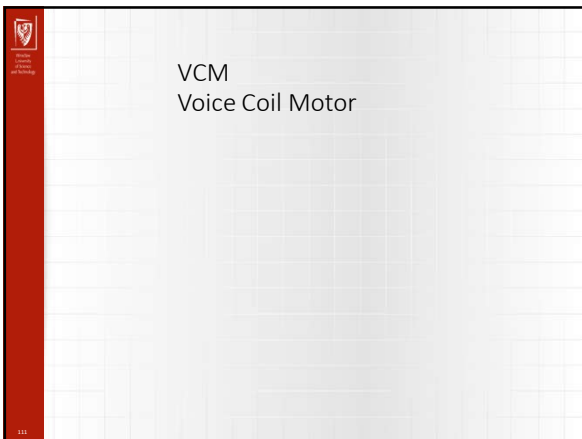

---

---



---

---


---

---

---

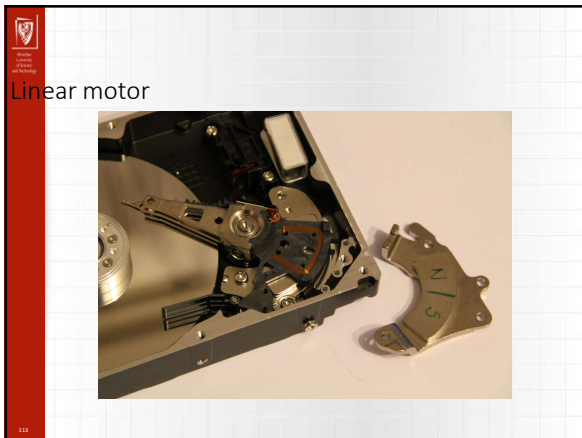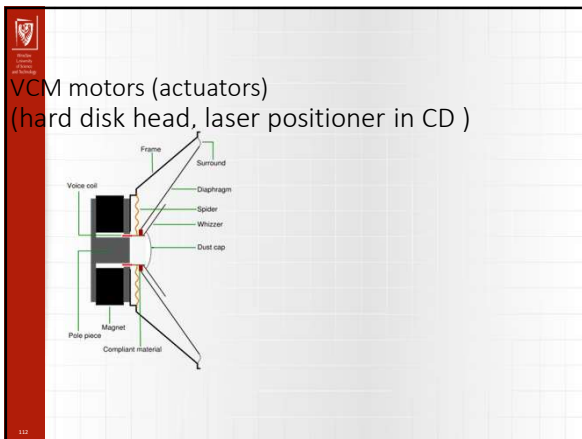

Type	Advantages	Disadvantages	Typical Application	Typical Drive
AC Induction (Shaded Pole)	Least expensive Long life Low power	Rotation slips from frequency Low starting torque	Fans	difficult to control
AC Induction (with phase capacitor)	Medium power High starting torque	Rotation slips from frequency	Appliances Stationary Power Tools	Uni/Poly-phase AC
AC Squirrel cage 3ph	High power	Rotation slips from frequency	Industry/ hp machines	Inverter frequency Vector control (Bloomberg)
Brushed DC	Low initial cost Simple speed control	Maintenance (brushes) Medium lifespan	Treadmill exercisers automotive motors (seats, blowers, windows)	Direct DC or PWM
BL DC	Long lifespan low maintenance High efficiency	High initial cost Requires a controller	Hard drives CD/DVD players electric vehicles	DC switching, PWM
Universal motor	High starting torque, compact, high speed	Maintenance (brushes) Medium lifespan	Portable tools Grid powered	Uni-phase AC or Direct DC
Stepper DC 1ph/2ph	Precision positioning High holding torque	High initial cost Requires a controller	Positioning in printers and floppy drives	DC switching
AC Synchronous	Rotation in-sync with freq - hence no slip long-life	More expensive	Industrial motors Clocks Audio turntables tape drives	Uni/Poly-phase AC



## Summary

- Electromechanical relays
- SSR
- AC motors
  - squirrel cage (3 phase, shade pole, capacitor, split phase)
  - synchronous
- DC motors
  - Permanent magnet DC
  - Universal motors
- Brushless DC (BLDC)
- Step motors
- Linear (Voice Coil Motor – VCM)

---

---

---


---

---

---

---

---



## Test questions example:

- What are the basic types of relays ?
- What is the role of a protection (flyback) diode in an electromechanical relay control circuit??
- Compare types of motors there basic features and way of control them:
  - AC Induction (Shaded Pole),
  - AC Induction (split-phase capacitor/inductor),
  - AC Squirrel cage(3 phase),
  - Brushed DC
  - Brushless DC
  - Universal motor,
  - Stepper motor,
  - AC Synchronous motor.

---

---

---

---

---

---

---

---