



Wrocław University of Science and Technology

Basic blocks of converters

Jerzy Mikulski





Wrocław University of Science and Technology

References


1. Marcelo Godoy Simões and Tiago Davi Curi Busarello , Power Electronic Converters and Systems, 2nd Edition Volume 1 (source of illustrations)




Wrocław University of Science and Technology

Serial & parallel controller

$$I_1 = I_z + I_o$$
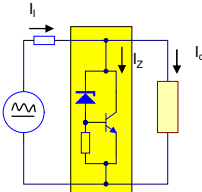
$$P_{loses} = I_z U_o + I_1 (E - U_o)$$


$$I_1 \approx I_o$$
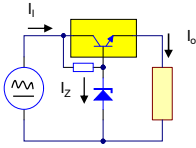
$$P_{loses} = I_1 (E - U_o)$$


Smaller dissipation power
Better efficiency



Linear vs. Pulse (switching) controller

$P_{\text{strat}} \approx (E - U_o) I_o$

Smaller dissipation power
Better efficiency

$P_{\text{strat}} \approx U_{\text{sat}} I_{\text{max}}$

$U_o = U_{AV} = \frac{t_{on}}{t_{on} + t_{off}} E$

Even smaller dissipation power
Even better efficiency


The average value of the impulse waveform


$U_{AV} = \frac{t_{on}}{T} E = \gamma E$


$T = t_{on} + t_{off}$ T – period
 $\gamma = t_{on}/T$ – duty factor

Step down converter

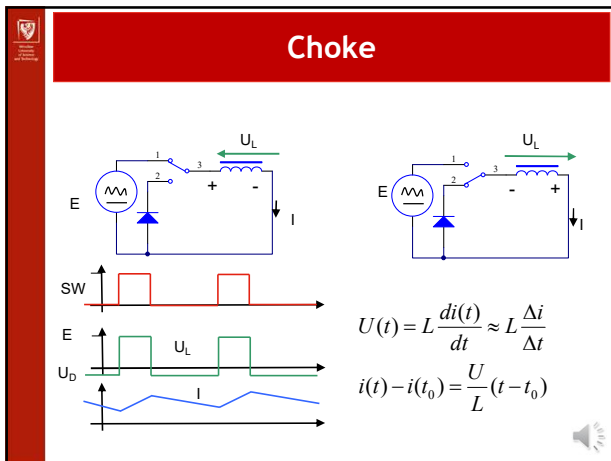
$U_o = U_{AV} = \frac{t_{on}}{t_{on} + t_{off}} E = \gamma E$




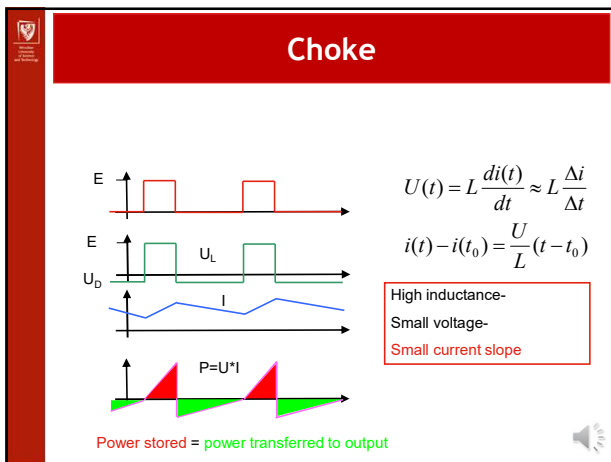

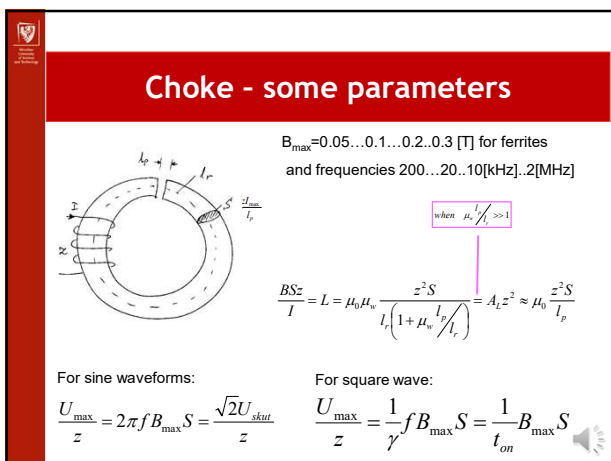

Step down (buck) converter

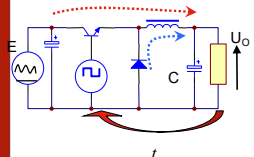

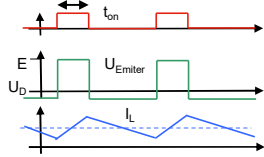

$$U_o = \gamma E = \frac{t_{on}}{T} E$$

$$I_{L,max} \approx 2 I_{O,max}$$

$$L_{min} \geq \frac{E - U_o}{I_{L,max}} t_{on}$$


$$C > \frac{I_{O,max} T}{4 U_{O,ripp}}$$


U_o – output voltage,
 E – input voltage,
 t_{on}, t_{off}, T – turn on, off, period
 $I_{L,peak}$ – peak current of choke and switch
 L_{min} – minimum inductance
 $U_{O,ripp}$ – ripple output voltage

simplified way of deriving equation of the output voltage of the step-down converter

chalk board or separate video

Step down converter (discontinuous mode)

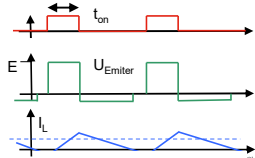

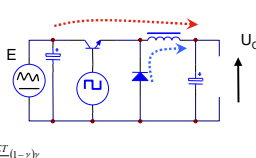

$$U_o = \frac{ET}{2L} (1 - \gamma)^2$$

Output voltage can reach the value E !!!

self-excited step-down controller

Step up (boost) converter

$$U_0 = \frac{1}{1-\gamma} E$$

$$I_{L_{oscyl}} \approx 2I_{Omax} \left(1 + \frac{L_{min}}{t_{off}} \right)$$

$$I_{min} \geq \frac{E}{L_{oscyl}} t_{on}$$

$$C > \frac{I_{Omax} T}{U_{Oripp}}$$

U_0 – output voltage,
 E – input voltage,
 t_{on}, t_{off}, T – turn on, off, period
 $I_{L_{peak}}$ – peak current of choke and switch
 L_{min} – minimum inductance
 U_{Oripp} – ripple output voltage

simplified way of deriving equation of the output voltage of the step-up converter

chalk board or separate video

Inverter (buck-boost)

$$U_o = -\frac{\gamma}{1-\gamma} E$$

$$I_{L,avg} \approx 2I_{O,max} \left(\frac{1}{1-\gamma} \right)$$

$$I_{L,min} \geq \frac{E}{L_{avg}} t_{on}$$

$$C > \frac{I_{O,max} T}{U_{O,ripple}}$$


U_o – output voltage,
 E – input voltage,
 t_{on}, t_{off}, T – turn on, off, period
 $I_{L,peak}$ – peak current of choke and switch
 L_{min} – minimum inductance
 $U_{O,ripp}$ – ripple output voltage

simplified way of deriving equation of the output voltage of the inverter

chalk board or separate video

Inverter


Inverter (discontinuous mode)

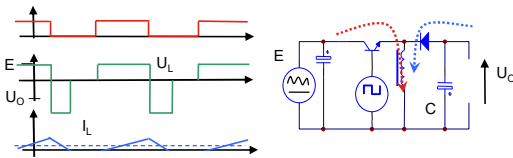


$$I_O < I_{Okryt} = \frac{E\gamma}{2L}(1-\gamma)T$$


Output voltage can ∞ !!!

Step up MC34063

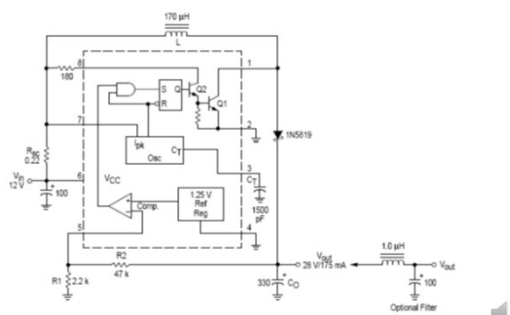

Inverting MC34063

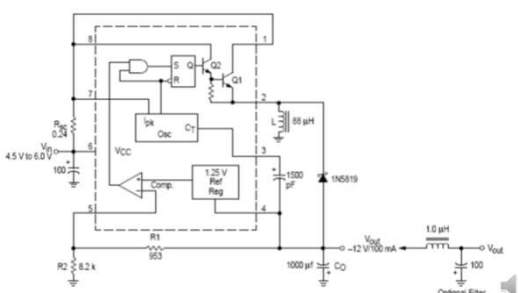


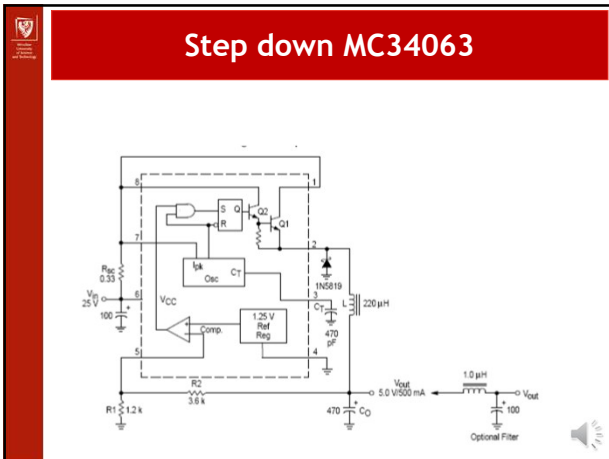


MC34063 data sheet expressions

Calculation	Step-Up	Step-Down	Voltage-Inverting
t_{on}/t_{off}	$\frac{V_{out} - V_F - V_{in(min)}}{V_{in(max)} - V_{sat}}$	$\frac{V_{out} + V_F}{V_{in(max)} - V_{sat} - V_{out}}$	$\frac{(V_{out} + V_F)}{V_{in} - V_{sat}}$
$t_{on} + t_{off}$	$\frac{1}{f}$	$\frac{1}{f}$	$\frac{1}{f}$
t_{off}	$\frac{t_{on} + t_{off}}{t_{off} + 1}$	$\frac{t_{on} + t_{off}}{t_{off} + 1}$	$\frac{t_{on} + t_{off}}{t_{off} + 1}$
t_{on}	$(t_{on} + t_{off}) - t_{off}$	$(t_{on} + t_{off}) - t_{off}$	$(t_{on} + t_{off}) - t_{off}$
CT	$4.0 \times 10^{-5} t_{on}$	$4.0 \times 10^{-5} t_{on}$	$4.0 \times 10^{-5} t_{on}$
$i_{pk(switch)}$	$2I_{out(max)} \left(\frac{t_{on}}{t_{off}} + 1 \right)$	$2I_{out(max)}$	$2I_{out(max)} \left(\frac{t_{on}}{t_{off}} + 1 \right)$
R_{ac}	$0.3 I_{pk(switch)}$	$0.3 I_{pk(switch)}$	$0.3 I_{pk(switch)}$
$I_{(min)}$	$\left(\frac{V_{in(min)} - V_{sat}}{I_{pk(switch)}} \right) t_{on(max)}$	$\left(\frac{V_{in(min)} - V_{sat} - V_{out}}{I_{pk(switch)}} \right) t_{on(max)}$	$\left(\frac{V_{in(min)} - V_{sat}}{I_{pk(switch)}} \right) t_{on(max)}$
CO	$9 \frac{I_{out(on)}}{V_{ripple(pp)}}$	$\frac{I_{pk(switch)}(t_{on} + t_{off})}{8V_{ripple(pp)}}$	$9 \frac{I_{out(on)}}{V_{ripple(pp)}}$

V_{sat} = Saturation voltage of the output switch.
 V_F = Forward voltage drop of the output rectifier.
 The following power supply characteristics must be chosen:
 V_{in} = Maximum input voltage.
 V_{out} = Desired output voltage. $R_{out} = 1.25 \left(1 + \frac{V_{out}}{V_{in}} \right)$
 I_{out} = Desired output current.
 t_{on} = Minimum desired output switching frequency at the selected values of V_{in} and I_{out} .
 $V_{ripple(pp)}$ = Desired peak-to-peak output ripple voltage. To prevent the calculated capacitor value will need to be increased due to its equivalent series resistance and board layout. The ripple voltage should be kept to a low value since it will directly affect the line and load regulation.

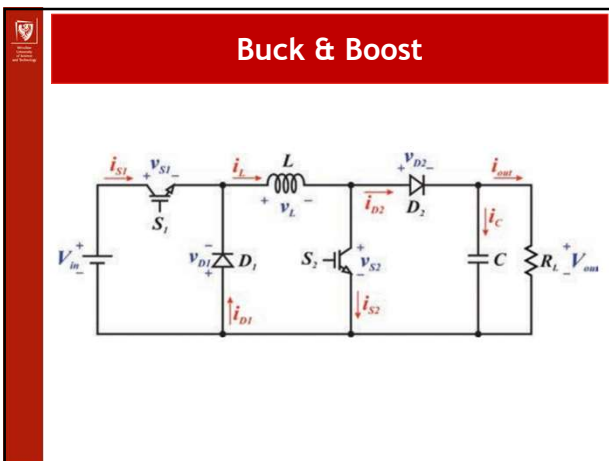


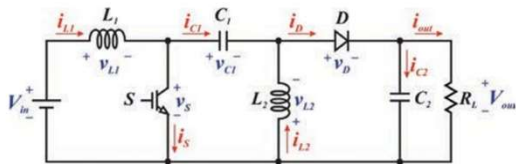SEPIC (Single-ended Primary-Inductor Converter)




$$V_{out} = V_{in} \frac{\gamma}{1 - \gamma}$$

Čuk

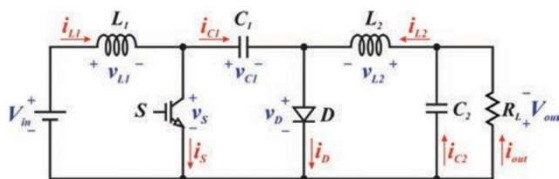



$$V_{out} = -V_{in} \frac{\gamma}{1 - \gamma}$$


Zeta

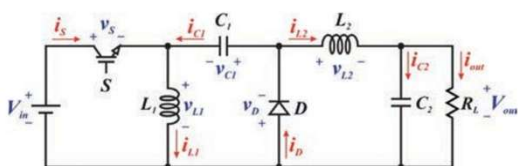
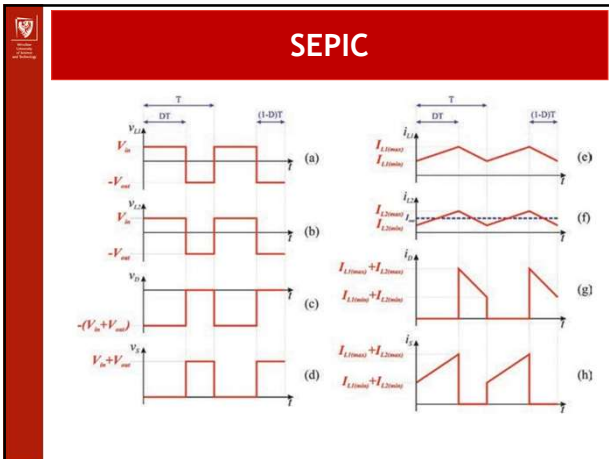
$$V_{out} = -V_{in} \frac{\gamma}{1 - \gamma}$$



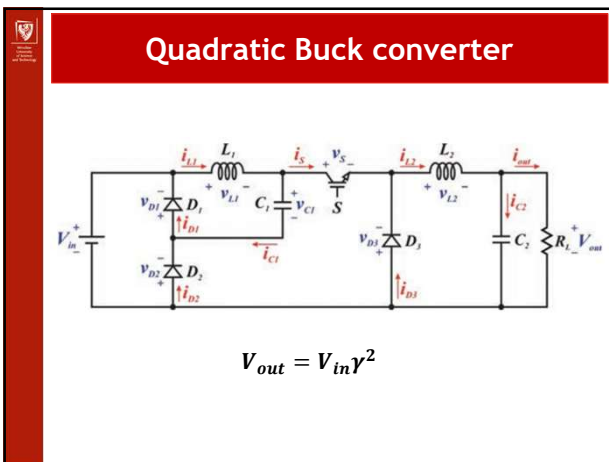

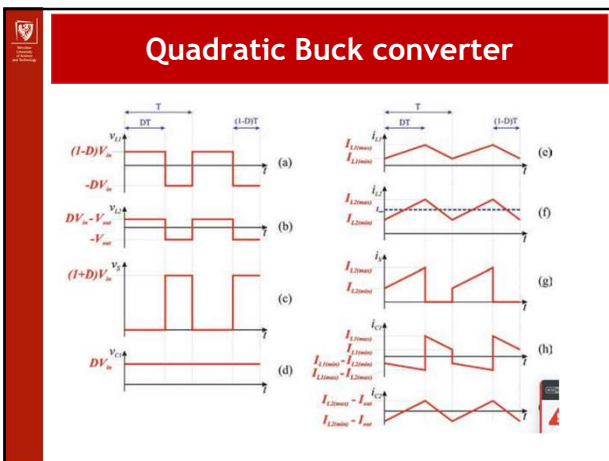


Quadratic Boost


$$V_{out} = V_{in} \frac{1}{(1-\gamma)^2}$$


Quadratic Boost


Flyback converter

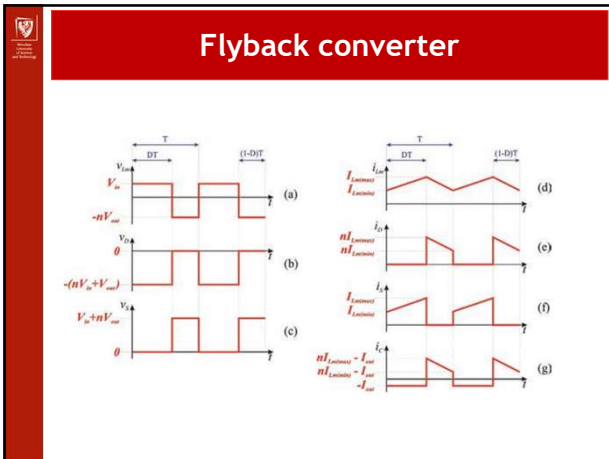
$$V_{out} = V_{in} \frac{1}{n(1-\gamma)}$$




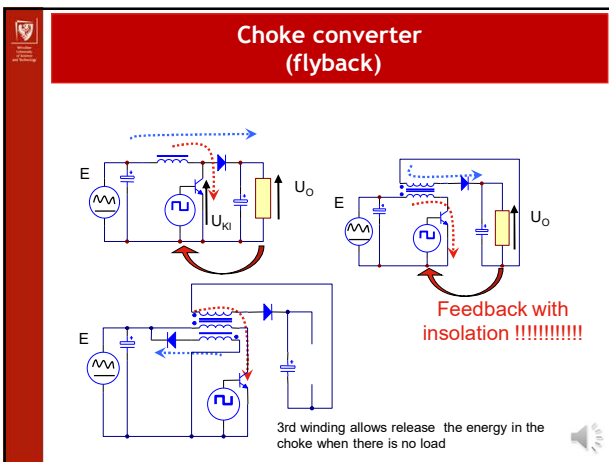

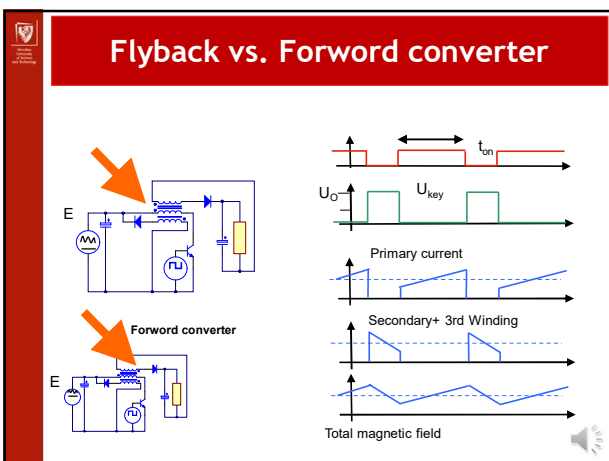

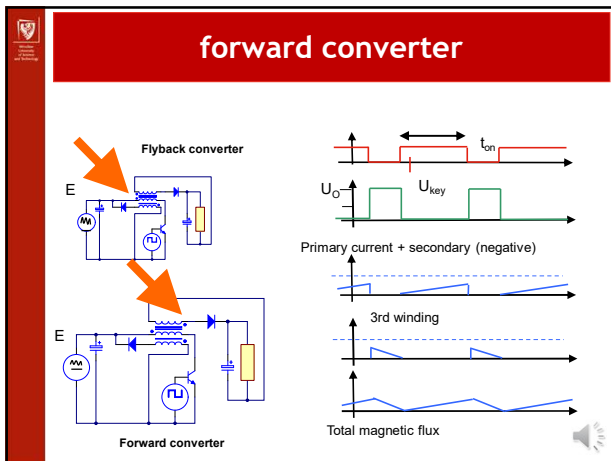

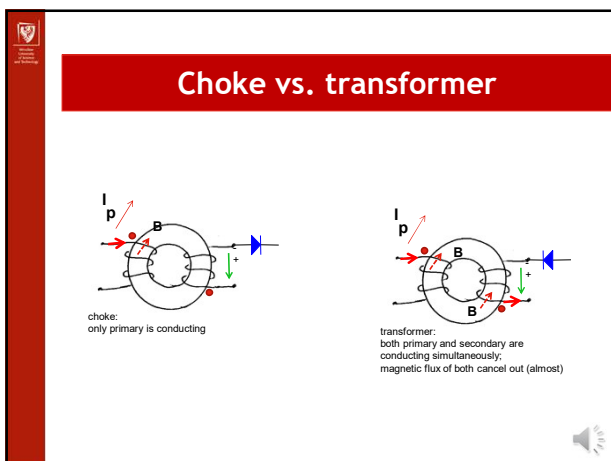

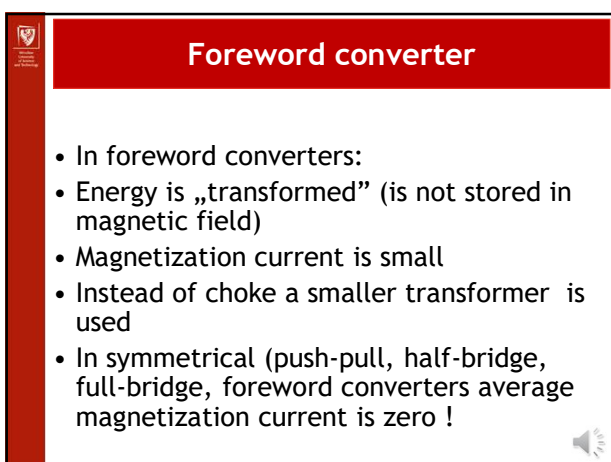

Forward converter


$$V_{out} = V_{in} \frac{\gamma}{n}$$

Forward converter


Two switch forward converter

$$V_{out} = V_{in} \frac{\gamma}{n}, \quad \gamma < 0.5$$

Two switch forward converter

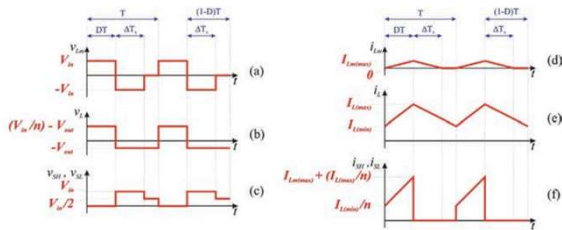


half-bridge converter

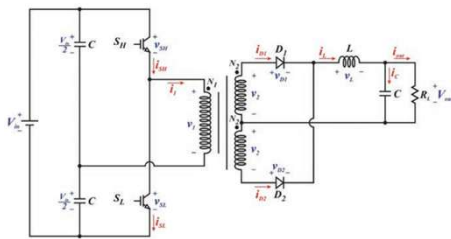

$$V_{out} = V_{in} \frac{\gamma}{n}, \quad \gamma < 0.5$$

half-bridge converter

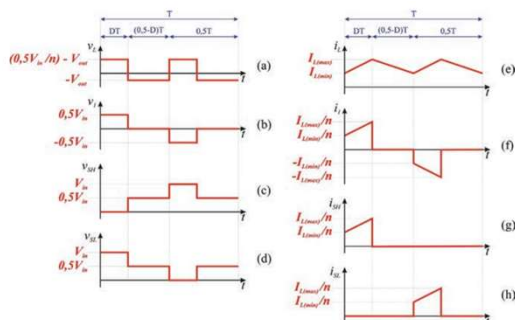


Full-bridge converter

$$V_{out} = V_{in} 2 \frac{\gamma}{n}; \quad \gamma < 0.5$$


Full-bridge converter (phase control)

High power converters (foreword)


PFC - peak current modulation

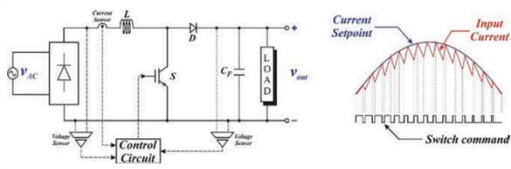



PFC - hysteresis modulation

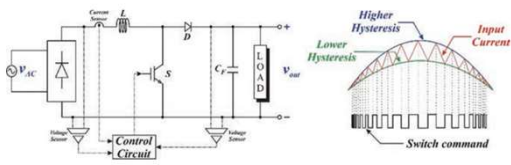


PFC - sinusoidal PWM


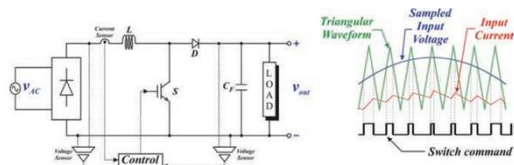


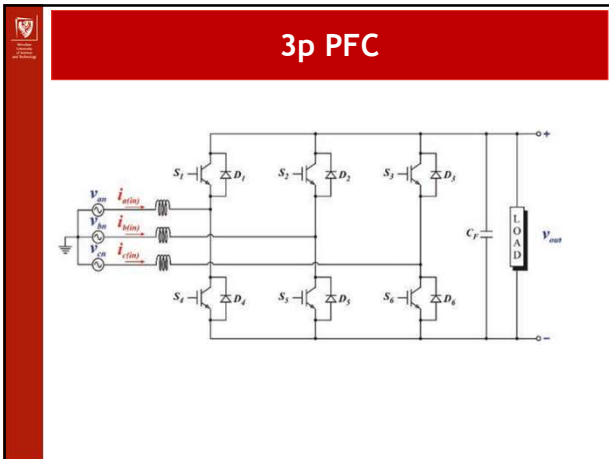


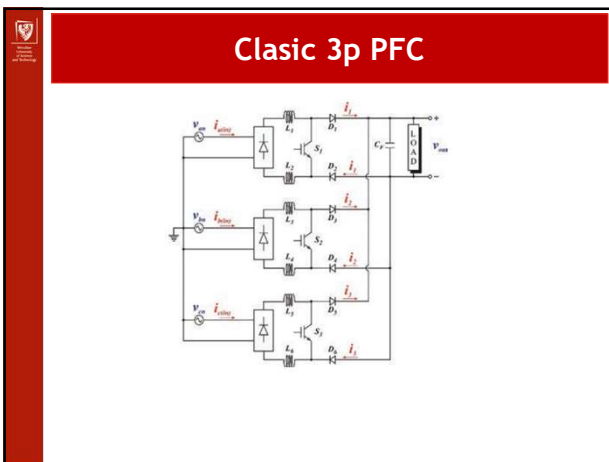


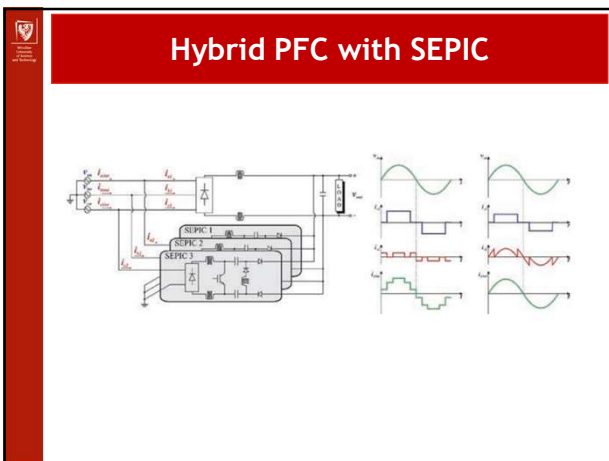


Hybrid PFC with BOOST

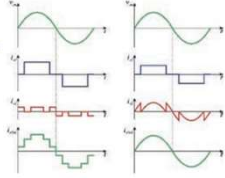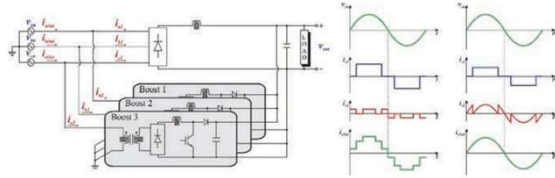


Hybrid PFC with BOOST+SEPIC

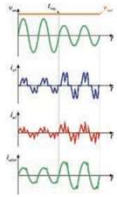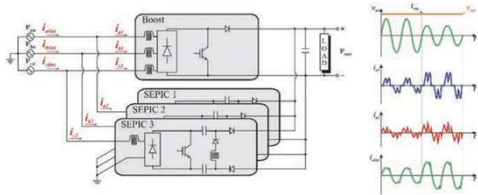


Bidirectional converters buck / boost

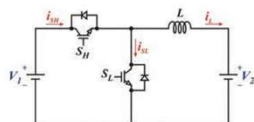


Bidirectional converters

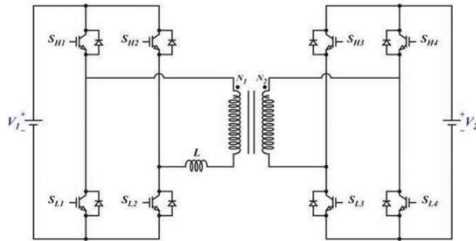

Interleaving

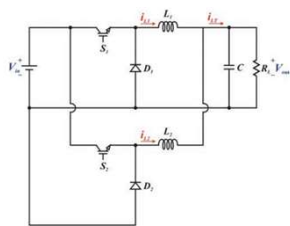

Interleaving

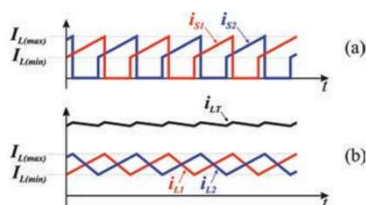

Converters - problems to overcome

High frequency (10-200kHz-2MHz) and short switching times (10-200ns):


- fast diodes and transistors
- distortions - noises
- voltage spikes
- parasitic capacitances (resonances)
- skin effect

Additional reference:

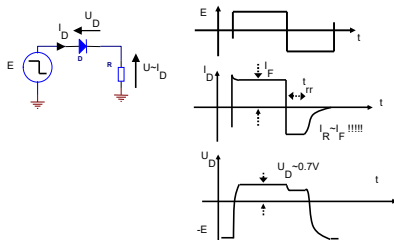I. Pressman, Switching Power Supply Design 3/e, McGraw-Hill Education Ltd.



Dynamic model of diode recovery time t_{rr}



Same diode comparison „oscilloscope show”

Symbol	U_{AKV} [V]	I_A [A]	U_F at I_F [V]	I_F [A]	U_{RM} at I_{RM} [V]	I_{RM} [A]	t_{rr} [ns]	$C(pF)$ at U_{AKV}	zastosowanie
1N4002	100	50	0.5	1	2.3	25	3500	15	Dioda prostownicza 1A
1N4007	1000	50	0.5	1	2.3	25	5000	15	Dioda prostownicza 1A - 1000V
RA159	1000	5	1.3	1	1.8	20	500	12/4V	Szybka prostownicza
1N4148	75	250	1	0.1		4A/1ms	4	0.8	Szybka przełączna
1N5819	40	100	0.4	1	1.2	25	7	40	Prostownicza Schottky
BAT 43	30	100	0.3	0.002	1	0.2	5	5	Schottky (m. moc)
DSEF12-12A	1200	100	2.7	15		90	40	7	Szybka, wykonalnicowa, mocyschottky
SDT06S60 Silicon-carbide	600	200	1.7	6		21.5	00	15	Szybka, wykonalnicowa, mocys



Sam diode parameters cont.

Symbol	U_F @ I_F [V] [A]	U_F [V] @ $I_F=1mA$	t_r [ns]	IR [μA]	
1N4002 (prostownicza 100V)	0.9	1	0.5	3500	50
1N4007 (prostownicza 1kV)	0.9	1	0.5	5000	50
BA159 (szybka 1kV)	1.3	1	0.47	500	5
1N4148 (przełączająca)	1	0.1	0.55	4	25nA
1N5819 (Schottky 1A)	0.4	1	0.2	7	1000
BAT43 (Schottky 0.2A)	0.3	0.2	0.25	5	100
DSEP12-12A (Schottky power, trr=40ns)	2.7	15	0.7	40	200
DT06S60 (SiC zero trr)	1.7	6	0.4	000 !!	100
LED IR			0.9		
LED R G Y O			1.3 + 1.6		
LED Blue & White			3.6		



Summary

Advantages:

- High efficiency
- Small dimensions

Drawbacks:

- Worse line and load regulation
- Interferences
- More expensive

Capacitive converters (charge pump) - for self studies (n.ICL7660)





Test problems

- Sketch a simplified model of a converter and derive the formula for the output voltage for: - a step-down converter (buck) - a step-up converter (boost) - an inverter (buck-boost).
- List the advantages and disadvantages of DC-DC converters.