




Wrocław University of Technology



Active filters




Wrocław University of Technology

Active filters

Electronic filters are circuits with signal processing functions, they remove unwanted frequency to enhance wanted ones.

Electronic filters can be:

- passive or active (RLC (SAW -surface acoustic wave) OR with active elements e.g. OpAmp)
- analog or digital (Signal Processing) or switched capacitor



Wrocław University of Technology

Active filters

Types of active filters:

Due to the way filters operate, the active filters can be classified as :

- continuous time filters
- switched capacitor filters

Frequency specification:

- high-pass,
- low-pass,
- band-pass,
- band-stop (band-rejection; notch),
- all-pass (usually specific phase transmission)

Wrocław University of Technology

Active filters - shape of transfer function

- Chebyshev (I or II kind)
- Elliptic (Cauer)
- Bessel (Thompson)
- Butterworth - Thompson

Wrocław University of Technology

Active filters realization


Active filters can be realized as:


- continuous time filters - analog filters
- switched capacitor filters


Wrocław University of Technology


Low-Pass filter

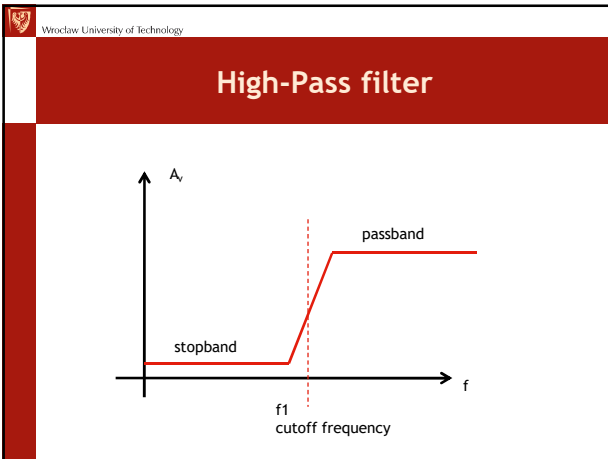
The graph shows the magnitude response A_v versus frequency f . The passband is the region where the magnitude is constant. The stopband is the region where the magnitude is low. The cutoff frequency f_c is the frequency at which the magnitude begins to drop.




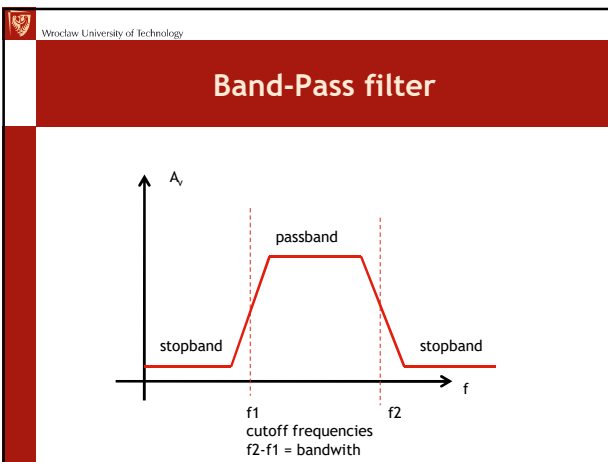

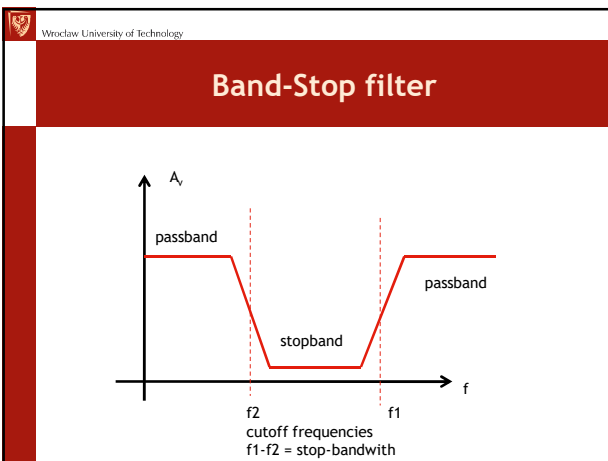

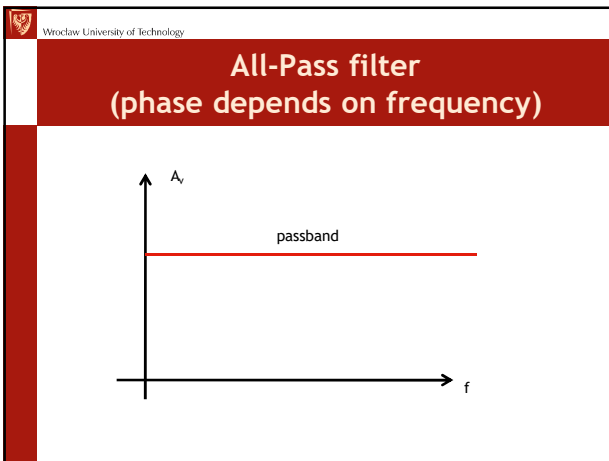

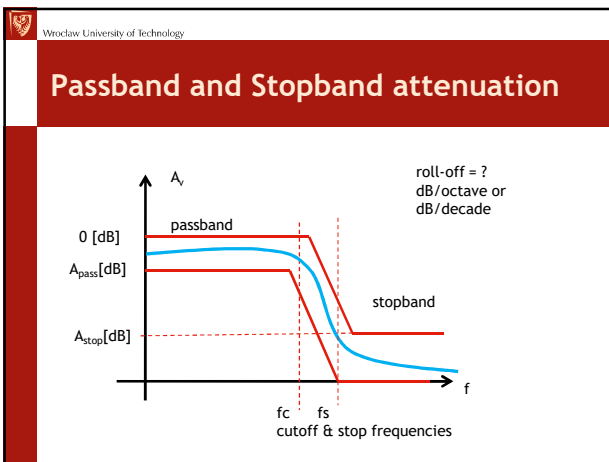

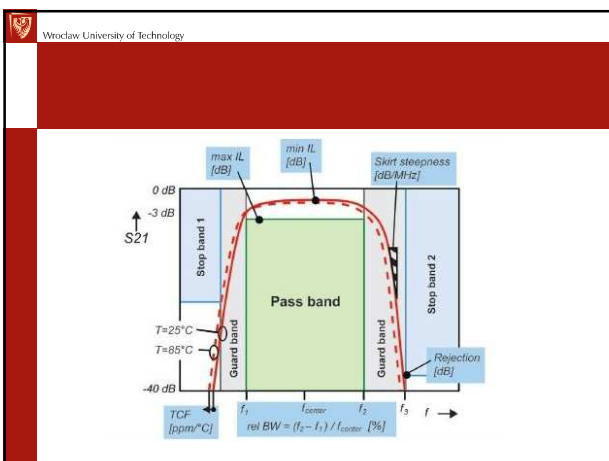

Wrocław University of Technology

Order of a filter

$$H(s) = \frac{U_{out}(s)}{U_{in}(s)} = \frac{a_m s^m + a_{m-1} s^{m-1} + \dots + a_0}{b_n s^n + b_{n-1} s^{n-1} + \dots + b_0} = \frac{a_m \prod_i (s - z_i)}{b_n \prod_j (s - p_j)}$$

n = number of capacitors and inductances (LC - filter)
 n = number of capacitors (RC - filters)

Wrocław University of Technology


Butterworth approximation pass-band max flatness


max flatness of pass-band
 Roll-off = 20*n dB/decade
 Roll-off = 6*n dB/octave
-for low & high -pass
-1/2 for stop & pass-band
 Phase/impulse response = acceptable


Wrocław University of Technology


Chebyshev (I) approximation pass-band ripples

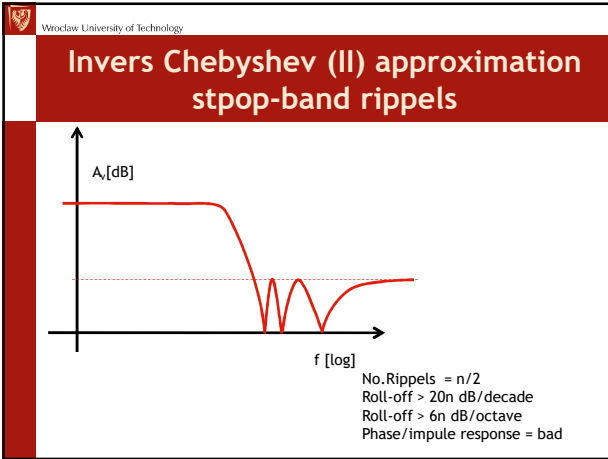No. Ripples = n/2
 Roll-off > 20n dB/decade
 Roll-off > 6n dB/octave
 Phase/impulse response = bad



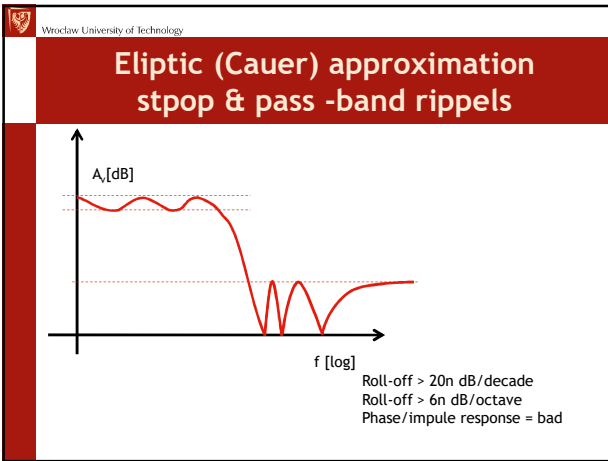

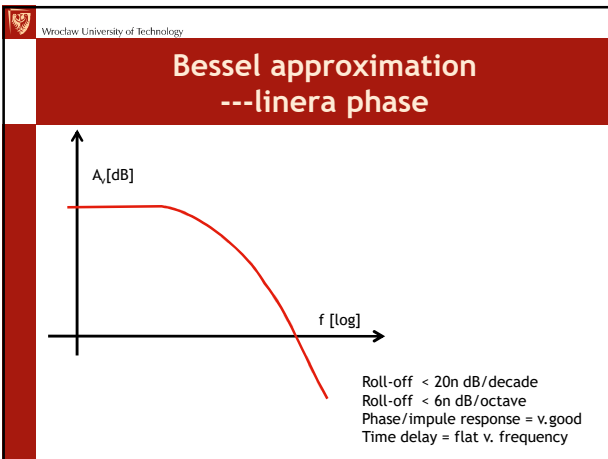


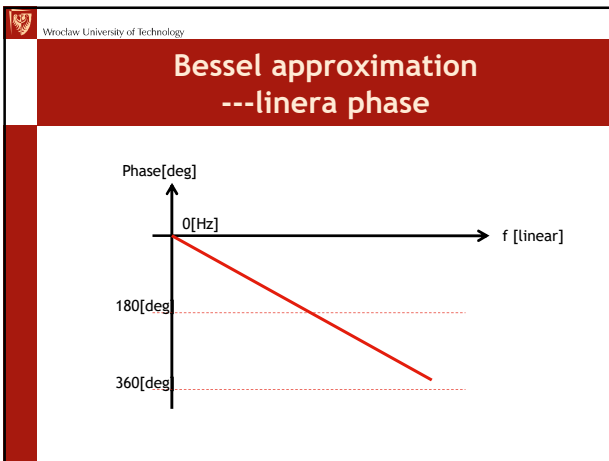



Wroclaw University of Technology


6th order filter attenuation


Type	fc [dB]	2fc [dB]
Bessel	3	14
Butteworth	3	36
Chebyshev	3	63
Invers Chebyshev (II)	3	63
elliptic	3	93

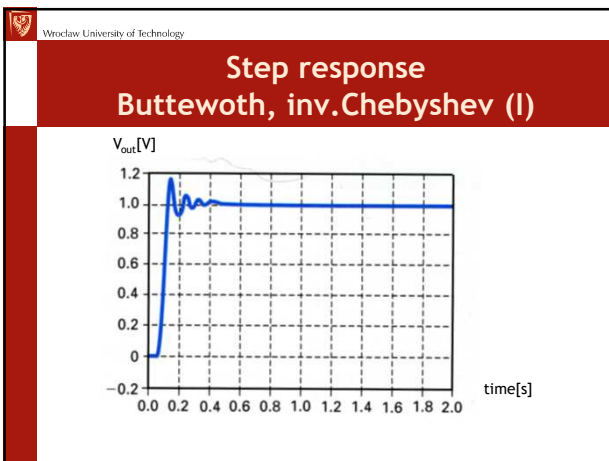


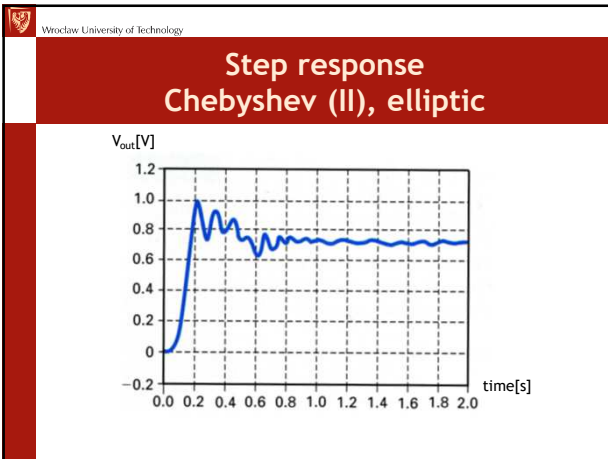


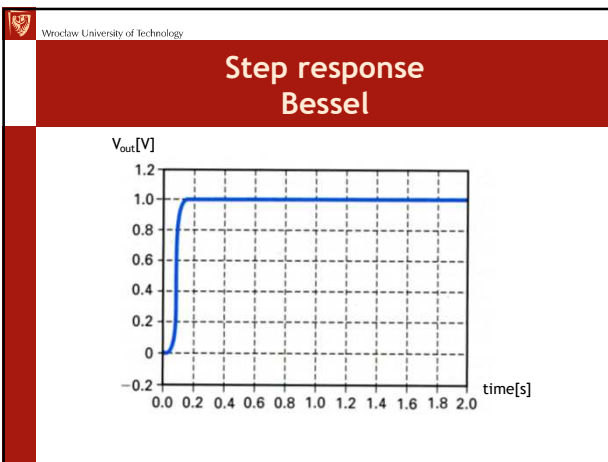


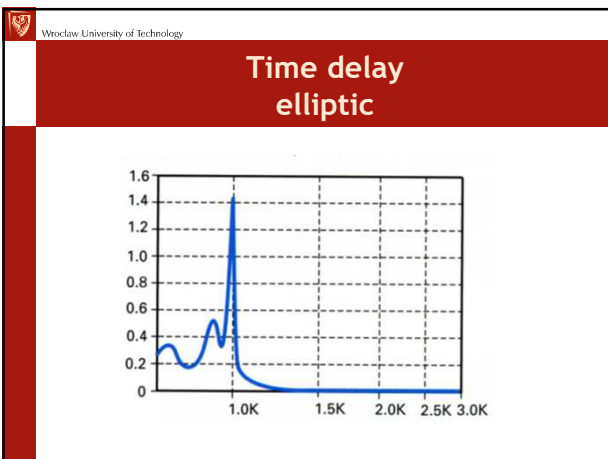


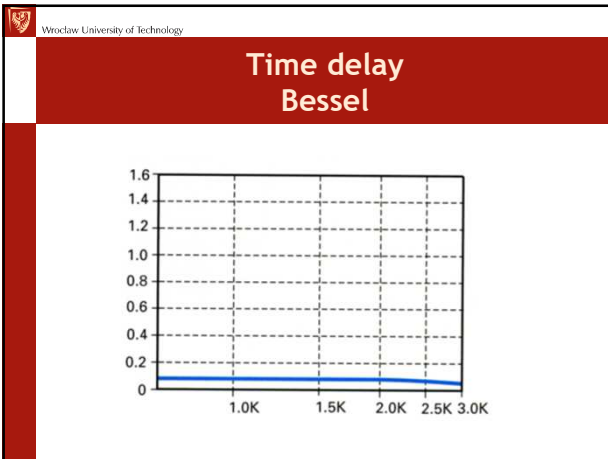


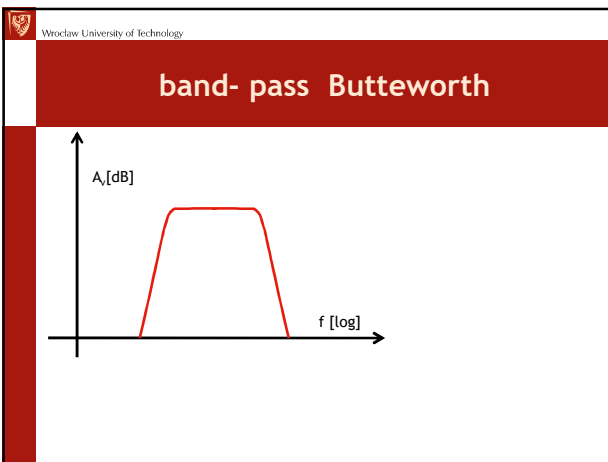


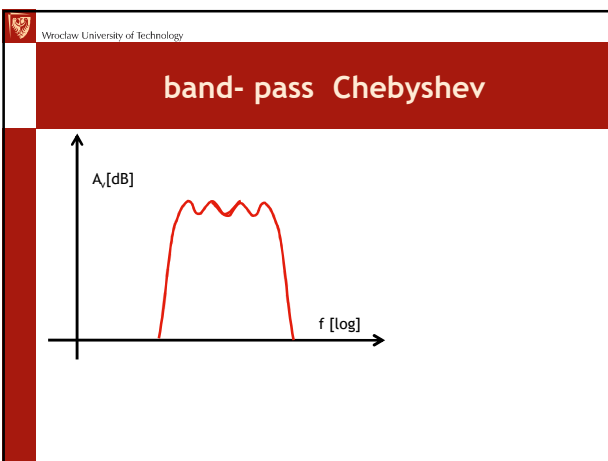


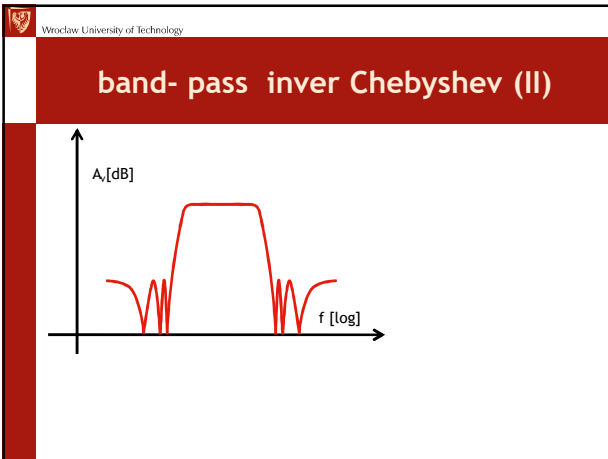


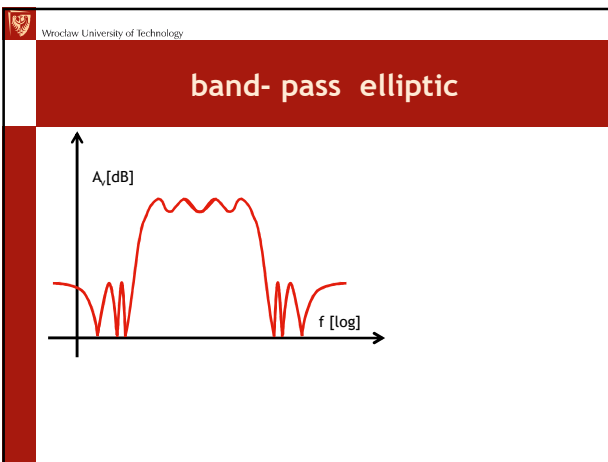


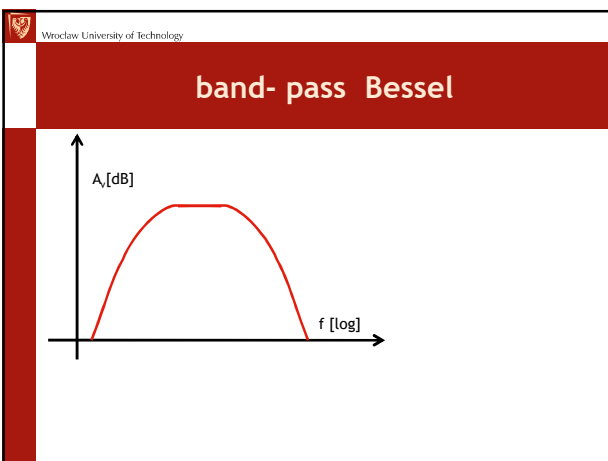


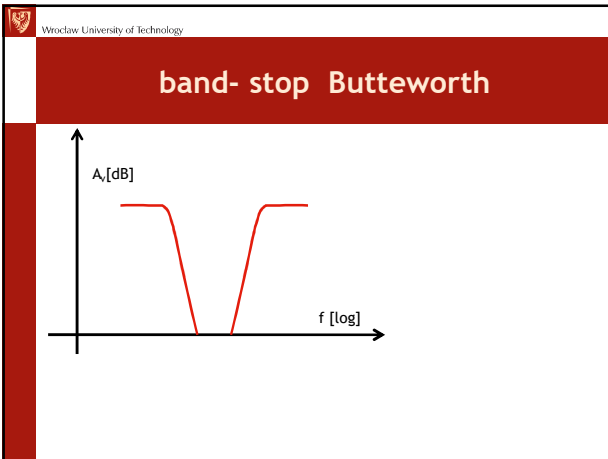

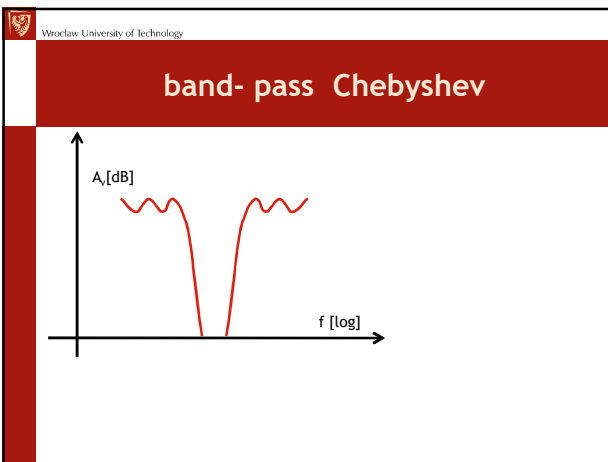

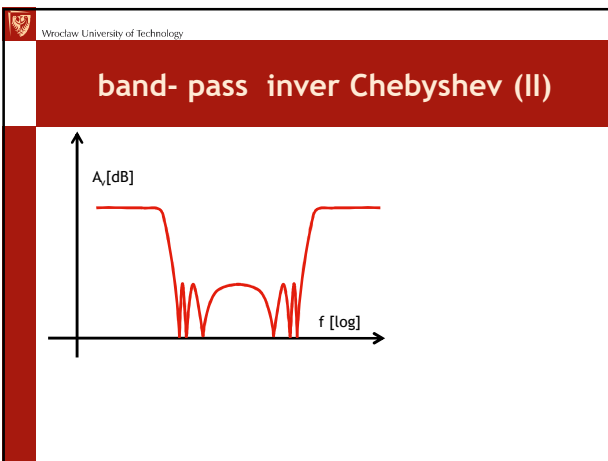

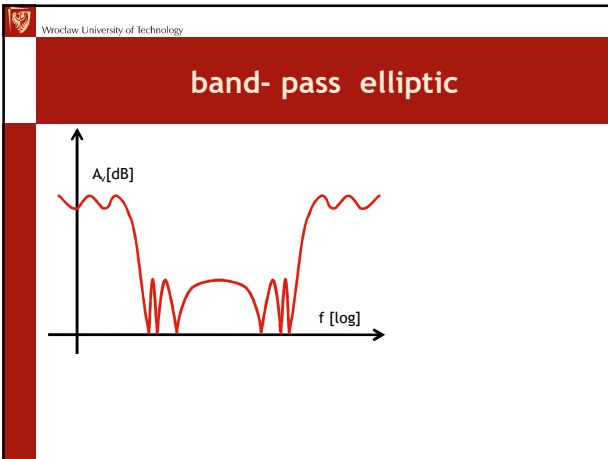

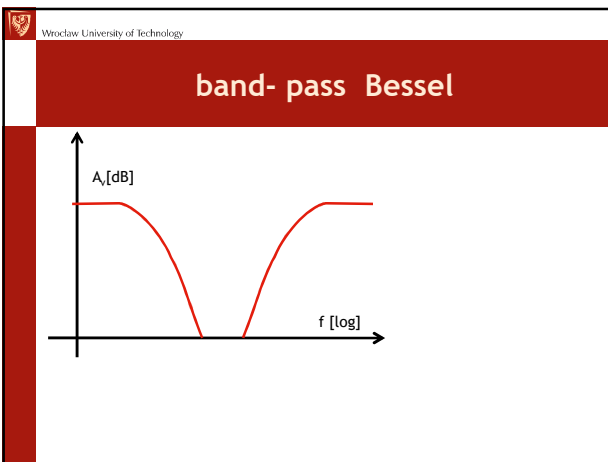


Wrocław University of Technology


Filter approximation general features

Type	passband	stopband	Roll-off	Step response
Bessel	flat	monotonic	poor	best
Butterworth	flat	monotonic	good	good
Chebyshev	rippled	monotonic	v. good	poor
ln.Chebyshev (II)	flat	rippled	best	poor
Elliptic (Cauer)	rippled	rippled	best	poor



Wrocław University of Technology

Active filter implementation



Wrocław University of Technology

Active filters - introduction


Transmittance:

$$H(s) = \frac{U_{out}(s)}{U_{in}(s)} = \frac{a_m s^m + a_{m-1} s^{m-1} + \dots + a_0}{b_n s^n + b_{n-1} s^{n-1} + \dots + b_0} = \frac{a_m \prod_i (s - z_i)}{b_n \prod_j (s - p_j)}$$

a_i, b_j - real numbers
 z_i, p_j - zeros and poles of transmittance

$$H(s) = |H(\omega)| \exp[j\varphi(\omega)]$$

$|H(s)|$ - amplitude transmittance
 $\varphi(s)$ - phase transmittance



Wrocław University of Technology

Active filters - introduction c.d.

Transmittance factorization:

$$H(s) = \frac{N(s)}{D(s)} = \prod_k H_k(s) = \prod_k \frac{N_k(s)}{M_k(s)}$$

Degree of $N_k(s) \leq$ degree of $M_k(s) \leq 2$

For $M_k(s) = 2$ biquadratic section:

$$H_k(s) = \frac{a_2 s^2 + a_1 s + a_0}{s^2 + b_1 s + b_0} = \frac{N_k(s)}{s^2 + b_1 s + b_0}$$

Wrocław University of Technology

Active filters - intro

Biquadratic section can be expressed as:

$$H_k(s) = \frac{N_k(s)}{s^2 + \frac{\omega_0}{Q}s + \omega_0^2} = \frac{N_k(s)}{(s-p_1)(s-p_2)}$$

where: p_1, p_2 - poles of the transmittance

For quality $Q > 1/2$ poles are complex numbers

$$p_{1,2} = -\frac{\omega_0}{2Q} + j\frac{\omega_0}{2Q}\sqrt{4Q^2 - 1} = \sigma_p \pm j\omega_p$$

Wrocław University of Technology

Active filters - intro

Real and imaginary parts are:

$$\sigma_p = -\frac{\omega_0}{2Q} \quad \omega_p = \omega_0 \sqrt{1 - \frac{1}{4Q^2}}$$

Specific frequency and quality are

$$\omega_0 = \sqrt{\sigma_p^2 + \omega_p^2} \quad Q = \frac{\sqrt{\sigma_p^2 + \omega_p^2}}{2|\sigma_p|} = \frac{\omega_0}{2|\sigma_p|}$$

Damping factor:

$$\alpha = \frac{1}{2Q}$$

Wrocław University of Technology

Active filters - intro

When denominator is written in the form:

$$s^2 + b_1s + b_0 = s^2 + \frac{\omega_0}{Q}s + \omega_0^2$$

Parameters Q (quality) and ω_0 (characteristic frequency)

$$Q = \frac{\sqrt{b_0}}{b_1}$$

$$\omega_0 = \sqrt{b_0}$$

b_0, b_1 - real coefficients

Wrocław University of Technology

Interpretation of Q and ω_0

$$H_{LP}(s) = H_0 \frac{\omega_0^2}{s^2 + \frac{\omega_0}{Q}s + \omega_0^2}$$

Wrocław University of Technology

Interpretation of Q and ω_0

$$H_{HP}(s) = H_0 \frac{s^2}{s^2 + \frac{\omega_0}{Q}s + \omega_0^2}$$

Wrocław University of Technology

Interpretation of Q and ω_0

$$H_{BP}(s) = H_0 \frac{\omega_0 s}{s^2 + \frac{\omega_0}{Q}s + \omega_0^2}$$

$$Q = \frac{\omega_0}{\Delta\omega} = \frac{\omega_0}{\omega_{gH} - \omega_{gL}}$$

Wrocław University of Technology

Interpretation of Q and ω_0

$$H_{BR}(s) = H_0 \frac{s^2 + \frac{\omega_z}{Q_z} s + \omega_z^2}{s^2 + \frac{\omega_0}{Q} s + \omega_0^2}$$

Wrocław University of Technology

Filtry aktywne - wprowadzenie

$Q_z = \infty$ - elliptic filter with transfer function:

$$H_{BR}(s) = H_0 \frac{\omega_z^2}{\omega_0^2} \frac{\frac{s^2}{\omega_z^2} + 1}{\frac{s^2}{\omega_0^2} + \frac{s}{Q\omega_0} + 1}$$

Wrocław University of Technology

Filters transformation

$S = \frac{s}{\omega_0}$ $H_i(S) = \frac{Ku}{A_i S^2 + B_i S + 1}$

Low pass filter

Wrocław University of Technology

LOW → HIGH pass

$S \rightarrow \frac{1}{S}$ High pass filter

Wrocław University of Technology

LOW → BAND PASS

$S \rightarrow \frac{1}{\Delta\Omega} \left(S + \frac{1}{S} \right)$ Band pass filter

Wrocław University of Technology

LOW → BAND STOP

$S \rightarrow \frac{\Delta\Omega}{\left(S + \frac{1}{S} \right)}$

Wrocław University of Technology

Active filters - factorization

Transmittance factorization:

$$H(s) = \frac{N(s)}{D(s)} = \prod_k H_k(s) = \prod_k \frac{N_k(s)}{M_k(s)}$$

order of $N_k(s) \leq$ order of $M_k(s) \leq 2$

For order $M_k(s) = 2$ biquadratic section, or =1 first order section:

$$H_k(s) = \frac{a_2 s^2 + a_1 s + a_0}{s^2 + b_1 s + b_0} = \frac{N_k(s)}{s^2 + b_1 s + b_0} = \frac{N_k(s)}{a_1 s^2 + b_1 s + 1}$$

OR

$$H_k(s) = \frac{a_1 s + a_0}{b_1 s + b_0}$$

Wrocław University of Technology

N	i	a_i	b_i	f_{ci}/f_c	Q_i
<i>Chebyshev filters, 0.5 dB ripple</i>					
1	1	1.0000	0.0000	1.000	-
2	1	1.3634	1.3827	1.000	0.86
3	1	1.8636	0.0000	0.517	-
3	2	0.6902	1.1931	1.335	1.71
4	1	2.6787	3.4341	0.538	0.71
4	2	0.3648	1.1500	1.419	2.91
5	1	2.9235	0.0000	0.842	-
5	2	1.4025	2.5334	0.881	1.18
5	3	0.2290	1.0833	1.480	4.54
6	1	3.8645	6.9797	0.366	0.68
6	2	0.7828	1.8573	1.078	1.81
6	3	0.1589	1.0711	1.495	6.51
7	1	4.0211	0.0000	0.249	-
7	2	1.8729	4.1795	0.645	1.09
7	3	0.4861	1.5676	1.208	2.58
7	4	0.1156	1.0443	1.517	8.84
8	1	5.1117	11.9607	0.276	0.68
8	2	1.0639	2.5965	0.844	1.61
8	3	0.5439	1.4206	1.284	3.47
8	4	0.0885	1.0407	1.521	11.53
9	1	5.1318	0.0000	0.195	-
9	2	2.4783	6.6307	0.506	1.06
9	3	0.6839	2.2008	0.989	2.21
9	4	0.2559	1.3153	1.344	4.48
9	5	0.0695	1.0272	1.532	14.58
10	1	6.3648	18.3695	0.222	0.67
10	2	1.3582	4.3453	0.689	1.53
10	3	0.4822	1.9440	1.091	2.89
10	4	0.1094	1.2520	1.381	5.61
10	5	0.0563	1.0763	1.533	17.90

Wrocław University of Technology

1st order high pass filter


$$A_v = \frac{U_{out}}{U_{in}} = \frac{R}{R + \frac{1}{sC}} = \frac{sCR}{sCR + 1}$$

$$= \frac{R}{R + \frac{1}{j\omega C}} = \frac{1}{1 + \frac{1}{j\omega CR}} = \frac{1}{1 + \frac{1}{j\omega RC}} = \frac{1}{1 + \frac{\omega_1}{j\omega}} = \frac{1}{1 + \frac{j}{jf_1}}$$

$f_1 = \frac{1}{2\pi RC}$

Wrocław University of Technology

1st order low pass filter

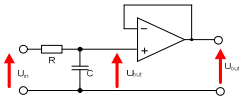


$$A_v = \frac{U_{out}}{U_{in}} = \frac{1/sC}{R + 1/sC} = \frac{1}{1 + jsCR} = \frac{1}{1 + j\omega \frac{1}{\omega_c}} = \frac{1}{1 + j \frac{f}{f_c}} = \frac{1}{1 + j\omega \frac{1}{2\pi RC}}$$

$f_c = \frac{1}{2\pi RC}$

Wrocław University of Technology

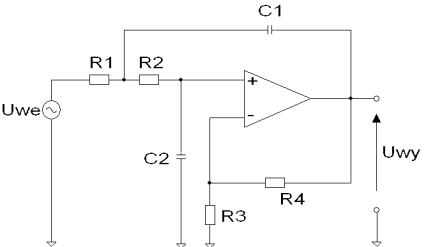Active filters Sallen - Key low pass implementation



Wrocław University of Technology


Sallen - Key low pass implementation

Transmittance:

$$H_{LP}(s) = \frac{U_{wy}(s)}{U_{we}(s)} = \frac{\frac{1 + R_4/R_3}{R_1 R_2 C_1 C_2}}{s^2 + \left(\frac{1}{R_1 C_1} + \frac{1}{R_2 C_1} + \frac{R_4/R_3}{R_2 C_2} \right) s + \frac{1}{R_1 R_2 C_1 C_2}}$$

where:

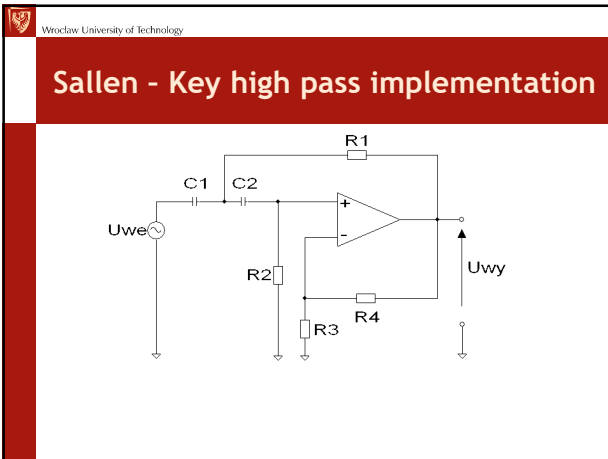
$$\omega_0 = \frac{1}{\sqrt{R_1 R_2 C_1 C_2}} \quad Q = \frac{1}{\left(\frac{1}{R_1 C_1} + \frac{1}{R_2 C_1} + \frac{R_4/R_3}{R_2 C_2} \right)}$$



Wrocław University of Technology

Sallen - Key high pass implementation
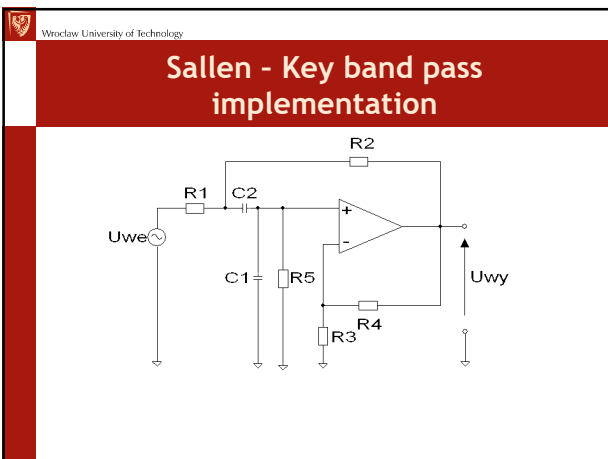
$$H_{HP}(s) = \frac{U_{out}(s)}{U_{in}(s)} = \frac{(1 + R_4/R_3)s^2}{s^2 + \left(\frac{1}{R_2C_1} + \frac{1}{R_2C_2} + \frac{R_4/R_3}{R_1C_1}\right)s + \frac{1}{R_1R_2C_1C_2}}$$



Wrocław University of Technology

Sallen - Key band pass implementation

$$H_{BP}(s) = \frac{U_{out}(s)}{U_{in}(s)} = \frac{\frac{1+R_4/R_3}{R_2 C_1} s}{s^2 + \left(\frac{1}{R_1 C_1} + \frac{1}{R_3 C_2} + \frac{1}{R_3 C_1} + \frac{R_4/R_3}{R_2 C_1} \right) s + \frac{R_1+R_2}{R_1 R_2 R_3 C_1 C_2}}$$

$$\omega_0 = \sqrt{\frac{R_1+R_2}{R_1 R_2 R_3 C_1 C_2}} \quad Q = \frac{\sqrt{\frac{R_1+R_2}{R_1 R_2 R_3 C_1 C_2}}}{\left(\frac{1}{R_1 C_1} + \frac{1}{R_3 C_2} + \frac{1}{R_3 C_1} + \frac{R_4/R_3}{R_2 C_1} \right)}$$

Wrocław University of Technology


LOW PASS multiple negative feedback

Wrocław University of Technology

LOW PASS multiple negative feedback

$$H_{LP}(s) = \frac{U_{wy}(s)}{U_{we}(s)} = \frac{-\frac{R_2/R_1}{R_2 R_3 C_1 C_2}}{s^2 + \frac{s}{C_1} \left(\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} \right) + \frac{1}{R_2 R_3 C_1 C_2}}$$
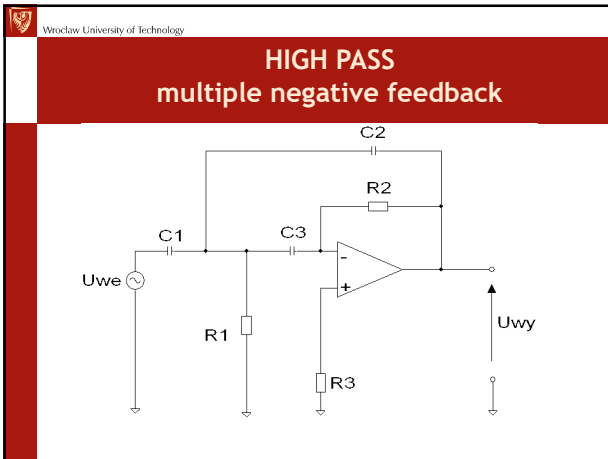
$$\omega_0 = \frac{1}{\sqrt{R_2 R_3 C_1 C_2}} \quad Q = \left[\sqrt{C_2} \left(\sqrt{\frac{R_3}{R_2}} + \sqrt{\frac{R_2}{R_3}} + \frac{\sqrt{R_2 R_3}}{R_1} \right) \right]^{-1}$$



Wrocław University of Technology


HIGH PASS multiple negative feedback

Transfer function:

$$H_{HP}(s) = \frac{U_{out}(s)}{U_{in}(s)} = \frac{-C_1/C_2 s^2}{s^2 + \frac{s}{R_2} \left(\frac{C_1}{C_2 C_3} + \frac{1}{C_2} + \frac{1}{C_3} \right) + \frac{1}{R_1 R_2 C_2 C_3}}$$

where:
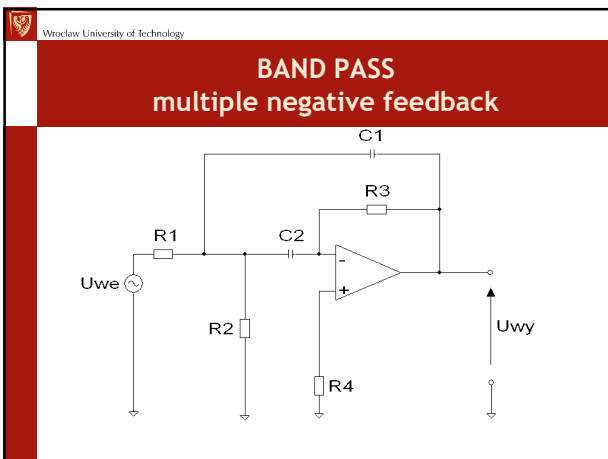
$$\omega_0 = \frac{1}{\sqrt{R_1 R_2 C_2 C_3}} \quad Q = \left[\sqrt{\frac{R_1}{R_2}} \left(\frac{C_1}{\sqrt{C_2 C_3}} + \sqrt{\frac{C_3}{C_2}} + \sqrt{\frac{C_2}{C_3}} \right) \right]^{-1}$$




Wrocław University of Technology

BAND PASS multiple negative feedback


$$H_{BP}(s) = \frac{U_{out}(s)}{U_{in}(s)} = \frac{-\frac{s}{R_1 C_1}}{s^2 + s \left(\frac{1}{R_3 C_1} + \frac{1}{R_3 C_2} \right) + \frac{R_1 + R_2}{R_1 R_2 R_3 C_1 C_2}}$$

Wrocław University of Technology

LC resonant circuit (serial)

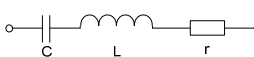


$$f_0 = \frac{1}{2\pi\sqrt{LC}}$$

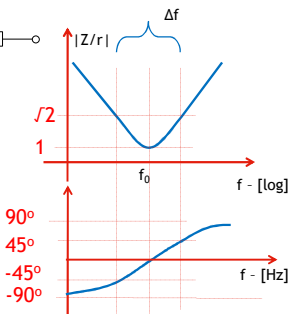
$$Q = \frac{f_0}{\Delta f} = \frac{\omega_0 L}{r}$$


Wrocław University of Technology

LC resonant circuit (paralel)

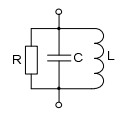

$$f_0 = \frac{1}{2\pi\sqrt{LC}}$$
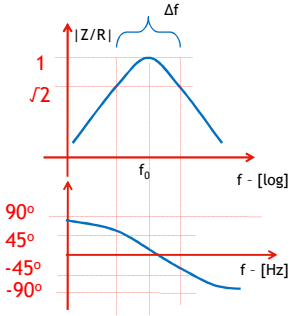
$$Q = \frac{f_0}{\Delta f} = \frac{R}{1/\omega_0 C}$$


Wrocław University of Technology

Q-factor definition

$$Q = \frac{f_0}{\Delta f} = \frac{\omega_0}{\omega_{gH} - \omega_{gL}}$$

Wrocław University of Technology

Band pass

Wrocław University of Technology

BAND STOP

Wrocław University of Technology

Filtiry aktywne - wielokrotne, ujemne sprzężenie zwrotne

Transmitancja filtru:

$$H_{BR}(s) = -\left(\frac{R_6}{R_{51}} H_{BP}(s) + \frac{R_6}{R_{52}}\right)$$

Przy częstotliwości środkowej $\omega = \omega_0$

$$\left. \begin{aligned} |H_{BP}(\omega = \omega_0)| &= 1 \frac{V}{V} \\ \phi(\omega = \omega_0) &= \pi \end{aligned} \right\} H_{BP} = -1 \frac{V}{V}$$

Dla: $R_{51} = R_{52} = R$

$$H_{BR}(\omega = \omega_0) = 0$$

Wrocław University of Technology

BAND STOP (NOTCH FILTER)

$C1 = C2 = C$
 $R4 = R3 = R$
 $R2 = R1 = R$
 $f_0 = 1/2\pi RC$

$f_N = \frac{1}{4\pi RC}$

Wrocław University of Technology

ALL PASS FILTER

$$H(s) = \frac{N(s)}{D(s)} = \prod_k H_k(s)$$

$$H_k(s) = \frac{s^2 - a_1s + a_0}{s^2 + b_1s + b_0}$$

$$|H_k(s)| = 1$$

Wrocław University of Technology

phase shifter (all pass filter of 1st order)

$$\frac{V_{out}}{V_{in}} = -\frac{1 - sCR_3}{1 + sCR_3}$$

Wrocław University of Technology

Biquadratic monolithic universal filter UF42 by TI (state variable filter)

Note: If $R_1 = 50k\Omega$, the external gain-setting resistor can be eliminated by connecting V_{ref} to pin 2.

Pin numbers are for DIP package. SOIC-16 pinout.

Wrocław University of Technology

Switched capacitor filter

$$I = \frac{U}{R}$$

$$I = \frac{dQ}{dt} = \frac{d(UC_s)}{dt} = \frac{UC_s}{T_s} = UC_s f_s$$

$$R = \frac{1}{C_s f_s}$$

Wrocław University of Technology

C switched filter

Transfer function

$$\frac{U_{wy}}{U_{we}} = -\frac{1}{\omega \tau}$$

Where: $\tau = RC$

Wrocław University of Technology

C switched filters

Transfer function

$$\frac{U_{wy}}{U_{we}} = -\frac{1}{\omega \tau}$$

$$\tau = CR_{ZAST} = \frac{C}{f_s C_s} = \frac{\eta}{2\pi f_s}$$

$$\frac{\eta}{2\pi} = \frac{C}{C_s}$$

$$\eta = (50 \div 200)$$

Wrocław University of Technology

C switched integrator

Wrocław University of Technology

C switched integrator

$$\frac{U_{wy}}{U_{we}} = \frac{f_s C_S}{sC} = \frac{1}{s}$$

$$\tau = CR_{ZAST} = \frac{C}{f_s C_S} = \frac{\eta}{2\pi f_s}$$

Wrocław University of Technology

4 biquadratic filters with switched capacitors in LTC1064 by LT

Wrocław University of Technology

Problems

1. Q-factor of a bandpass filter ?
2. Types of filters (band stop, b. pass etc.)
3. Types of frequency response of filters (Bessel,)
4. Biquadratic filter (biquad section)
5. Active filters topologies (Sallen - Key, multiple feedback, state variable, C-switching)
