

3. Operational amplifier - inverting amplifier, non-inverting amplifier, combiner, differential circuit

1) Task

In the amplifier circuit from Fig.1 (inverting amplifier) assuming ideal OA parameters should be:

- a) Determine the voltage transmittance of the system;
- b) Estimate the voltage gain of the circuit when $R_1 = 10 \text{ k}\Omega$, $R_2 = 20 \text{ k}\Omega$.

2) Task

Determine A_V , R_{in} , R_{out} , f_g of the amplifier circuit from Fig.1 considering the finite voltage gain of OA. For calculations, assume $R_1 = 15 \text{ k}\Omega$, $R_2 = 15 \text{ k}\Omega$ and OA with parameters: $A_{VOL} = 10^5 \text{ V/V}$, $f_{(pl)} = 10 \text{ Hz}$, $f_T = 1 \text{ MHz}$, $R_{ins} = 10^9$, $R_{(inr)} = 10^{(6)}$, $R_{(outWO)} = 75 \Omega$.

3) Task

In the amplifier circuit from Fig.2 assuming ideal OA parameters and $R_g = 500 \Omega$, $R_L = 10 \text{ k}\Omega$ should:

- a) Select R_1 , R_2 so that $A_V = -6 \text{ V/V}$;
- b) Select R_d to compensate for the input polarization current.

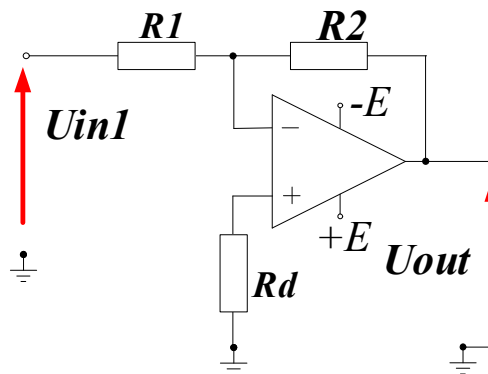


Fig.1 . Inverting amplifier

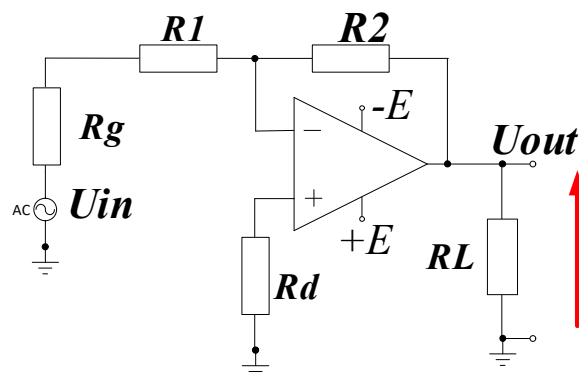


Fig.2 . Inverting amplifier

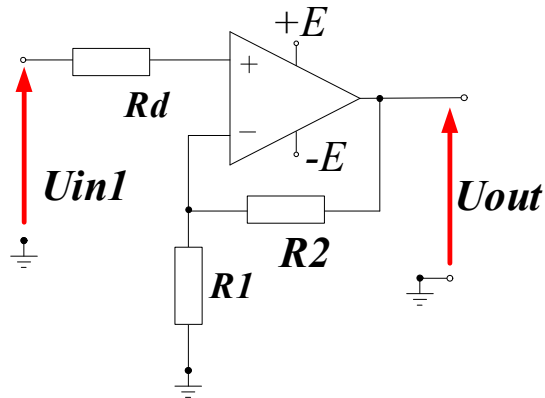


Fig.3 . Non-inverting amplifier

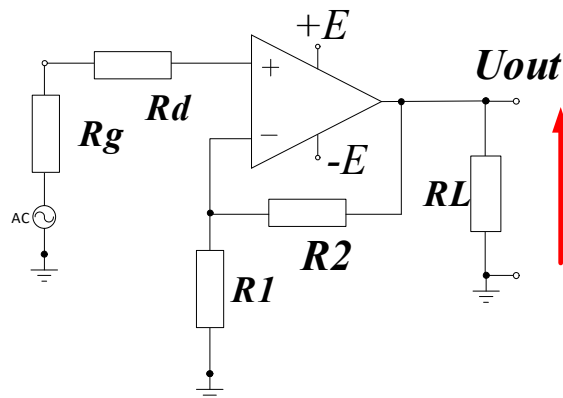


Fig.4 . Non-inverting amplifier

4) Task

In the amplifier circuit from Fig.3 (non-inverting amplifier) assuming ideal OA parameters should be:

- a) Determine the voltage transmittance of the system;
- b) Estimate the voltage gain of the system when $R_1 = 10 \text{ k}\Omega$, $R_2 = 20 \text{ k}\Omega$;
- c) Analyze the possibility of obtaining voltage gain $A_V = 1$.

5) Task

Determine A_V , R_{in} , R_{out} , f_g of the amplifier circuit from Fig.3 considering the finite voltage gain of WO. For calculations, assume $R_1 = 15 \text{ k}\Omega$, $R_2 = 15 \text{ k}\Omega$ and OA with parameters: $K_{UR} = 10^5 \text{ V/V}$, $f_{(pl)} = 10 \text{ Hz}$, $f_T = 1 \text{ MHz}$, $R_{ins} = 10^9$, $R_{(inr)} = 10^{(6)}$, $R_{(outWO)} = 75 \Omega$.

6) Task

In the amplifier circuit from Fig.4 assuming ideal OA parameters and $R_G = 500 \Omega$, $R_{(L)} = 10 \text{ k}\Omega$ should:

- a) Select R_1 , R_2 so that $A_V = 4 \text{ V/V}$
- b) Select R_d to compensate for the input polarization current

7) Task

In the amplifier circuit from Fig.5 (differential amplifier) assuming ideal WO parameters should be:

- a) Determine the relationship for the output voltage U_{OUT} as a function of the input voltages U_{IN1} , U_{IN2} , and U_{IN3} ,
- b) Determine the relationship on U_{OUT} when $R_3 = R_{(1)}$ and $R_4 = R_{(2)}$.

8) Task

In the circuit of the amplifier in Fig.5 (differential amplifier) assuming ideal OA parameters should be:

- a) Estimate the output voltage U_{OUT} when $U_{IN1} = 1 \text{ V}$, $U_{IN2} = 5 \text{ V}$, $U_{IN3} = 5 \text{ V}$, $R_1 = 10 \text{ k}\Omega$, $R_{(2)} = 50 \text{ k}\Omega$, $R_{(3)} = 20 \text{ k}\Omega$, $R_{(4)} = 10 \text{ k}\Omega$;
- b) Select the resistance values in the circuit so that it realizes the function $U_{OUT} = -5 U_{IN1} + 6 U_{IN2}$ ($U_{IN3} = 0 \text{ V}$)

c)

9) Task

In the amplifier circuit from Fig.5 (differential amplifier) assuming ideal WO parameters should be:

- a) Determine the condition for minimizing the effect of input polarization current;
- b) Determine the inunction resistance of the individual injunctions of the system.
- c)

10) Task (exam task - example)

In the amplifier circuit from Fig.5 (r ožnic amplifier) assuming ideal OA parameters and $U_{IN1} = 2 \text{ V}$, $U_{IN2} = 2 \text{ V}$, $U_{IN3} = 2 \text{ V}$, $R_1 = 10 \text{ k}\Omega$, $R_3 = 20 \text{ k}\Omega$, $R_2 = 40 \text{ k}\Omega$, $R_4 = 10 \text{ k}\Omega$, estimate the value of the output voltage U_{OUT} ;

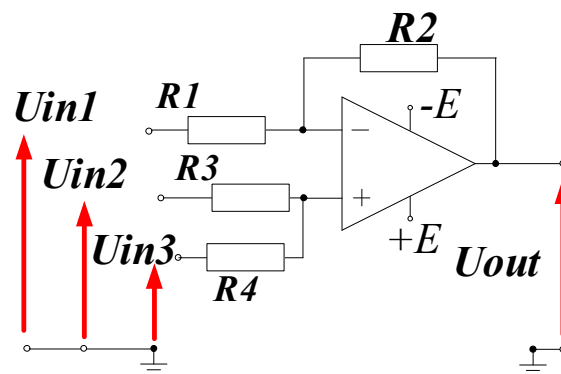


Fig.5 . Differential amplifier

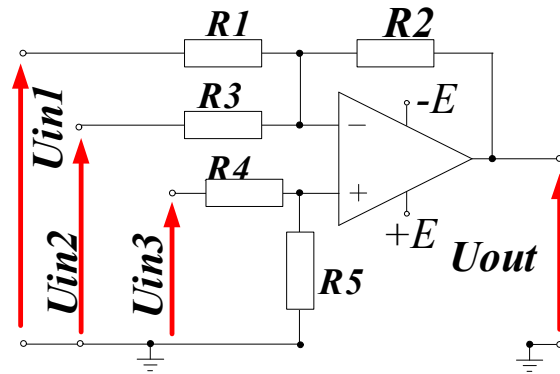


Fig.6 . Level shifting summing amplifier

11) Task

In the amplifier circuit from Fig.6 (combiner) assuming ideal OA parameters, determine the dependence on the output voltage U_{OUT} as a function of the input voltages U_{IN1} , U_{IN2} and U_{IN3} .

12) Task (exam task - example)

In the amplifier circuit from Fig.6 (combiner) assuming ideal OA parameters and $U_{IN1} = 2\text{ V}$, $U_{IN2} = 2\text{ V}$, $U_{IN3} = 2\text{ V}$, $R_1 = 10\text{ k}\Omega$, $R_{(3)} = 20\text{ k}\Omega$, $R_{(2)} = 40\text{ k}\Omega$, $R_{(4)} = 10\text{ k}\Omega$, $R_{(5)} = 10\text{ k}\Omega$ should: Estimate the value of the output voltage U_{OUT} ;

13) Task (exam task - example)

In the amplifier circuit from Fig.6 (combiner) assuming ideal OA parameters, select circuit elements to realize the function:

- a) $U_{OUT} = -(2 U_{IN1} + U_{IN2})$;
- b) $U_{OUT} = -(5 U_{IN1} + 6 U_{IN2})$.