

6 BJ Transistor amplifiers

1) Task

Estimate the operating point of a transistor (I_{CQ} , U_{CEQ}) operating in an amplifier circuit from Figure 1. For calculations, assume: $R_B = 220 \text{ k}\Omega$, $R_C = 1 \text{ k}\Omega$, $R_E = 510 \text{ }\Omega$, $V_{CC} = 10 \text{ V}$, $U_{BE} = 0.65 \text{ V}$, $\beta = 100$.

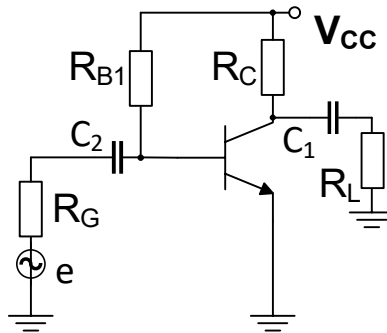


Figure 1 . Common emitter amp.- base polarization.

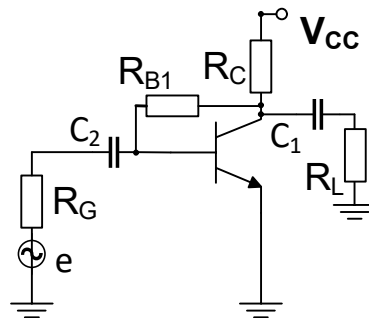


Figure 2 . Common emitter amp. .- base polarization with collector feedback

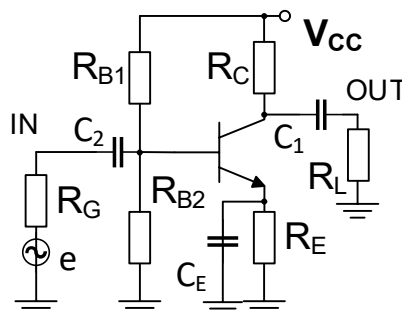


Figure 3 . Common emitter amp. .- potentiometric polarization with emitter feedback

2) Task

Estimate the operating point of a transistor (I_{CQ} , U_{CEQ}) operating in an amplifier circuit from Figure 2. For calculations, assume: $R_B = 133 \text{ k}\Omega$, $R_C = 1.8 \text{ k}\Omega$, $V_{CC} = 10 \text{ V}$, $U_{(BE)} = 0.65 \text{ V}$, $\beta = 100$.

3) Task

Estimate the operating point of a transistor (I_{CQ} , U_{CEQ}) operating in an amplifier circuit from Figure 3. For calculations, assume: $R_{B1} = 15 \text{ k}\Omega$, $R_{B2} = 8.2 \text{ k}\Omega$, $R_C = 820 \Omega$, $R_E = 510 \Omega$, $V_{CC} = 10 \text{ V}$, $U_{EB} = 0.65 \text{ V}$, $\beta = 100$.

4) Task

Estimate the operating point of a transistor (I_{CQ} , U_{CEQ}) operating in an amplifier circuit from Figure 4. For calculations, assume: $R_B = 100 \text{ k}\Omega$, $R_C = 8.2 \text{ k}\Omega$, $R_E = 10 \text{ k}\Omega$, $V_{CC} = \pm 12 \text{ V}$, $U_{EB} = 0.65 \text{ V}$, $\beta = 200$.

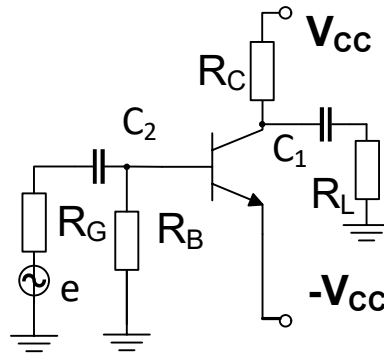


Figure 4. Common emitter amp with negative emitter polarization.

5) Taskk

Estimate the operating points of the transistors (I_{CQ} , U_{CEQ}) operating in the amplifier circuit from Figure 5. For calculations, assume: $R_{C1} = 10 \text{ k}\Omega$, $R_{C2} = 5 \text{ k}\Omega$, $R_{E1} = 5 \text{ k}\Omega$, $R_{E2} = 6.1 \text{ k}\Omega$, $R(F) = 100 \text{ k}\Omega$, $V_{CC} = 18 \text{ V}$, $U_{BE1} = U_{BE2} = 0.65 \text{ V}$, $\beta(1) = \beta(2) = 100$.

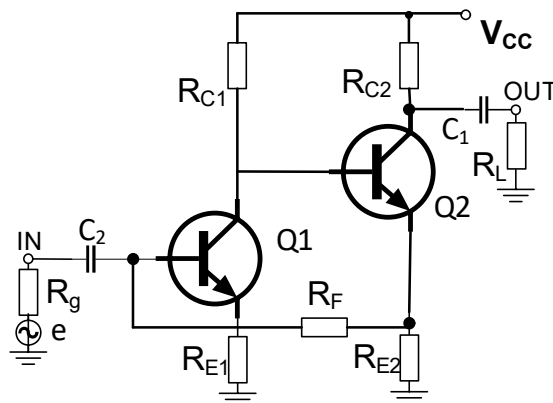


Figure 5. Dual BJT amp with feedback end emitter feedback of Q1

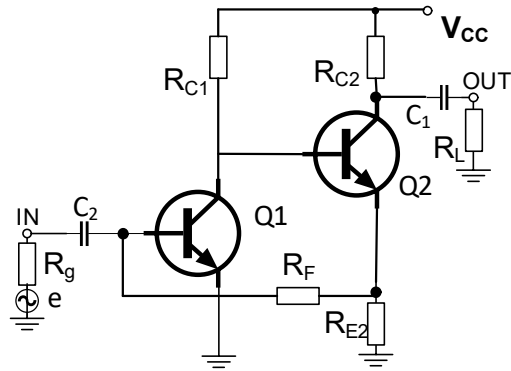


Figure6 . Dual BJT amp with feedback end without emitter feedback of Q1

6) Taskk

Estimate the operating points of the transistors (I_{CQ} , U_{CEQ}) operating in the amplifier circuit from Figure6 . For calculations, assume: $R_{C1} = 15 \text{ k}\Omega$, $R_{C2} = 5 \text{ k}\Omega$, $R_{E2} = 1.2 \text{ k}\Omega$, $R_F = 100 \text{ k}\Omega$, $V_{CC} = 18 \text{ V}$, $U_{BE1} = U_{BE2} = 0.65 \text{ V}$, $\beta_1 = \beta_2 = 100$.

7) Task

Draw small-signal equivalent circuit diagrams of amplifier circuits from Figure7 in the medium, low and high frequencies.

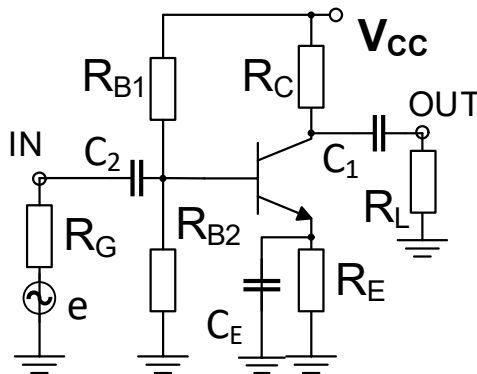


Figure7 . Common emitter amplifier.

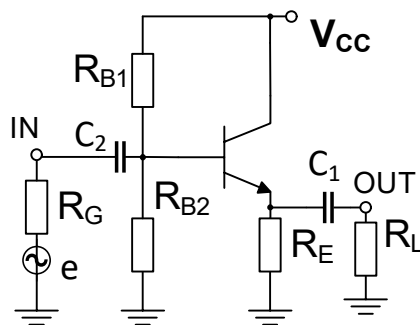


Figure8 . Common collector amplifier

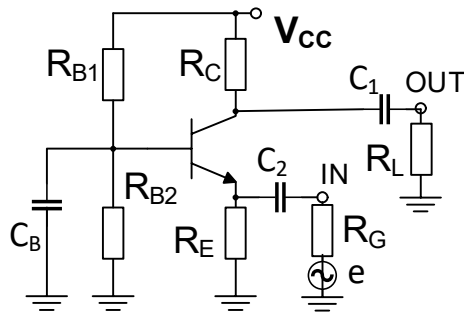


Figure9 . Common base amplifier

8) Task

Draw small-signal equivalent circuit diagrams of amplifier circuits with Figure 9 in the mid-frequency range.

9) Task

Estimate the equivalent parameters of small-signal equivalent models of a bipolar transistor operating at the operating point $I_{CQ} = 1 \text{ mA}$, $U_{CEQ} = 5 \text{ V}$. For calculations, assume $\beta = 100$, $U_{EY} = 100 \text{ V}$, $r_{bb'} = 50 \Omega$. a) hybrid π -type model;

- b) h matrix type model;
- c) y matrix type model.

10) Task

Estimate the effective voltage gain of the amplifier from Figure 7. For the calculation, assume: $R_{B1} = 56 \text{ k}\Omega$, $R_{B2} = 20 \text{ k}\Omega$, $R_C = 6.8 \text{ k}\Omega$, $R_E = 3.3 \text{ k}\Omega$, $R_G = 1 \text{ k}\Omega$, $R_L = 10 \text{ k}\Omega$, $\beta = 200$, transistor operating point $I_{CQ} = 1 \text{ mA}$, $U_{CEQ} = 5 \text{ V}$.

11) Task

Estimate the effective current gain of the amplifier from Figure 7. For the calculation, assume: $R_{B1} = 56 \text{ k}\Omega$, $R_{B2} = 20 \text{ k}\Omega$, $R_C = 6.8 \text{ k}\Omega$, $R_E = 3.3 \text{ k}\Omega$, $R_G = 1 \text{ k}\Omega$, $R_L = 10 \text{ k}\Omega$, $\beta = 200$, transistor operating point $I_{CQ} = 1 \text{ mA}$, $U_{CEQ} = 5 \text{ V}$.

12) Task

Estimate the input and output resistance of the amplifier from Figure 7. For calculations, assume: $R_{B1} = 56 \text{ k}\Omega$, $R_{B2} = 20 \text{ k}\Omega$, $R_C = 6.8 \text{ k}\Omega$, $R_E = 3.3 \text{ k}\Omega$, $R_G = 1 \text{ k}\Omega$, $R_L = 10 \text{ k}\Omega$, $\beta = 200$, transistor operating point $I_{CQ} = 1 \text{ mA}$, $U_{CEQ} = 5 \text{ V}$.

13) Task

Estimate the lower limit frequency of the amplifier circuit from Figure 7. For calculations, assume: $R_{B1} = 56 \text{ k}\Omega$, $R_{B2} = 20 \text{ k}\Omega$, $R_C = 6.8 \text{ k}\Omega$, $R_E = 3.3 \text{ k}\Omega$, $C(1) = 1 \mu\text{F}$, $C(2) = 1 \mu\text{F}$, $C(E) = 100 \mu\text{F}$, $R(G) = 1 \text{ k}\Omega$, $R(L) = 10 \text{ k}\Omega$, $\beta = 200$, transistor operating point $I_{CQ} = 1 \text{ mA}$, $U_{CEQ} = 5 \text{ V}$.

14) Taskk

Estimate the upper limit frequency of the amplifier circuit from Figure 7. For calculations, assume: $R_{B1} = 56 \text{ k}\Omega$, $R_{B2} = 20 \text{ k}\Omega$, $R_C = 6.8 \text{ k}\Omega$, $R_E = 3.3 \text{ k}\Omega$, $C_{bc} = 4.5 \text{ pF}$, $f_T = 150 \text{ MHz}$, $R(G) = 1 \text{ k}\Omega$, $R_L = 10 \text{ k}\Omega$, $\beta = 200$, transistor operating point $I_{CQ} = 1 \text{ mA}$, $U_{CEQ} = 5 \text{ V}$.

15) Task

Estimate the effective voltage gain of the amplifier from Figure 8. For the calculation, assume: $R_{B1} = 570 \text{ k}\Omega$, $R_{B2} = 3.9 \text{ M}\Omega$, $R_E = 10 \text{ k}\Omega$, $R_G = 5 \text{ k}\Omega$, $R_L = 10 \text{ k}\Omega$, $\beta = 200$, transistor operating point $I_{CQ} = 1 \text{ mA}$, $U_{CEQ} = 5 \text{ V}$.

16) Task

Estimate the effective current gain of the amplifier from Figure 8. For the calculation, assume: $R_{B1} = 570 \text{ k}\Omega$, $R_{B2} = 3.9 \text{ M}\Omega$, $R_E = 10 \text{ k}\Omega$, $R_G = 5 \text{ k}\Omega$, $R_L = 10 \text{ k}\Omega$, $\beta = 200$, transistor operating point $I_{CQ} = 1 \text{ mA}$, $U_{CEQ} = 5 \text{ V}$.

17) Task

Estimate the input and output resistance of the amplifier from Figure 8. For calculations, assume: $R_{B1} = 570 \text{ k}\Omega$, $R_{B2} = 3.9 \text{ M}\Omega$, $R_E = 10 \text{ k}\Omega$, $R_G = 5 \text{ k}\Omega$, $R_L = 10 \text{ k}\Omega$, $\beta = 200$, transistor operating point $I_{CQ} = 1 \text{ mA}$, $U_{CEQ} = 5 \text{ V}$.

18) Task

Estimate the effective voltage gain of the amplifier from Figure 9. For the calculation, assume: $R_{B1} = 100 \text{ k}\Omega$, $R_{B2} = 20 \text{ k}\Omega$, $R_C = 500 \Omega$, $R_E = 1 \text{ k}\Omega$, $R_G = 20 \Omega$, $R_L = 10 \text{ k}\Omega$, $\beta = 200$, transistor operating point $I_{CQ} = 1 \text{ mA}$, $U_{CEQ} = 10 \text{ V}$.

19) Task

Estimate the effective current gain of the amplifier from Figure 9. For the calculation, assume: $R_{B1} = 100 \text{ k}\Omega$, $R_{B2} = 20 \text{ k}\Omega$, $R_C = 500 \Omega$, $R_E = 1 \text{ k}\Omega$, $R_G = 20 \Omega$, $R_L = 10 \text{ k}\Omega$, $\beta = 200$, transistor operating point $I_{CQ} = 1 \text{ mA}$, $U_{CEQ} = 10 \text{ V}$.

20) Task

Estimate the input and output resistance of the amplifier from Figure 9. For calculations, assume: $R_{B1} = 100 \text{ k}\Omega$, $R_{B2} = 20 \text{ k}\Omega$, $R_C = 500 \Omega$, $R_E = 1 \text{ k}\Omega$, $R_G = 20 \Omega$, $R_L = 10 \text{ k}\Omega$, $\beta = 200$, transistor operating point $I_{CQ} = 1 \text{ mA}$, $U_{CEQ} = 10 \text{ V}$.